



**SNS COLLEGE OF ENGINEERING**

**(Autonomous)**

**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**



**23ECT203 - LINEAR INTEGRATED CIRCUITS**

# Ideal OP-AMP characteristics

23ECT203/ LIC/ Ms.V.Aishwarya, AP/ECE

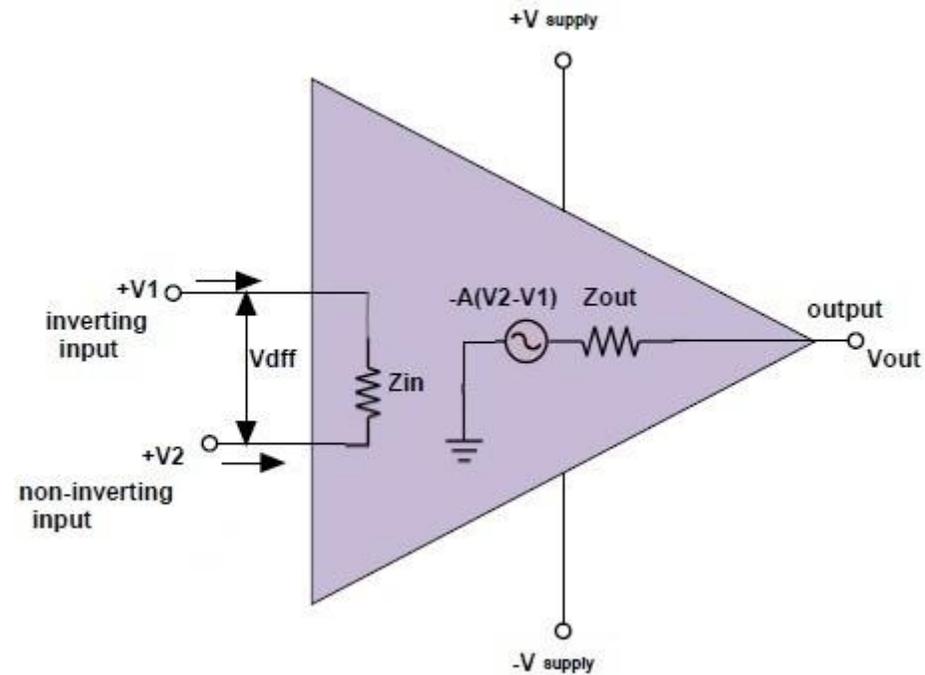




# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



- Infinite input impedance
- Zero output impedance
- Zero common-mode gain, or, infinite common-mode rejection
- Infinite open-loop gain  $A$
- Infinite bandwidth.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Infinite Open-Loop Gain (AOL): An ideal op-amp has an infinitely large open-loop gain. This means that it can amplify input signals to an arbitrarily large output voltage without any limitations. In practical op-amps, the open-loop gain is very high, but it is not infinite.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Infinite Input Impedance: The ideal op-amp has infinite input impedance, which means that it draws no current into its inputs. As a result, the voltage at the inverting and non-inverting inputs is the same (virtual short circuit), making the analysis of op-amp circuits easier.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Zero Output Impedance: The ideal op-amp has zero output impedance, which means that it can drive any load without any voltage drop. In reality, op-amps have low but finite output impedance.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Infinite Bandwidth: An ideal op-amp has an infinitely wide bandwidth, allowing it to amplify signals of any frequency without distortion. In practice, op-amps have a limited bandwidth that decreases at higher frequencies.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Zero Input Offset Voltage: The ideal op-amp has zero input offset voltage, meaning that there is no voltage difference between its inverting and non-inverting inputs when the output is zero. In real op-amps, there is a small offset voltage that can introduce errors.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Infinite Slew Rate: The ideal op-amp has an infinitely fast slew rate, meaning it can instantly respond to changes in the input voltage. In practice, op-amps have a finite slew rate that limits their response to fast input voltage changes.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Infinite Common-Mode Rejection Ratio (CMRR): An ideal op-amp rejects any common-mode voltage applied to its inputs, amplifying only the differential voltage. This property ensures that noise and interference on both inputs do not affect the output. In real op-amps, CMRR is very high but not infinite.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



No Noise: The ideal op-amp is noiseless, meaning it does not introduce any noise at its inputs or outputs. In real op-amps, noise is present, and its magnitude depends on the op-amp's design and manufacturing.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Infinite Power Supply Rejection Ratio (PSRR): An ideal op-amp is immune to changes in the power supply voltage, meaning that variations in the supply voltage do not affect its performance. In reality, PSRR is high but not infinite.





# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Thank  
you

