



## INDUSTRIAL ELECTRONICS

### TWO MARKS

#### UNIT V

- 1. What is the difference between ON-OFF control and phase control?**
  - a. ON-OFF control: In this method, the thyristors are employed as switches to connect the load circuit to the source for a few cycles of the load voltage and disconnect it for another few cycles. Phase control: In this method, thyristor switches connect the load to the ac source for a portion of each half cycle of input voltage.
  
- 2. What is the advantage of ON-OFF control?**
  - a. Due to zero-voltage and zero current switching of thyristors, the harmonics generated by the switching action are reduced.
  
- 3. What is the disadvantage of ON-OFF control?**
  - a. This type of control is applicable in systems that have high mechanical inertia and high thermal time constant.
  
- 4. What is the duty cycle in ON-OFF control method?**
  - a. Duty cycle  $K = n / (n + m)$ , where  $n =$  no. of ON cycles,  $m =$  no. of OFF cycles
  
- 5. What is meant by unidirectional or half-wave ac voltage controller?**
  - a. Here the power flow is controlled only during the positive half-cycle of the input voltage.
  
- 6. . What are the disadvantages of unidirectional or half-wave ac voltage controller?**
  - a. Due to the presence of diode on the circuit, the control range is limited and the effective RMS output voltage can be varied between 70.7% and 100%. b. The input current and output voltage are asymmetrical and contain a dc component. If there is an input transformer, saturation problem will occur. It is only used for low power resistive load.
  
- 7. What is meant by bidirectional or half-wave ac voltage controller?**

Here the power flow is controlled during both cycles of the input voltage.
  
- 8. What is the control range of firing angle in ac voltage controller with RL load?**

The control range is  $F < \alpha < 180^\circ$ , where  $F =$  load power factor angle.

- 9. What type of gating signal is used in single phase ac voltage controller with RL load?**  
High frequency carrier gating signal is used for single phase ac voltage controller with RL load.
- 10. What are the disadvantages of continuous gating signal?**  
a. More heating of the SCR gate.  
b. Increases the size of pulse transformer.
- 11. What is meant by high frequency carrier gating?**  
Thyristor is turned on by using a train of pulses from a to p. This type of signal is called as high frequency carrier gating.
- 12. What is meant by sequence control of ac voltage regulators?**  
It means that the stages of voltage controllers in parallel triggered in a proper sequence one after the other so as to obtain a variable output with low harmonic content.
- 13. What are the advantages of sequence control of ac voltage regulators?**  
a. System power factor is improved.  
b. Harmonics are reduced in the source current and the load voltage.
- 14. What is meant by cyclo-converter?**  
It converts input power at one frequency to output power at another frequency with one-stage conversion. Cycloconverter is also known as frequency changer.
- 15. What are the two types of cyclo-converters?**  
a. Step-up cyclo-converters  
b. Step-down cyclo-converters
- 16. What is meant by step-up cyclo-converters?**  
In these converters, the output frequency is less than the supply frequency.
- 17. What is meant by step-down cyclo-converters?**  
In these converters, the output frequency is more than the supply frequency.
- 18. What are the applications of cyclo-converter?**  
a. Induction heating  
b. Speed control of high-power ac drives  
c. Static VAR generation  
d. Power supply in aircraft or ship boards
- 19. What is meant by positive converter group in a cyclo converter?**  
The part of the cycloconverter circuit that permits the flow of current during Positive half cycle of output current is called positive converter group.
- 20. What is meant by negative converter group in a cyclo converter?**  
The part of the cyclo converter circuit that permits the flow of current during negative half cycle of output current is called negative converter group.