



SNS College  
of Engineering

# SNS COLLEGE OF ENGINEERING

Coimbatore  
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

**19EET501 / POWER ELECTRONICS AND DRIVES**

**V SEM EEE**

**UNIT 3 –AC CONVERTERS**

**THREE PHASE INVERTER (180 degree)**

Dr. C. UDHAYA SHANKAR

ASP/EEE, SNSCE




SNS College  
of Engineering

SNS COLLEGE OF TECHNOLOGY, COIMBATORE  
(An Autonomous Institution)  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING



# A 3-phase Inverter

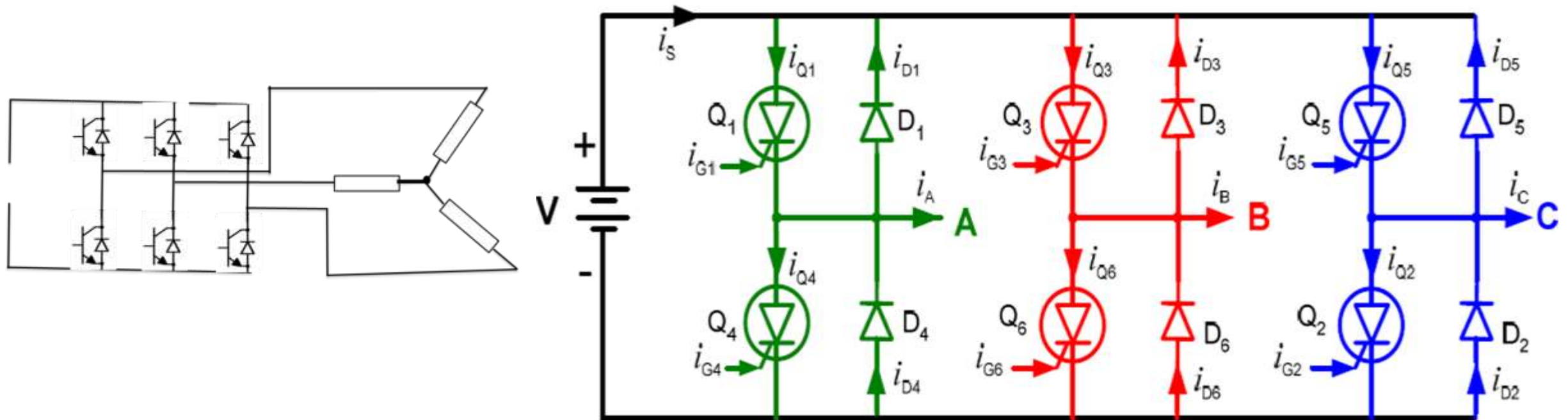



SNS College  
of Engineering

SNS COLLEGE OF TECHNOLOGY, COIMBATORE  
(An Autonomous Institution)  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING



- This is a controlling scheme for 3-phase inverter.
- Each switch conduct for period of 180 degree.
- Switches are triggered in sequence of their numbers with an interval of  $60^\circ$ .
- At a time, three switches(one from each leg) conduct.
- Two switches of same leg are prevented from conducting.
- Switch pair in each leg, i.e. S1 , S4,S3 , S6 and S5 , S2.
- One complete cycle is divide into 6 modes.



SNS College  
of Engineering

SNS COLLEGE OF TECHNOLOGY, COIMBATORE  
(An Autonomous Institution)  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING



S.NO	INTERVAL	DEVICE CONDUCTING	INCOMING DEVICE	OUTGOING DEVICE
1	I	5, 6, 1	1	4
2	II	6, 1, 2	2	5
3	III	1, 2, 3	3	6
4	IV	2, 3, 4	4	1
5	V	3, 4, 5	5	2
6	VI	4, 5, 6	6	3




SNS College  
of Engineering

SNS COLLEGE OF TECHNOLOGY, COIMBATORE  
(An Autonomous Institution)  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING




## Waveform of gating signals

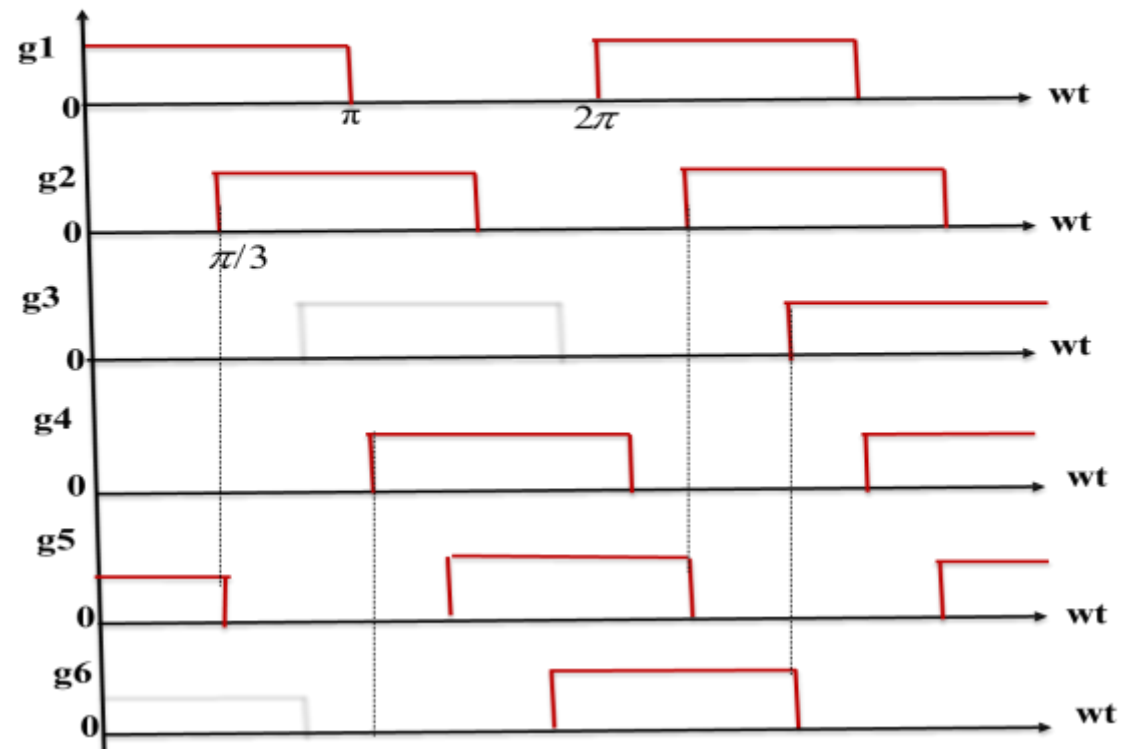




# Mode 1 Operation

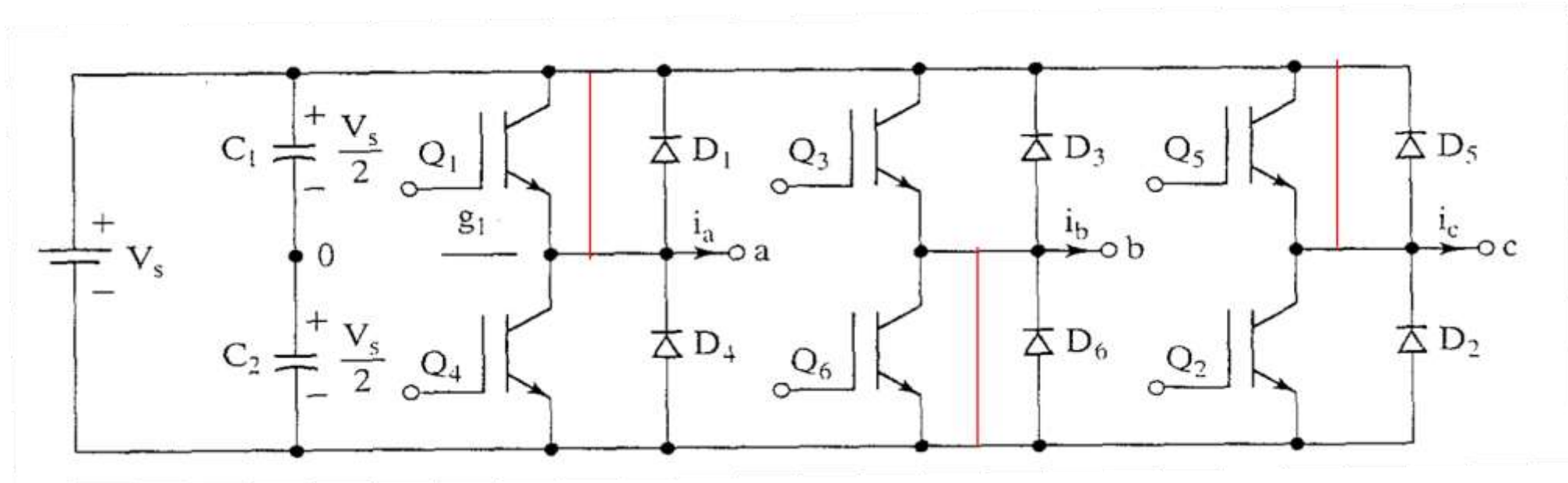

## Mode 1 Operation

$$0 \leq \omega t \leq \frac{\pi}{3}$$

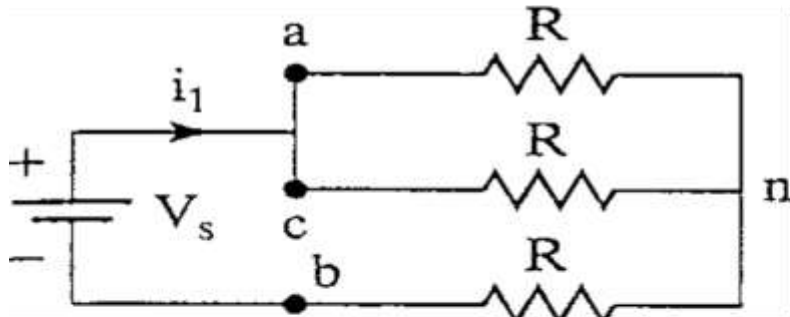

$Q_1, Q_5, Q_6$  conduct

$$R_{eq} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_1 = \frac{V_s}{R_{eq}} = \frac{2V_s}{3R}$$

$$v_{an} = v_{cn} = \frac{i_1 R}{2} = \frac{V_s}{3}$$

$$v_{bn} = -i_1 R = \frac{-2V_s}{3}$$




SNS College  
of Engineering

SNS COLLEGE OF TECHNOLOGY, COIMBATORE  
(An Autonomous Institution)  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING




# Mode 2 Operation

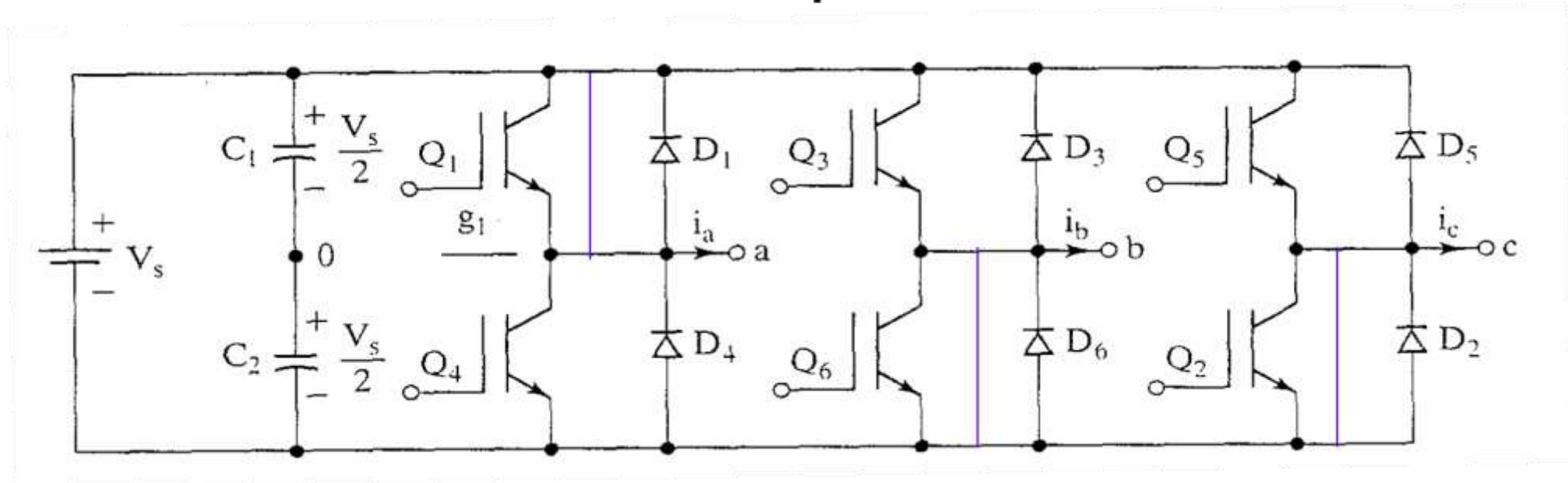


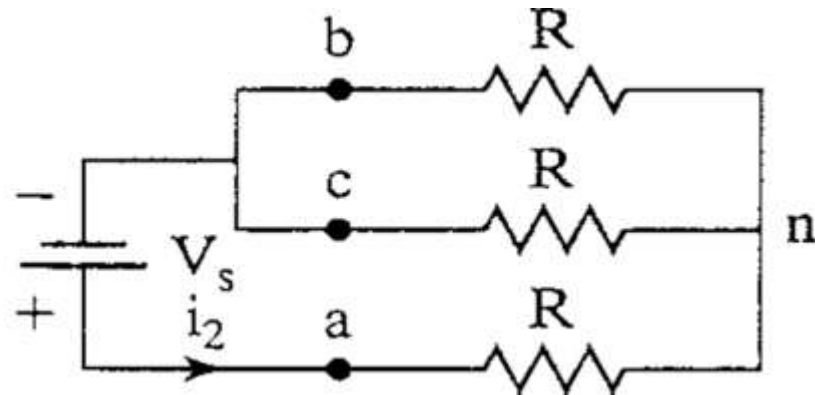
## Mode 2 Operation

$$\frac{\pi}{3} \leq \omega t \leq \frac{2\pi}{3}$$



$Q_1, Q_2, Q_6$  conduct


$$R_{eq} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_2 = \frac{V_s}{R_{eq}} = \frac{2V_s}{3R}$$

$$v_{an} = i_2 R = \frac{2V_s}{3}$$


$$v_{bn} = v_{cn} = \frac{i_2 R}{2} = \frac{V_s}{3}$$

### Mode 3 Operation

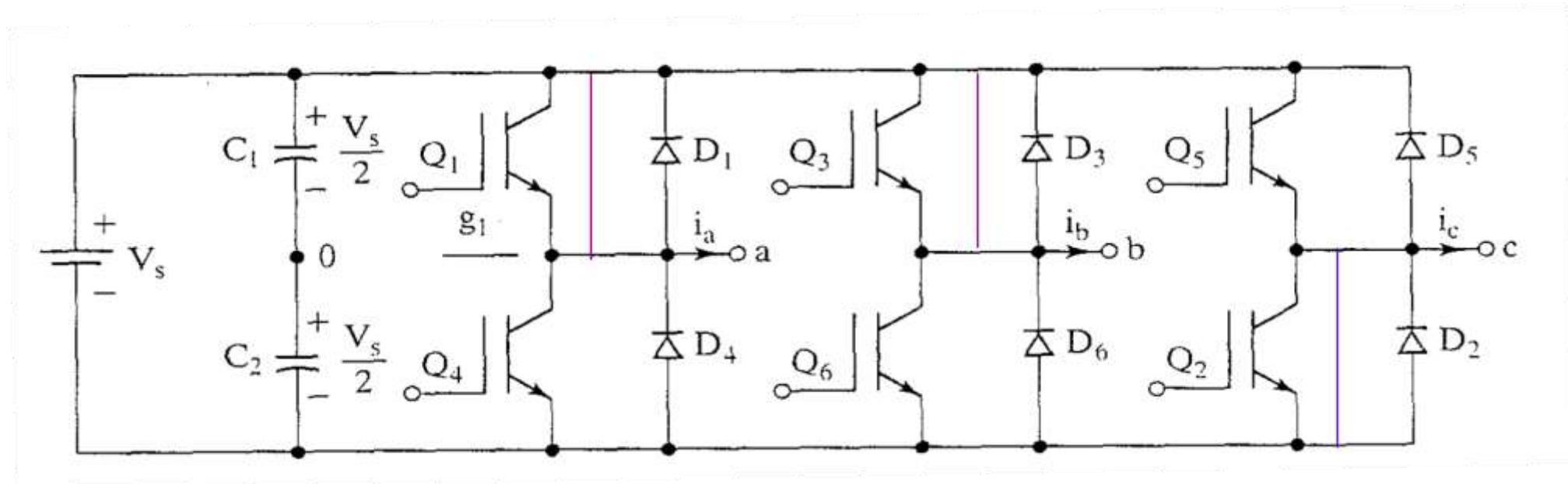
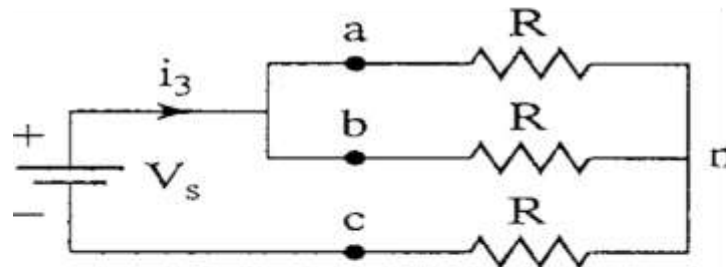
## Mode 3 Operation

$$\frac{2\pi}{3} \leq \omega t \leq \pi$$



$Q_1, Q_2, Q_3$  conduct

$$R_{eq} = R + \frac{R}{2} = \frac{3R}{2}$$

$$i_3 = \frac{V_s}{R_{eq}} = \frac{2V_s}{3R}$$

$$v_{an} = v_{bn} = \frac{i_3}{2}$$

$$v_{cn} = i_3 R = \frac{-2V_s}{3}$$



SNS College  
of Engineering

SNS COLLEGE OF TECHNOLOGY, COIMBATORE  
(An Autonomous Institution)  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING



## Output phase voltage for star connected load

INTERVAL	I	II	III	IV	V	VI
$V_{AN}$	$\frac{V_s}{3}$	$\frac{2V_s}{3}$	$\frac{V_s}{3}$	$-\frac{V_s}{3}$	$-\frac{2V_s}{3}$	$-\frac{V_s}{3}$
$V_{BN}$	$-\frac{2V_s}{3}$	$-\frac{V_s}{3}$	$\frac{V_s}{3}$	$\frac{2V_s}{3}$	$\frac{V_s}{3}$	$-\frac{V_s}{3}$
$V_{CN}$	$\frac{V_s}{3}$	$-\frac{V_s}{3}$	$-\frac{2V_s}{3}$	$-\frac{V_s}{3}$	$\frac{V_s}{3}$	$\frac{2V_s}{3}$

# Phase Voltages for 180° Conduction

