



# **SNS COLLEGE OF ENGINEERING**

**Coimbatore-35**  
**An Autonomous Institution**

Accredited by – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19EC505–VLSI DESIGN**

III YEAR/<sub>1</sub> V SEMESTER

**UNIT 2 –COMBINATIONAL LOGIC CIRCUITS**


**TOPIC –Transmission Gate Logic**



 
# Transmission Gate Logic



- The most widely-used solution to deal with the voltage-drop problem is the use of transmission gates.
- It builds on the complementary properties of NMOS and PMOS transistors: NMOS devices pass a strong 0 but a weak 1, while PMOS transistors pass a strong 1 but a weak 0.
- The ideal approach is to use an NMOS to pull-down and a PMOS to pull-up.
- The transmission gate combines the best of both device flavors by placing a NMOS device in parallel with a PMOS device. The control signals to the transmission gate ( $\bar{C}$  and  $C$ ) are complementary



(a) Circuit

 


(b) Symbolic representation

### CMOS transmission gate



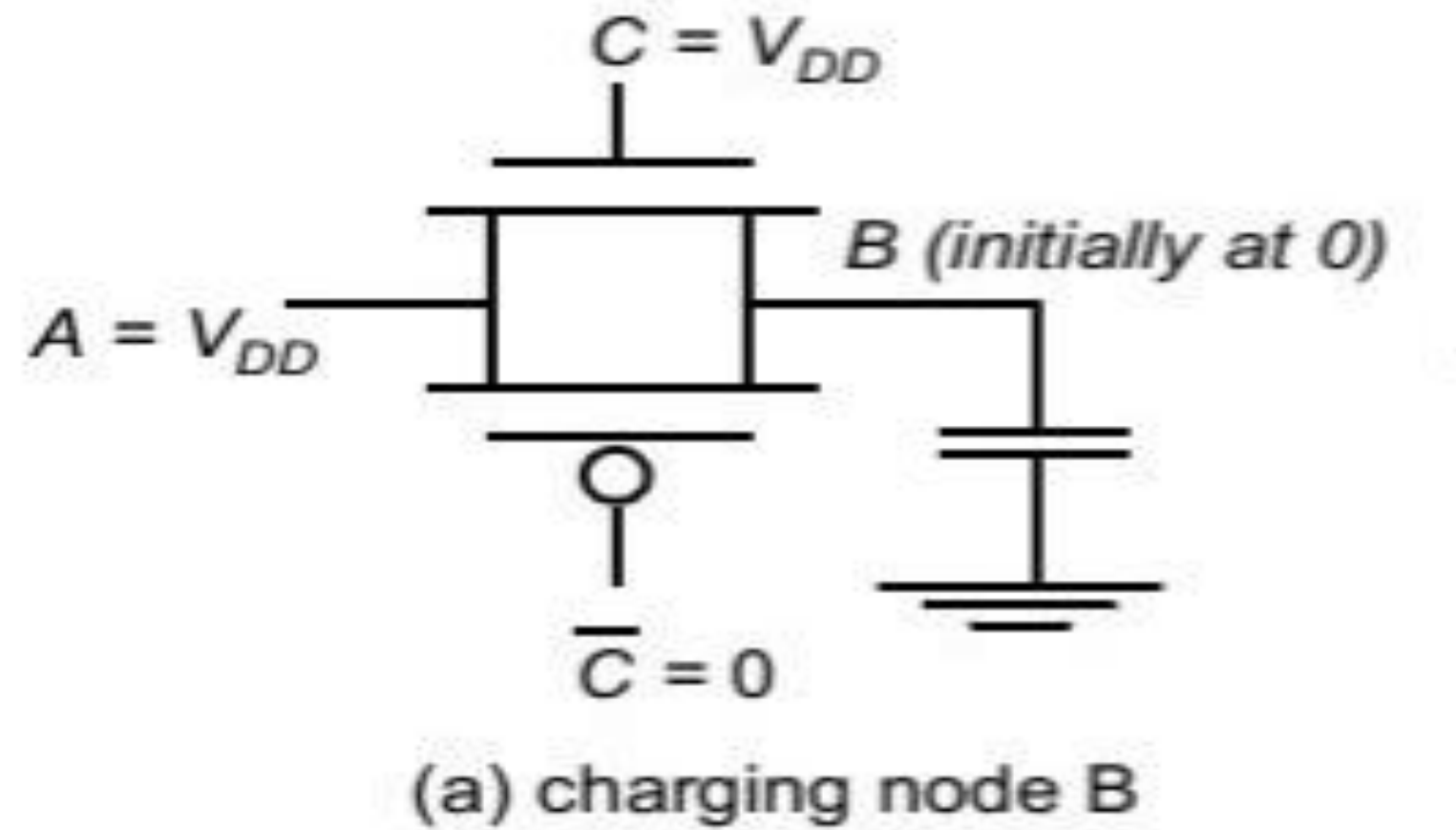
# Transmission gates enable rail-to-rail switching




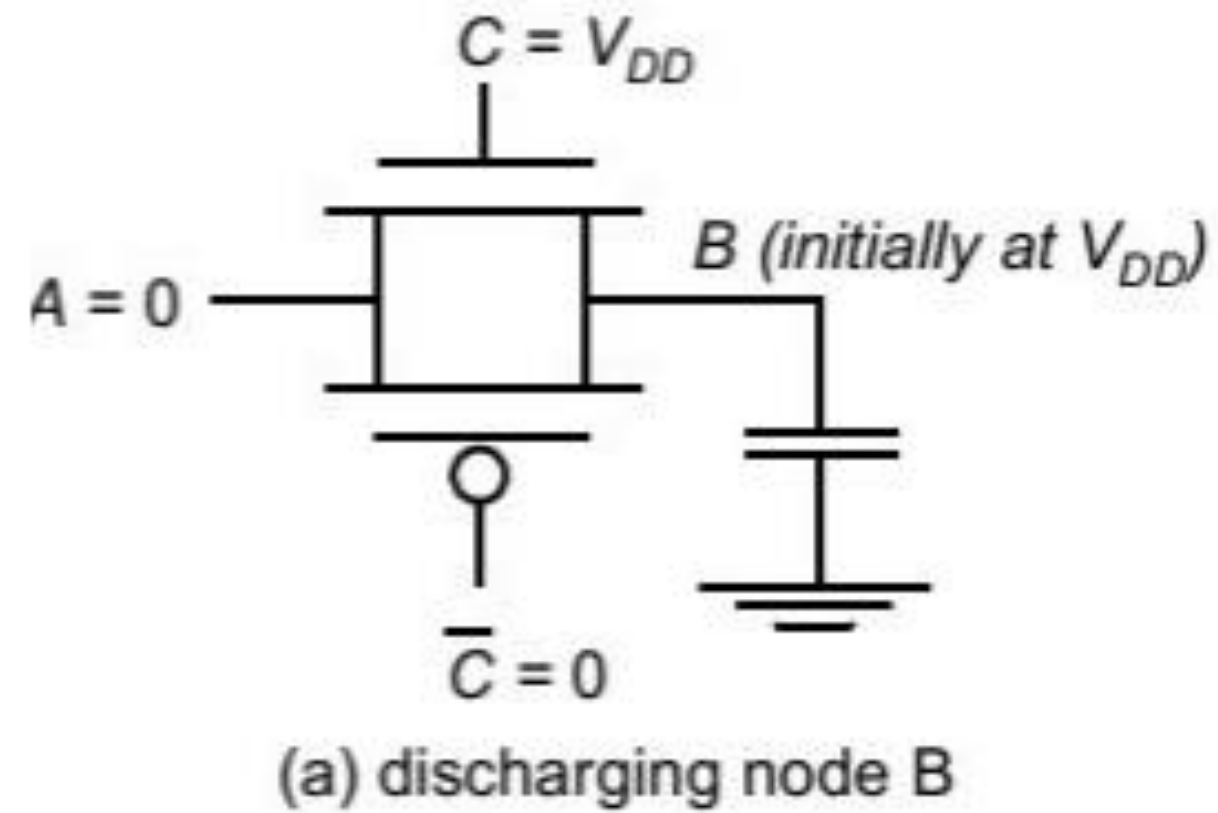
# Transmission gates enable rail-to-rail switching





**THANK YOU**