



# SNS COLLEGE OF ENGINEERING

Coimbatore-35  
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

- DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

- 19EC505–VLSI DESIGN

- III YEAR/ V SEMESTER

1

## UNIT 2 –COMBINATIONAL LOGIC CIRCUITS

### TOPIC – STATIC AND DYNAMIC CMOS DESIGN



## OUTLINE



- **STATIC VS DYNAMIC CMOS DESIGN**
- **COMPLEMENTARY CMOS LOGIC GATES**
- **NMOS OPERATION**
- **COMPLEX GATE**
- **DYNAMIC CIRCUIT LOGIC**
- **PRECHARGE & EVALUATE**
- **ACTIVITY**
- **COMPARISON OF CMOS CIRCUITS & EVALUATE CONTD..NMOS OPERATION**
- **ADVANTAGES**
- **DYNAMIC LOGIC PROBLEMS**
- **ASSESSMENT**
- **SUMMARY & THANK YOU**



# STATIC VS DYNAMIC CMOS DESIGN




## Static

Each gate output have a low resistive path to either  $V_{DD}$  or GND
 
## Dynamic

Relies on storage of signal the value in a capacitance  
requires high impedance nodes



**PUN and PDN are Dual Networks**




# COMPLEMENTARY CMOS LOGIC GATES



- nMOS pull-down network
- pMOS pull-up network
- a.k.a. static CMOS

	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

 




# EXAMPLE GATE: NAND



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

**Truth Table of a 2 input NAND gate**

 



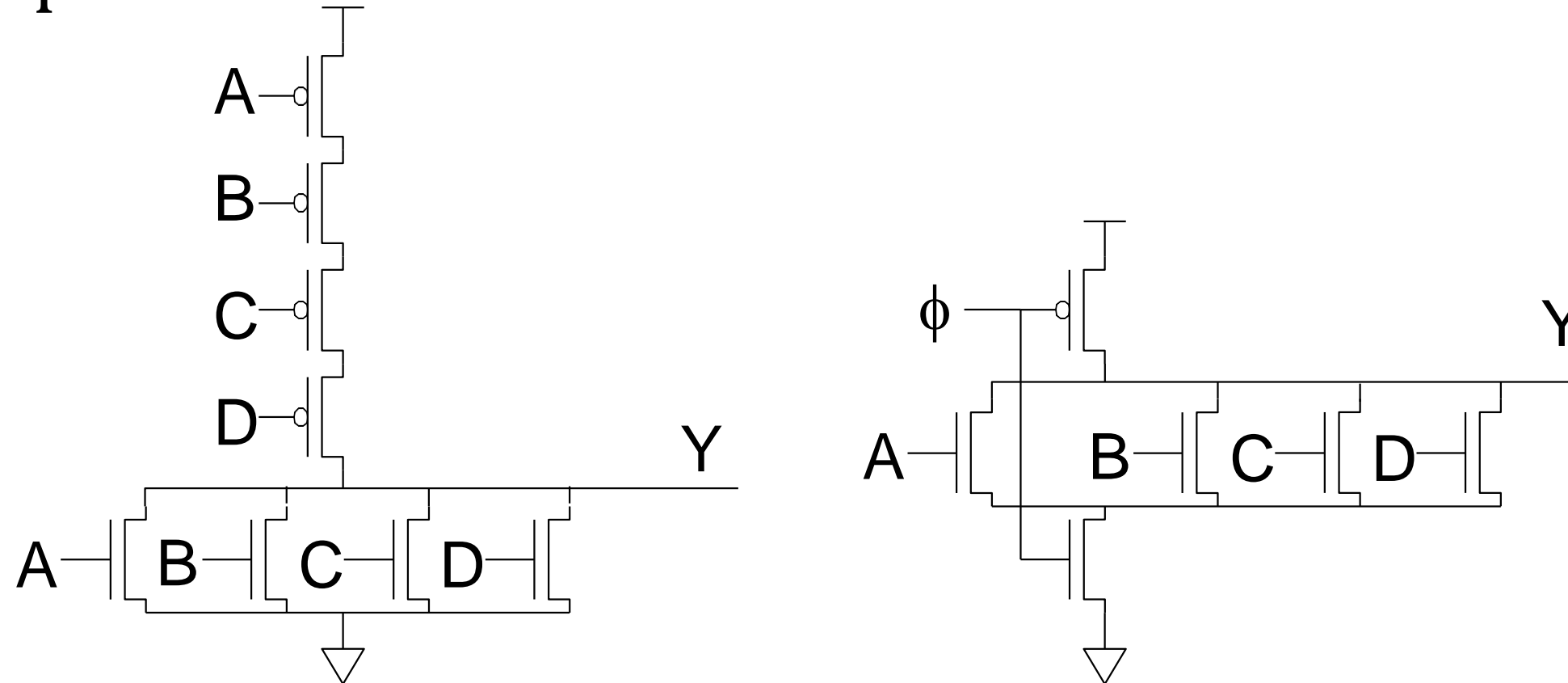
# DYNAMIC C-MOS LOGIC CIRCUITS-BASIC PRINCIPLES-INTRODUCTION



- Dynamic gates use a clocked pMOS pull-up
- To design high speed cascades
- Some cascades dissipates large amt of power
- Slow pFETs eliminate, clk- used for gate, data syn.
- Complex electric char.





## DYNAMIC CIRCUIT LOGIC




Static circuits are slow because fat pMOS load input

Dynamic gates use precharge to remove pMOS transistors from the inputs

**Precharge:**  $f = 0$  output forced high



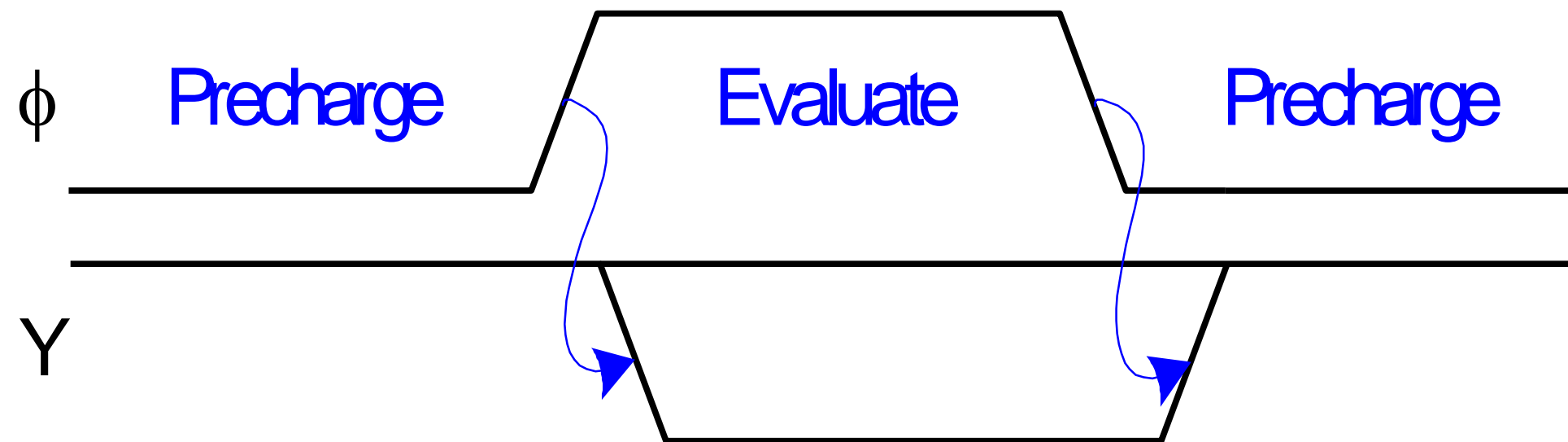
**Evaluate:**  $f = 1$  output may pull low





  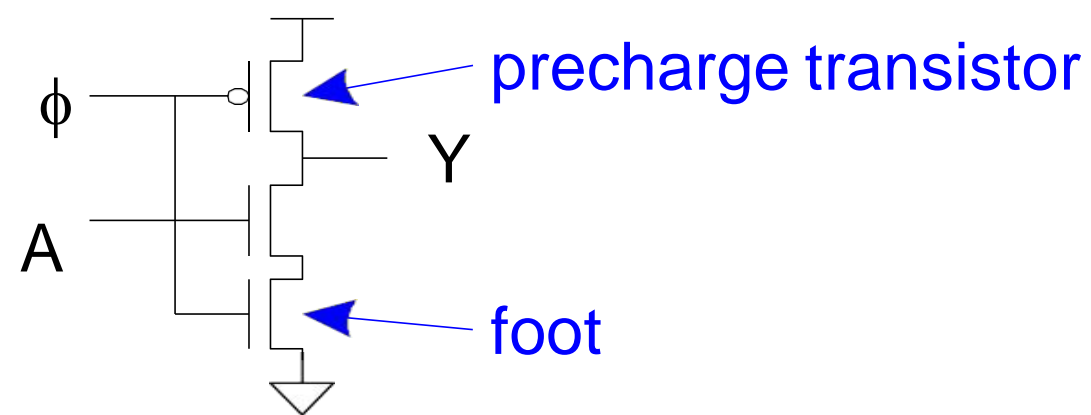
# THE FOOT

- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.





## DYNAMIC LOGIC: PRINCIPLES

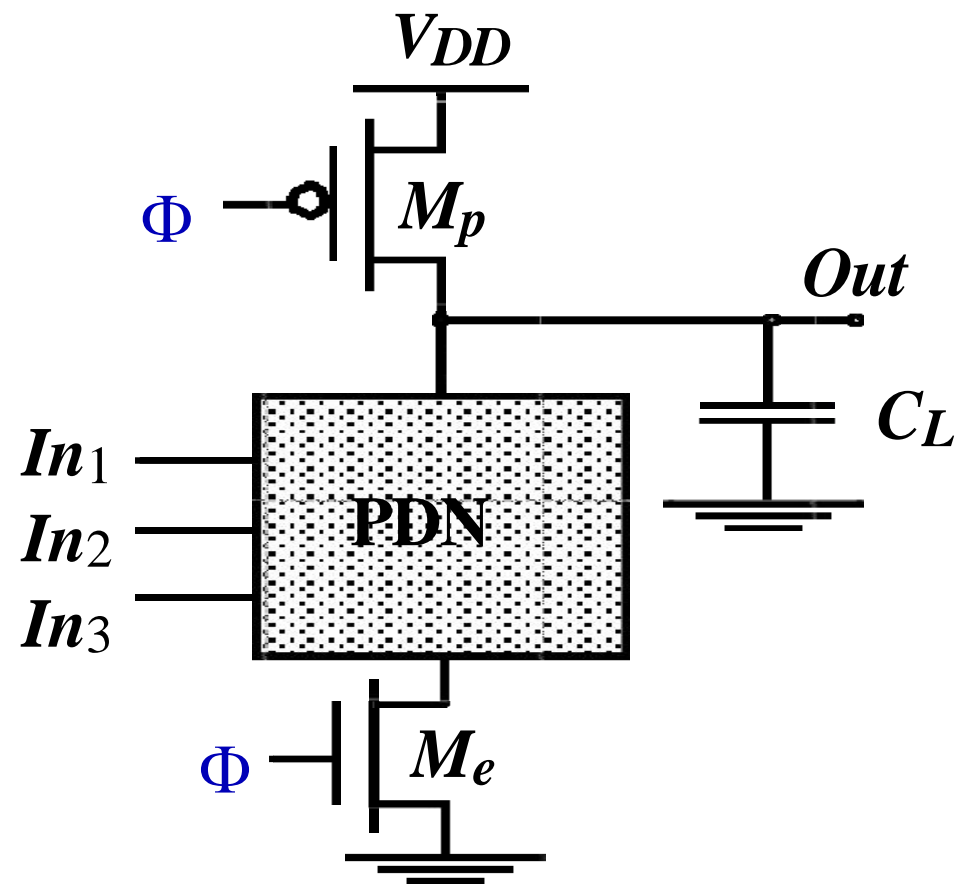

- **Precharge:**  $\Phi = 0$ ,  $Out$  is precharged to  $V_{DD}$  by  $M_p$ .  $M_e$  is turned off, no dc current flows (regardless of input values)
- **Evaluation**  
 $\Phi = 1$ ,  $M_e$  is turned on,  $M_p$  is turned off. Output is pulled down to zero depending on the values on the inputs. If not, precharged value remains on  $C_L$ .

**Important:** Once  $Out$  is discharged, it cannot be charged again! Gate input can make only one transition during evaluation

- Minimum clock frequency must be maintained
- Can  $M_e$  be eliminated?



## PRECHARGE & EVALUATE



It uses single clk ctrl comple.pair-Mp,Mn


Array of nFET-open or closed switch dep. on i/p(any one FET enough for 'sw')  
oper. ctrl by clk

**Clk=0** → precharge Mp-ON,Mn-OFF

Cout to charge to value  $V_{out}=V_{dd}$ ,every half cycle

**Clk=1** → evaluate of the operational cycle

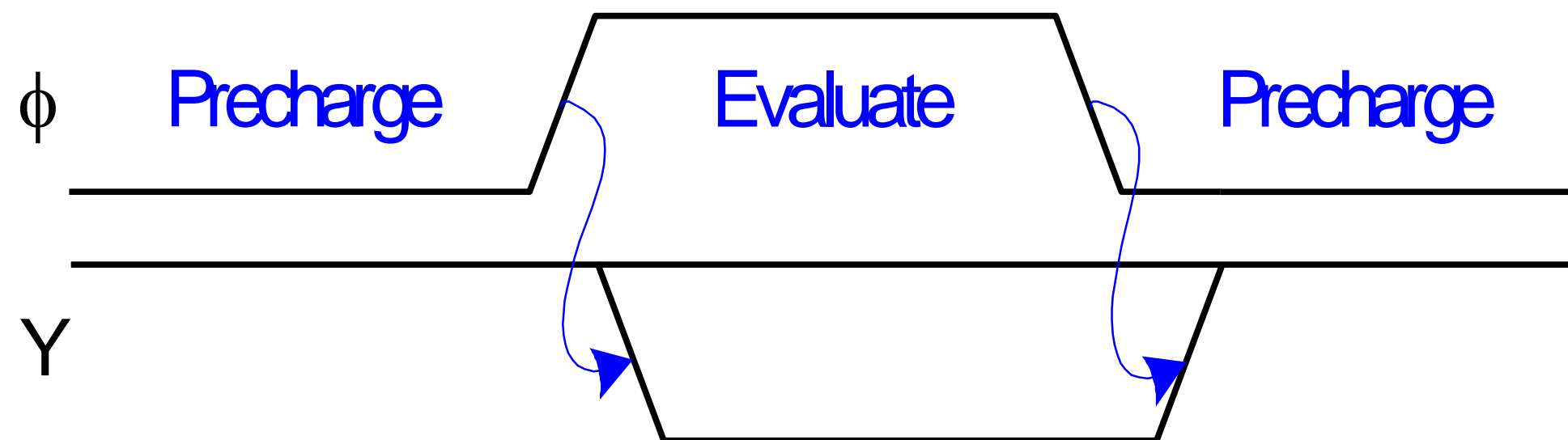Mp-OFF,Mn-ON.a,b,c accept into nFET logic array



# ACTIV ITY

## BRAIN TEASER




**Look at this series:**

**7, 10, 8, 11, 9, 12, ...**

**What number should come  
next?**


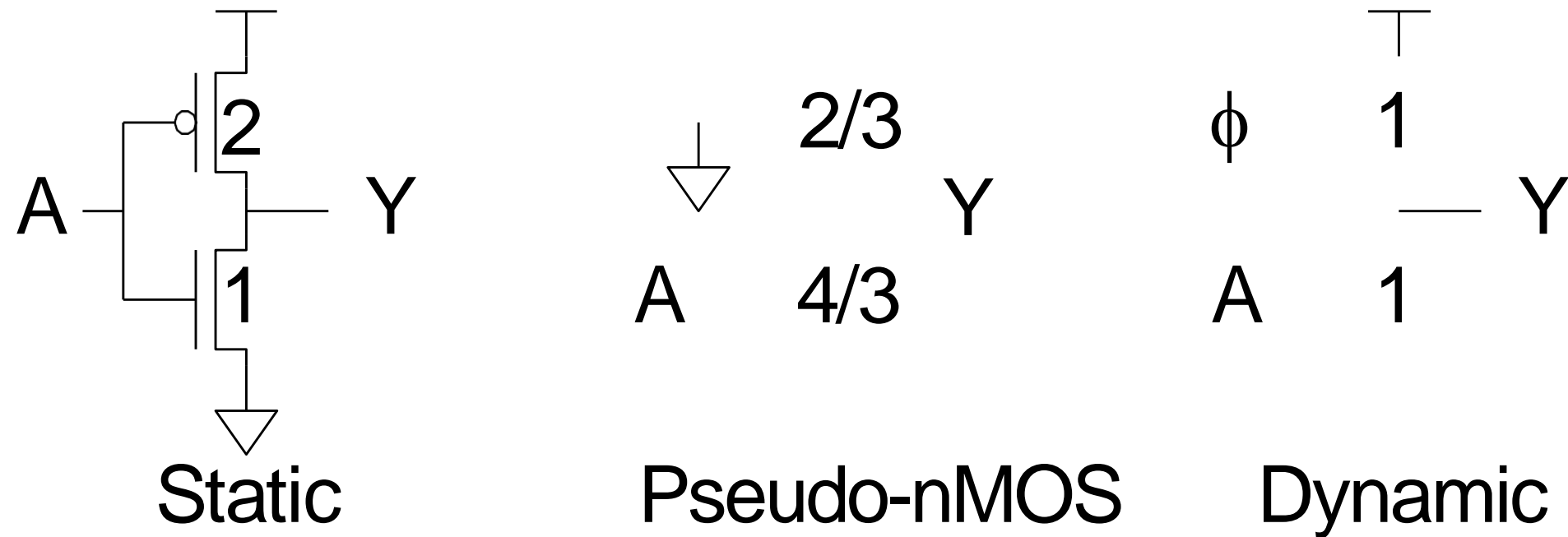
# COMPARISON OF CMOS CIRCUITS & EVALUATE CONTD..



If array acts open sw  $\rightarrow$   $V_{out}$  held at  $V_{dd} = f = 1$ .

If closed sw  $\rightarrow$   $C_{out} - V_{out} = 0v$ , so  $f = 0$

\*the sequence occurs every clk cycle

Ex:

**DYNAMIC NOR2, NAND2 GATES**



# DYNAMIC LOGIC ADVANTAGES



- To design high speed cascades
- Some cascades dissipates large amt of power
- Slow pFETs eliminate, clk- used for gate, data syn.
- Complex electric char.
- $N+2$  transistors for  $N$ -input function
  - Better than  $2N$  transistors for complementary static CMOS
  - Comparable to  $N+1$  for ratio-ed logic
- No static power dissipation
  - Better than ratio-ed logic
- Careful design, clock signal needed



# DYNAMIC LOGIC PROBLEMS




- Monotonicity
- Charge Leakage
- Charge Sharing
- Capacitive Coupling
- Clock Feed through


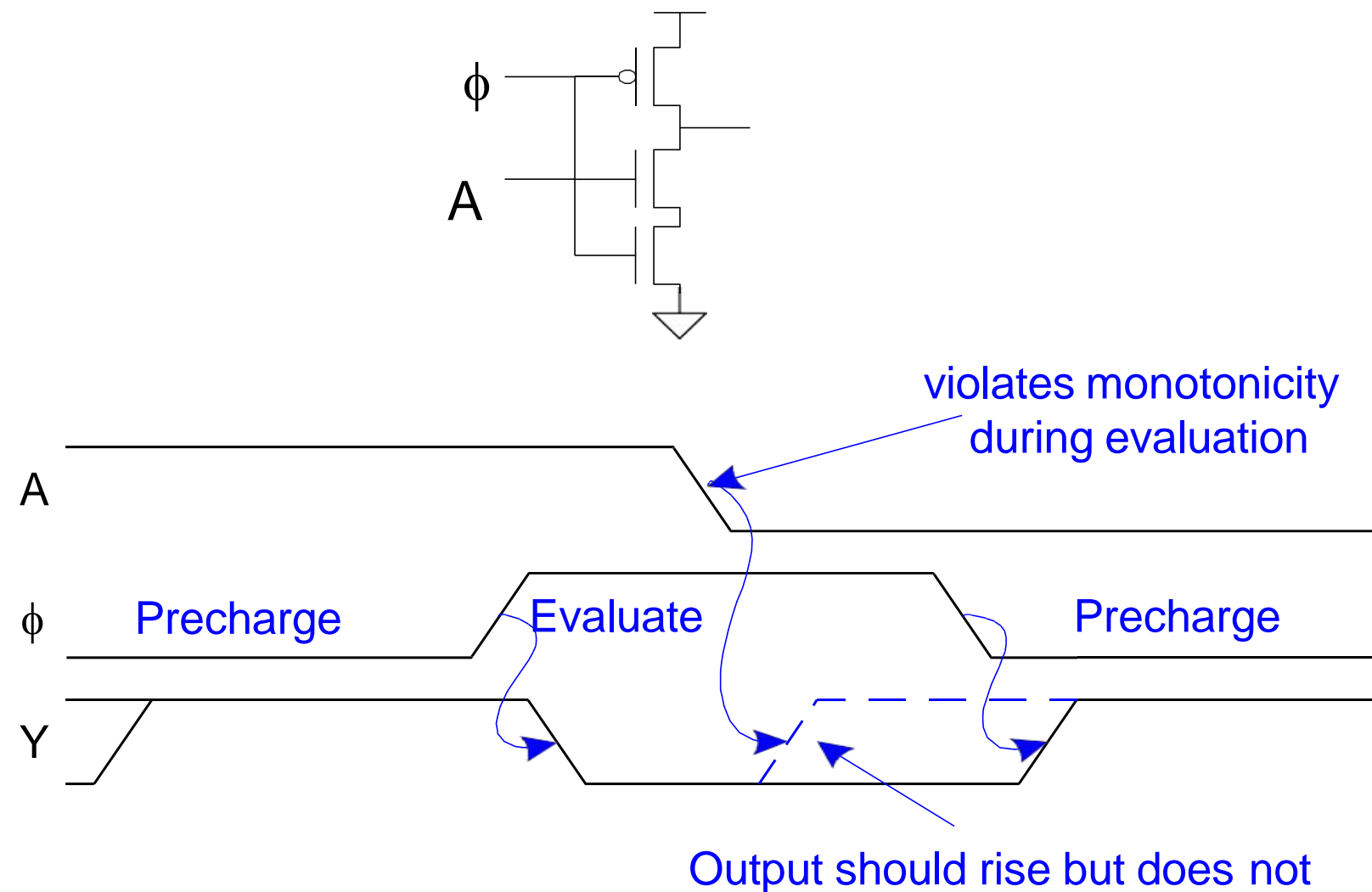
# MONOTONICITY



- Dynamic gates require monotonically rising inputs during evaluation
  - 0 -> 0
  - 0 -> 1
  - 1 -> 1
  - But not 1 -> 0






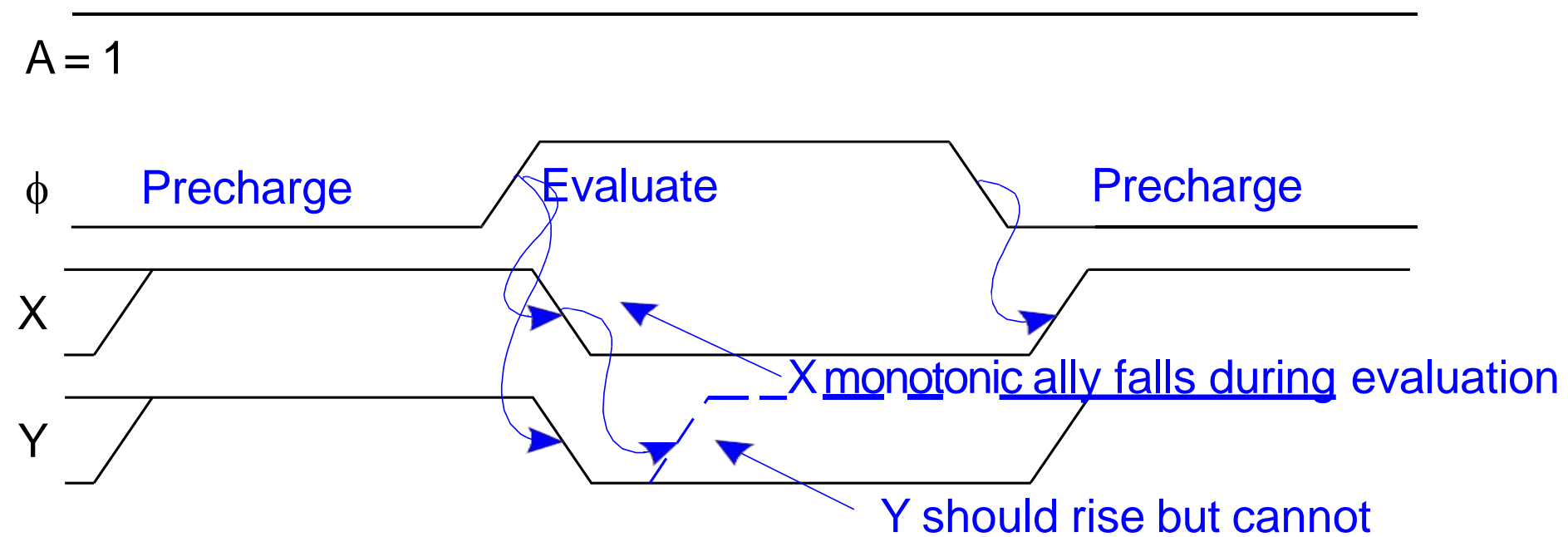 
# MONOTONICITY WOES



- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




STATIC AND DYNAMIC CMOS

DESIGN / 19EC505-VLSI


DESIGN//T.G.Ramabharathi/Ass  
istsn



# RELIABILITY PROBLEMS — CHARGE LEAKAGE

 

(a) Leakage sources

 

(b) Effect on waveforms

(1) Leakage through reverse-biased diode of the diffusion area

(2) Subthreshold current from drain to source


Minimum Clock Frequency:  $> 1$  MHz



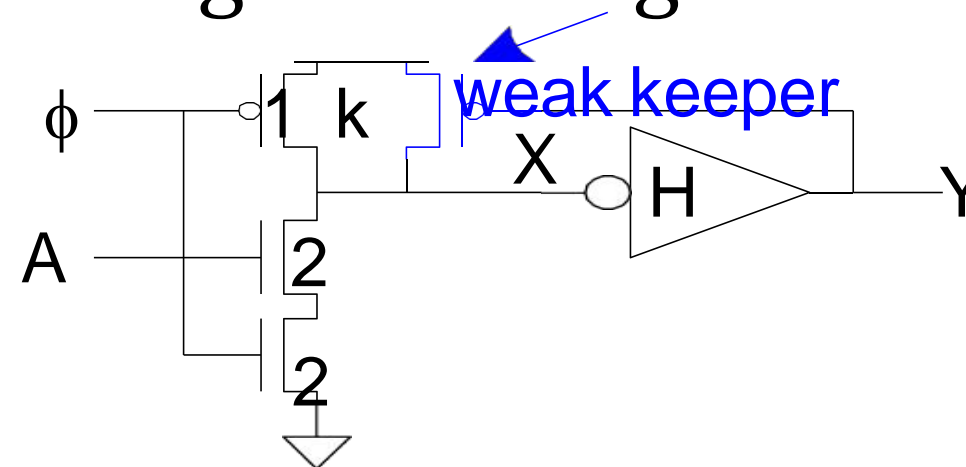
## LEAKAGE




- Dynamic node floats high during evaluation
  - Transistors are leaky ( $I_{OFF} \neq 0$ )
  - Dynamic value will leak away over time
  - Formerly miliseconds, now nanoseconds!
- Use keeper to hold dynamic node
  - Must be weak enough not to fight evaluation



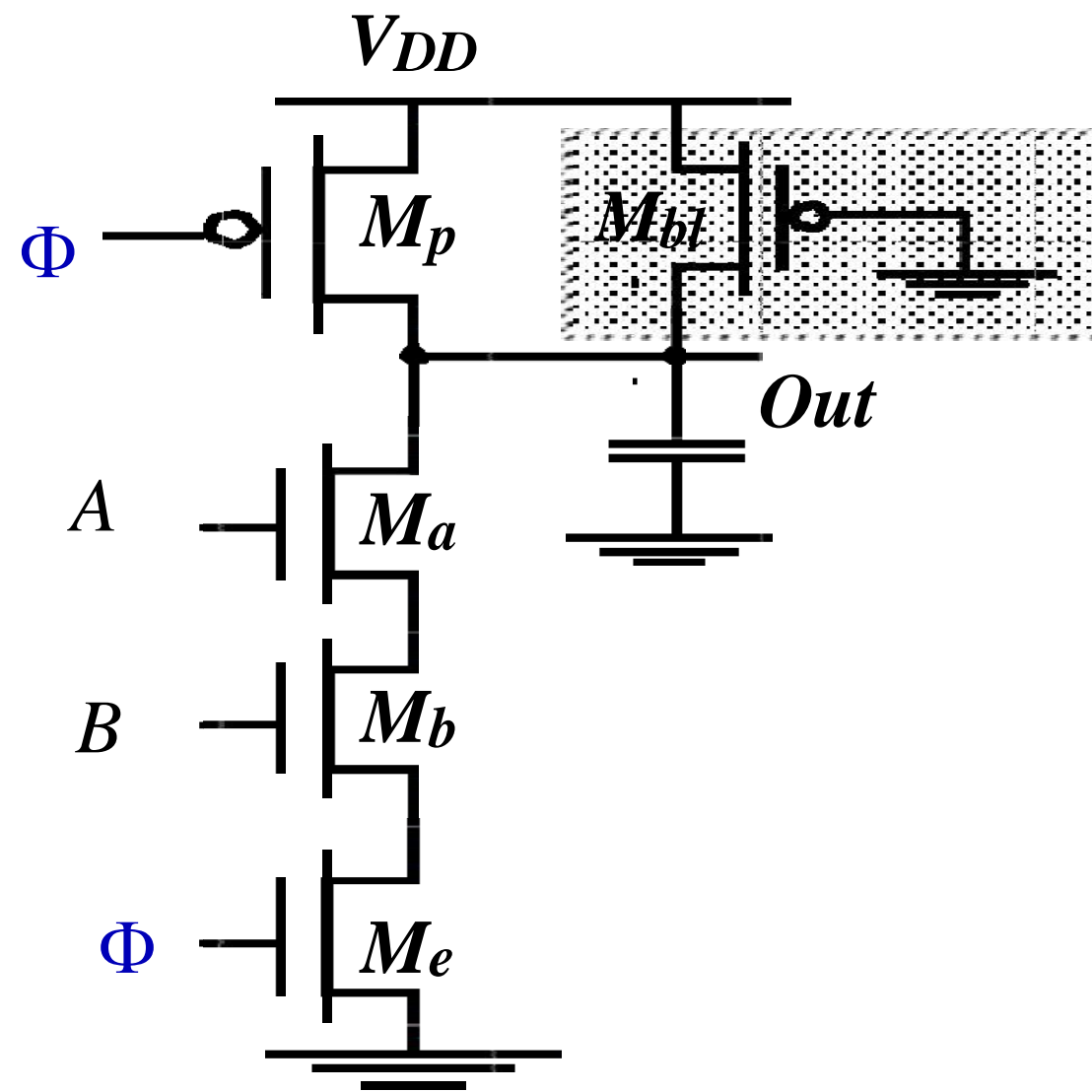

(a) Static bleeder

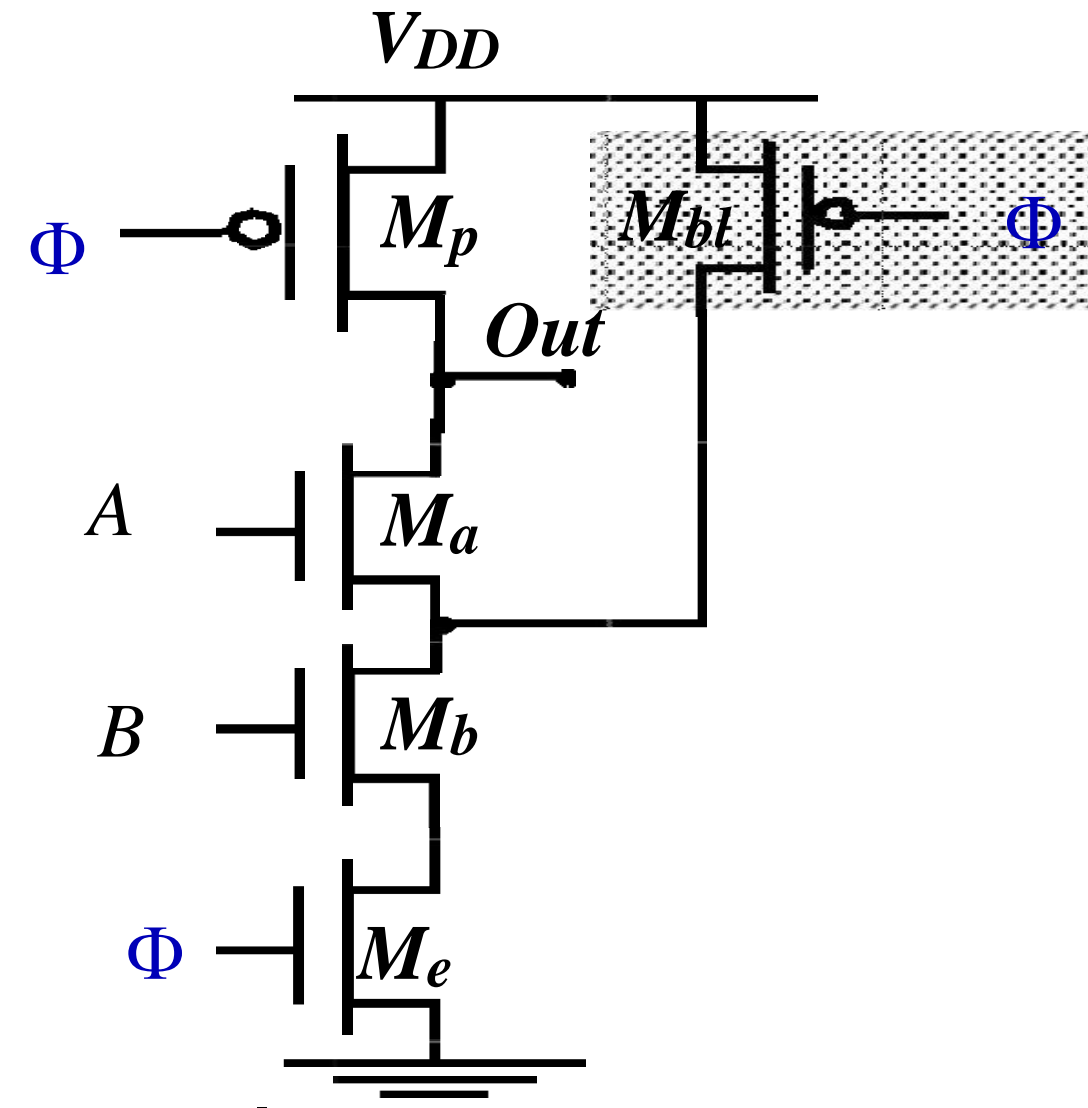

(b) Precharge of internal nodes



# ASSESSMENT



- Compare Static & Dynamic logic
- List out dynamic logic problems
- How monotonicity problem is solved?

20



# SUMMARY & THANK YOU