



SNS COLLEGE OF ENGINEERING

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF CSE (IoT)

23ITT201 – DIGITAL PRINCIPLES AND COMPUTER ORGANIZATION

II YEAR/ III SEMESTER

UNIT 1 – COMBINATIONAL LOGIC

TOPIC – BINARY ADDER



BINARY ADDER





Alternate name



ADDITION

3	1	4	8
+ 8	+ 3	+ 4	+ 6
<hr/>			
6	8	8	5
+ 6	+ 3	+ 2	+ 6
<hr/>			
7	3	7	2
+ 8	+ 0	+ 6	+ 3
<hr/>			
9	6	3	4
+ 3	+ 5	+ 3	+ 5
<hr/>			



PARALLEL ADDER



Alternate name




RIPPLE ADDER



For reference

Half adder:

 - A combinational logic circuit which is designed to add two binary digits is called as a **half adder**. The half adder provides the output along with a carry value (if any)







Half adder- Truth Table

Inputs		Outputs	
A	B	S (Sum)	C (Carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1




K- map for Half adder

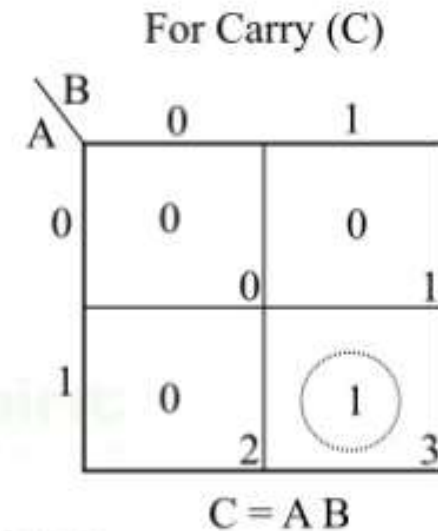 

Applications of Half adder

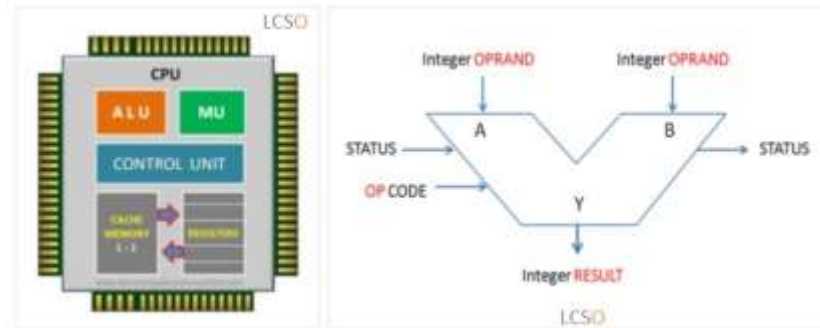- Half adder is used in **ALU (Arithmetic Logic Unit)** of computer processors to add binary bits.



- Half adder is used **to realize full adder circuit.**
- Half adder is used in **calculators.**
- Half adder is used to **calculate addresses and tables.**



Activity Time!!!

Lets have fun with
COLOURS 😊




RED	PINK	YELLOW	GREEN
ORANGE	BROWN	VOILET	WHITE
GRAY	BLUE	BROWN	RED
YELLOW	ORANGE	WHITE	BLUE
PINK	GRAY	RED	GREEN



For reference

Full adder:

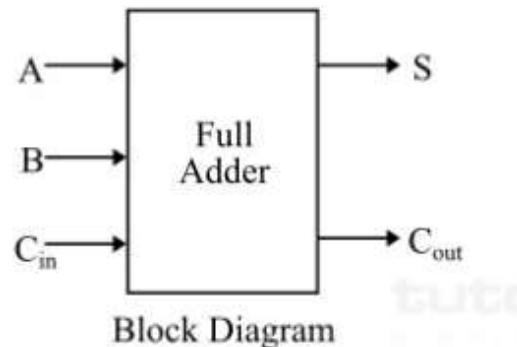- A combinational circuit which is designed **to add three binary digits** and produces two outputs (sum and carry) is known as a full adder.
- Thus, a full adder circuit adds three binary digits, where two are the inputs and one is the carry forwarded from the previous addition.






Full adder- Truth Table

Inputs			Outputs	
A	B	C _{in}	S (Sum)	C _{out} (Carry)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Hence, from the truth table, it is clear that the sum output of the full adder is equal to 1 when only 1 input is equal to 1 or when all the inputs are equal to 1.
- While the carry output has a carry of 1 if two or three inputs are equal to 1.



K- map for Full adder

 



Advantages of full adder

- Full adder provides facility to add the carry from the previous stage.
- The power consumed by the full adder is relatively less as compared to half adder.
- Full adder can be easily converted into a half subtractor just by adding a NOT gate in the circuit.
- Full adder produces higher output than half adder.
- Full adder is one of the essential parts of critical digital circuits like multiplexers.
- Full adder performs operations at higher speed.




Applications of full adder

- Full adders are used in ALUs (arithmetic logic units) of CPUs of computers.
- Full adders are used in calculators.
- Full adders also help in carrying out multiplication of binary numbers.
- Full adders are also used to realize critical digital circuits like multiplexers.
- Full adders are used to generate memory addresses.
- Full adders are also used in generation of program counterpoints.
- Full adders are also used in GPU (Graphical Processing Unit).

BINARY ADDER

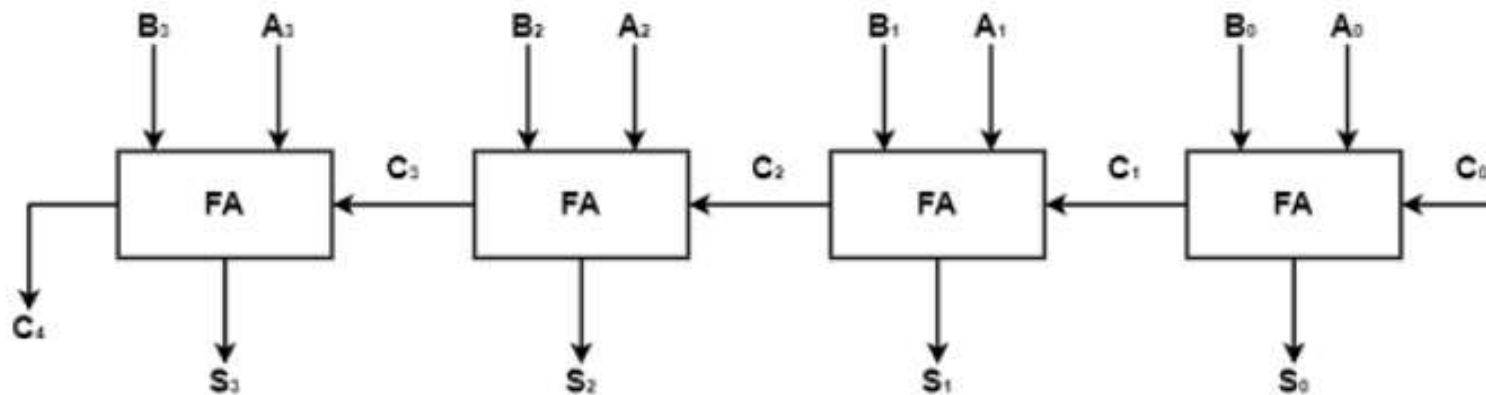- A Binary Adder is a digital circuit that implements the **arithmetic sum of two binary numbers** supported **with any length** is known as a binary adder.
- It is generated using **full-adder circuits connected in sequence**. The output carries from one full-adder linked to the input carry of the next full-adder.



4-Bit Binary Adder



BINARY ADDER

- The **augend bits of A** and the **addend bits of B** is created by subscript numbers from right to left, with subscript 0 indicating the low-order bit. The carries are linked in a chain by the **full-adders**.
- The input carry to the binary adder is C_0 and the output carry is C_4 . The S outputs of the full-adders create the needed sum bits.
- An **n-bit binary adder** is needed **n full-adders**.
- The output carries from each full-adder is linked to the input carry of the next-high-order full-adder.
- The n data bits for the A inputs come from one register including R1, and the n data bits for the B inputs come from another register including R2. The sum can be transferred to a third register or one of the source registers (R 1 or R2), restoring its earlier content.



SUMMARY



Thank You!