



SNS COLLEGE OF ENGINEERING

Coimbatore-35
An Autonomous Institution



Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

- DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

- 19EC505 –VLSI DESIGN

- III YEAR/ V SEMESTER

1

UNIT 3 –SEQUENTIAL LOGIC CIRCUITS

TOPIC 3 –TIMING ISSUES




OUTLINE




- **SYNCHRONOUS TIMING**
- **LATCH PARAMETERS**
- **REGISTER PARAMETERS**
- **CLOCK UNCERTAINTIES**
- **CLOCK NONIDEALITIES**
- **CLOCK SKEW AND JITTER**
- **POSITIVE AND NEGATIVE SKEW**
- **TIMING CONSTRAINTS**
- **ACTIVITY**
- **IMPACT OF JITTER**
- **SHORTEST PATH**
- **HOW TO COUNTER CLOCK SKEW?**
- **LATCH TIMING**
- **ASSESSMENT**
- **SUMMARY & THANKYOU**



SYNCHRONOUS TIMING

 


LATCH PARAMETERS

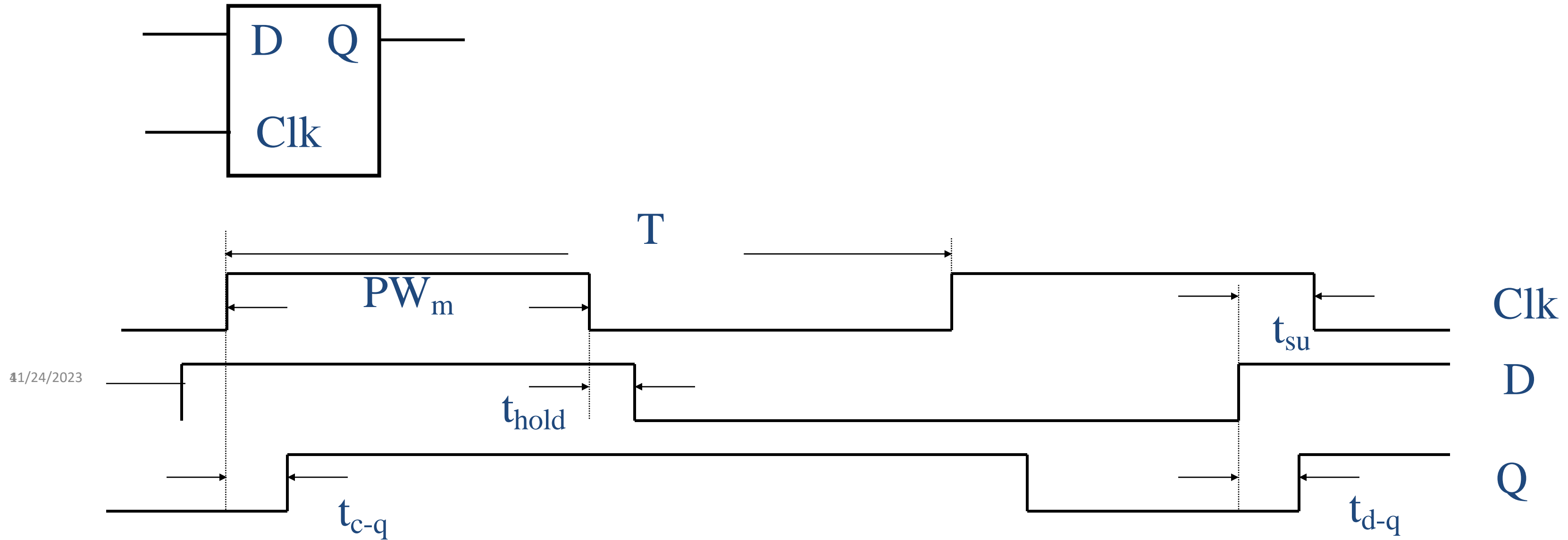

Delays can be different for rising and falling data transitions




REGISTER PARAMETERS

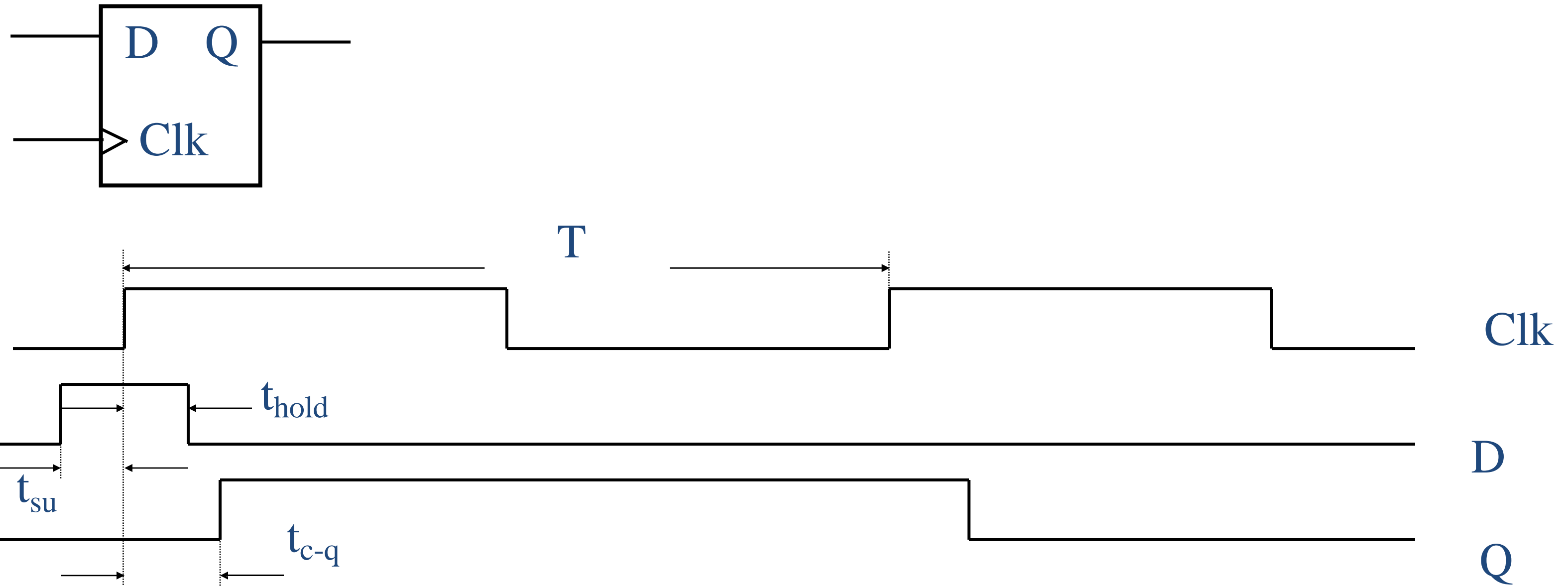

Delays can be different for rising and falling data transitions



CLOCK UNCERTAINTIES

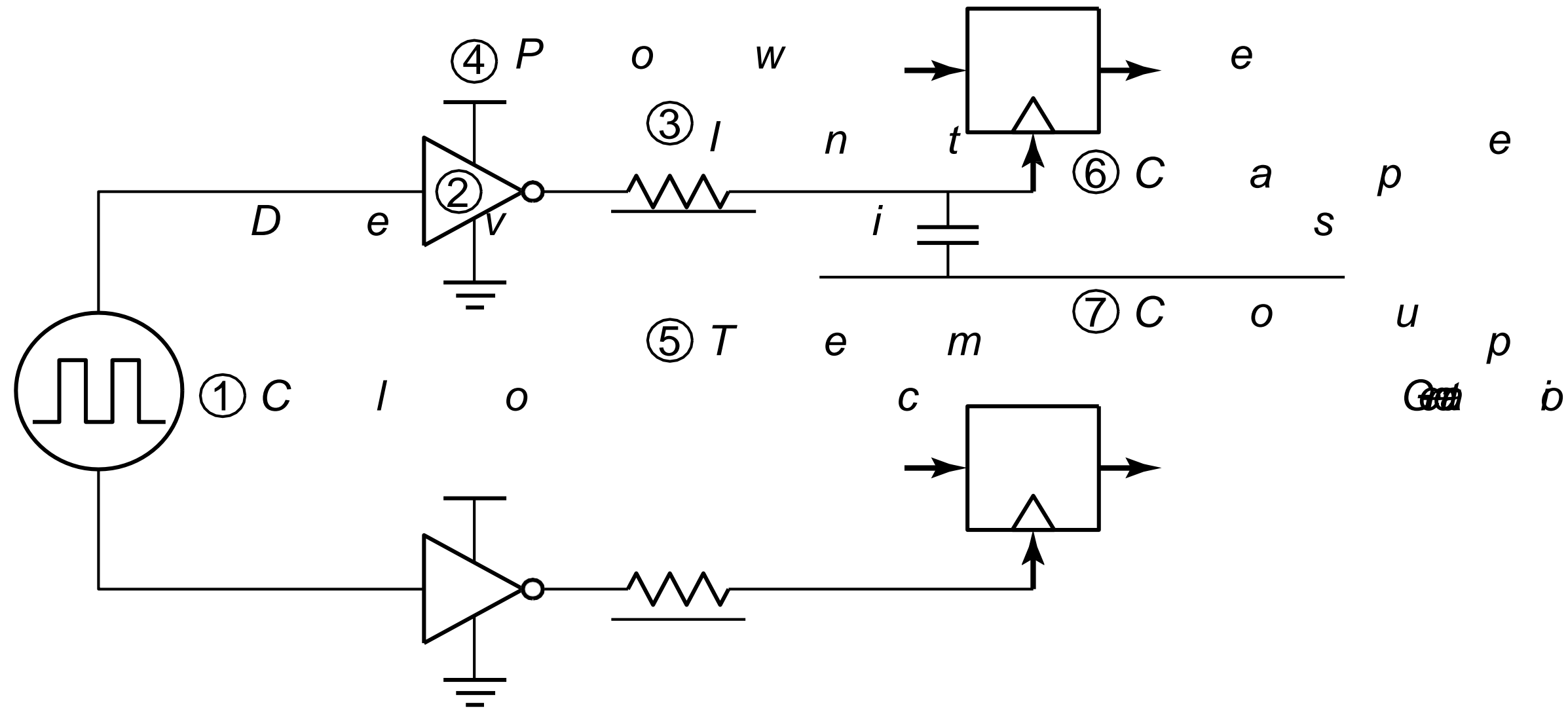




CLOCK NONIDEALITIES



- **Clock skew**
 - Spatial variation in temporally equivalent clock edges; deterministic + random, t_{SK}
- **Clock jitter**
 - Temporal variations in consecutive edges of the clock signal; modulation + random noise
 - Cycle-to-cycle (short-term) t_{JS}
 - Long term t_{JL}
- **Variation of the pulse width**
 - Important for level sensitive clocking




CLOCK SKEW AND JITTER

 



- Both skew and jitter affect the effective cycle time
- Only skew affects the race margin



CLOCK SKEW

 


POSITIVE AND NEGATIVE SKEW

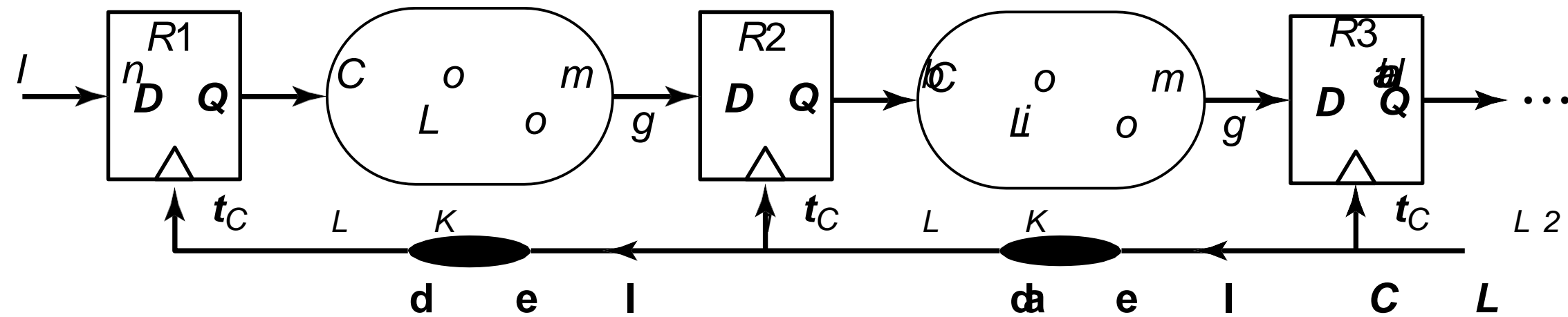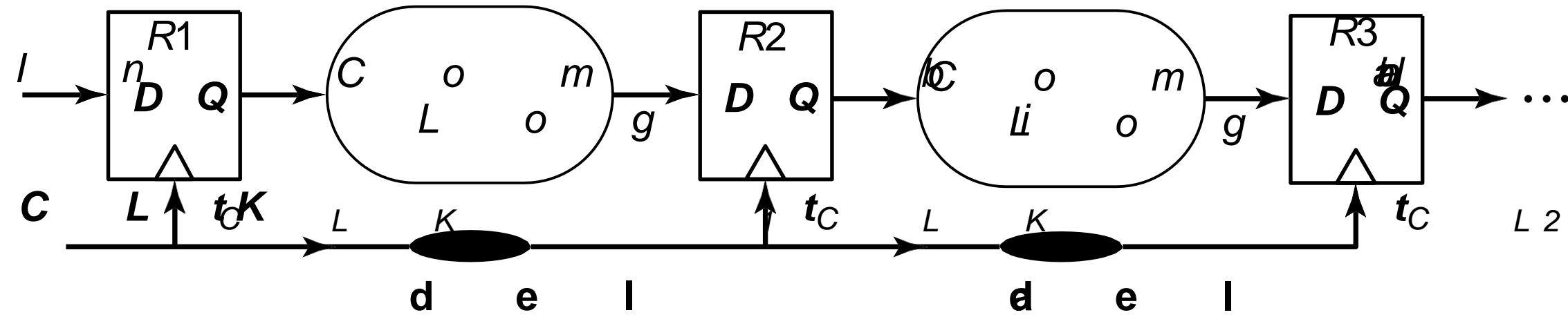



TIMING CONSTRAINTS

 

Minimum cycle time:

$$T - \delta = t_{c-q} + t_{su} + t_{logic}$$

Worst case is when receiving edge arrives early (positive δ)




CLASS ROOM ACTIVITY

STUDY THE PYRAMID CAREFULLY.

			E			
		1110		D		
	446		679		681	
198		263		431		265

WHAT ARE THE VALUES OF E AND D?


IMPACT OF JITTER

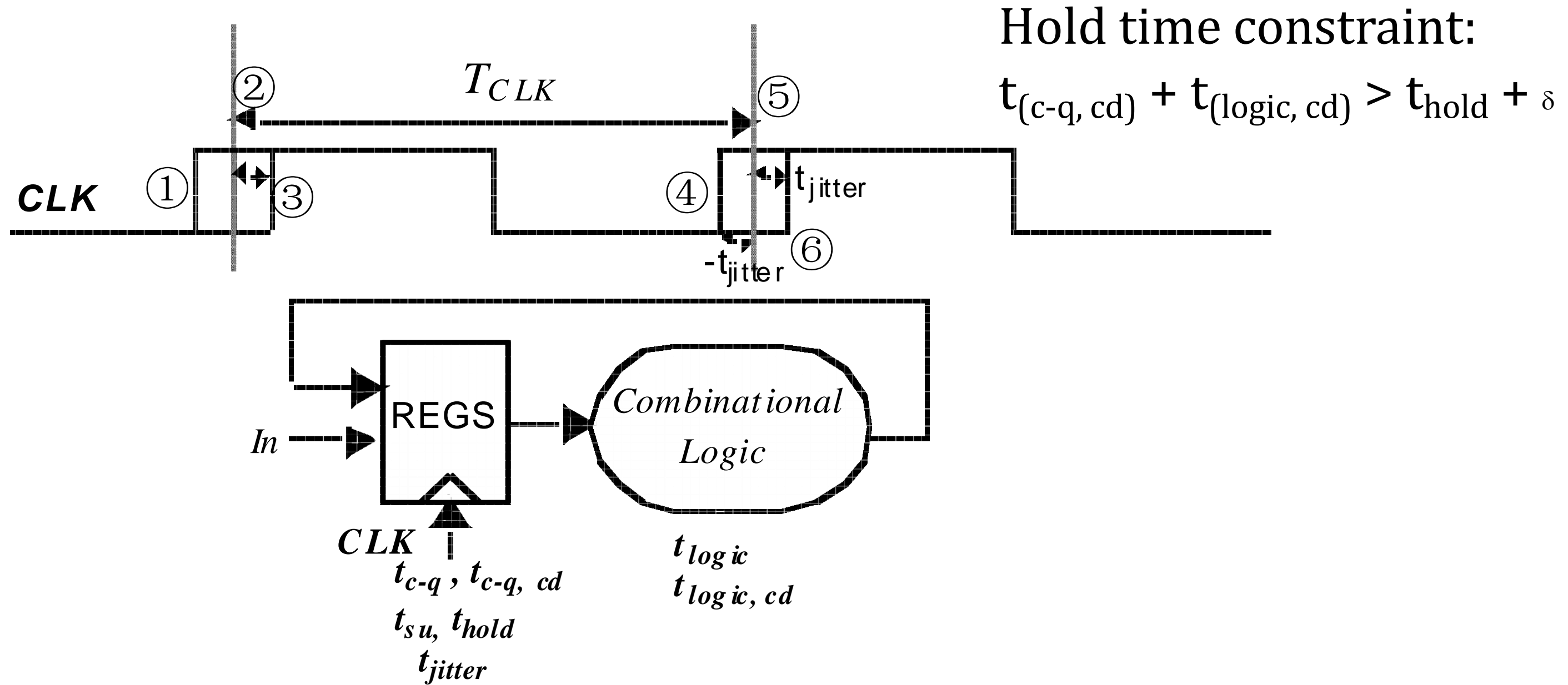




SHORTEST PATH

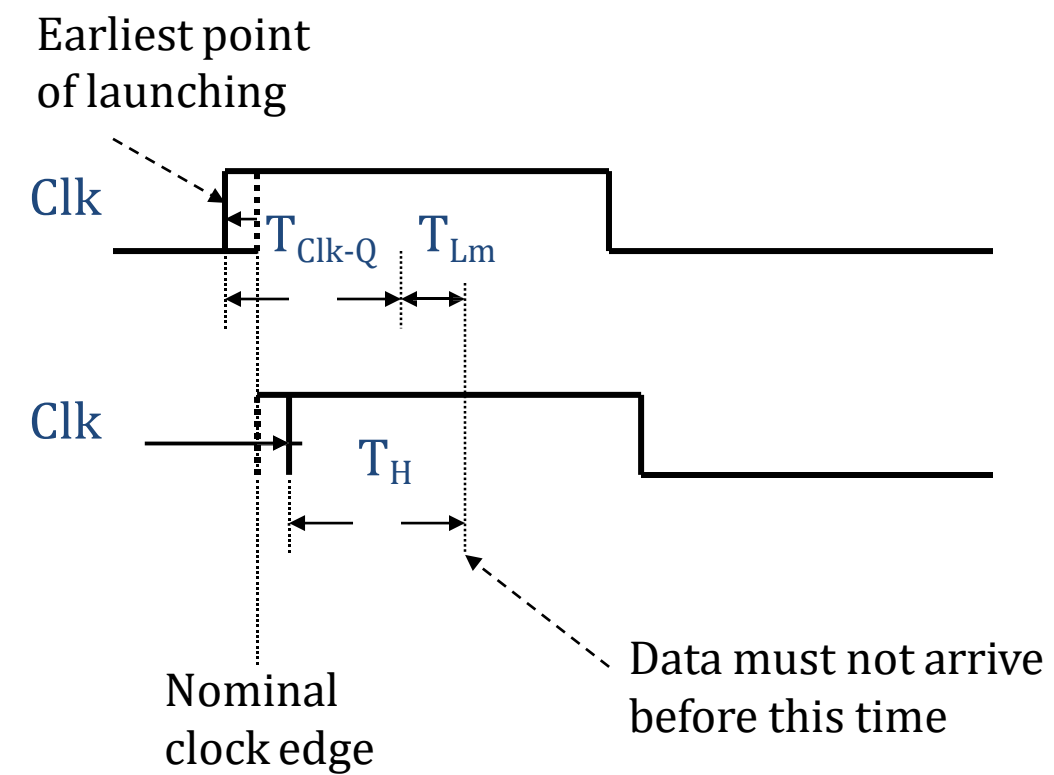Worst case is when receiving edge arrives late
Race between data and clock





HOW TO COUNTER CLOCK SKEW?

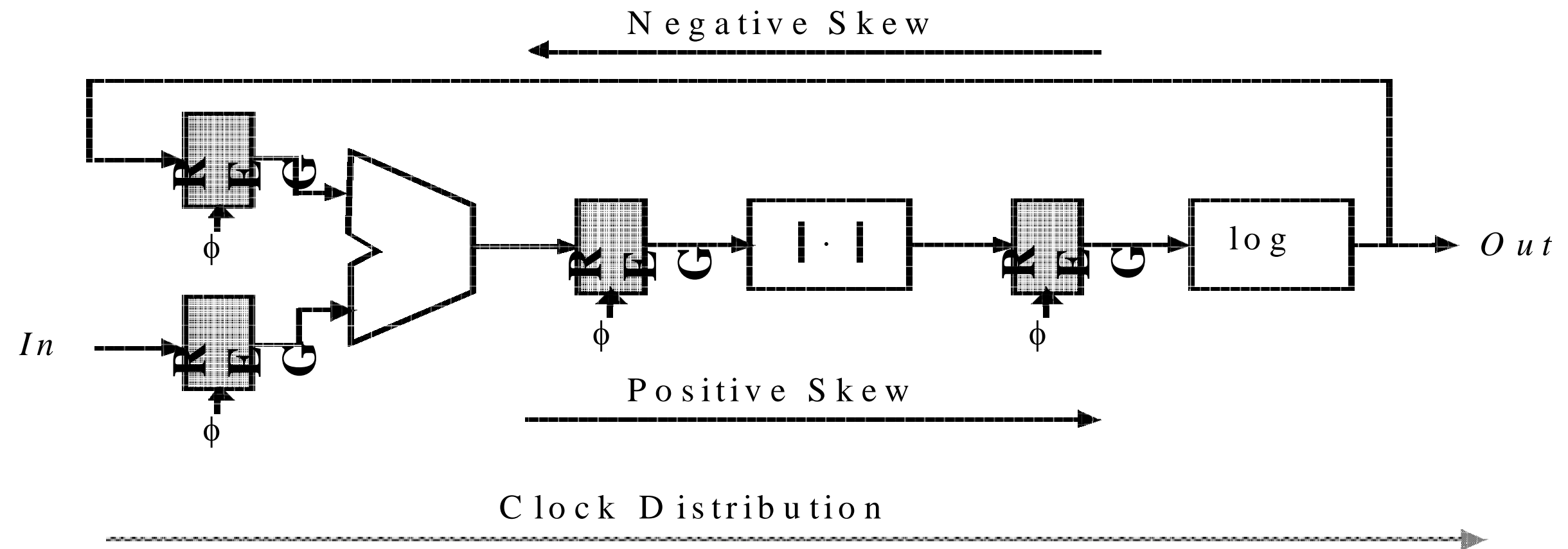


Data and Clock Routing



LATCH TIMING



 - When data arrives
- to closed latch
- Data has to be 're-launched'



• Latch is a 'soft' barrier

- When data arrives to transparent latch



ASSESSMENT

1. Compare latch & Register parameters
2. Define Clock Skew & Jitter
3. Differentiate positive skew & negative skew
4. How to counter clock skew?

SUMMARY & THANK YOU