



# **SNS COLLEGE OF ENGINEERING**



**Kurumbapalayam(Po), Coimbatore – 641 107**

**Accredited by NAAC-UGC with 'A' Grade**

**Approved by AICTE, Recognized by UGC & Affiliated to Anna University, Chennai**

## **Department of AI &DS**


**Course Name – 23ADT201 ARTIFICIAL  
INTELLIGENCE**

**II Year / III Semester**

**UNIT 4**


**LOGICAL REASONING**

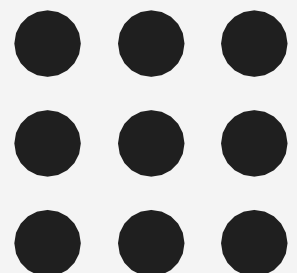**Topic: Knowledge Engineering Overview**





## Knowledge Engineering Overview

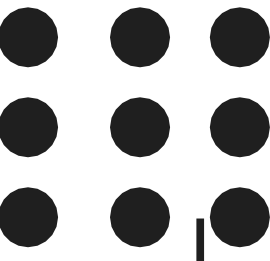

### CASE STUDY:

- **IBM Watson for Oncology:** IBM Watson uses Knowledge Engineering to analyze patient data and medical literature, providing oncologists with evidence-based treatment options for cancer patients. It leverages vast medical knowledge and learning algorithms to assist in making accurate diagnoses and recommending personalized treatment plans.



### Knowledge Engineering in FOL

- Knowledge Engineer is someone who
- **investigates** a particular domain,
- **learns** what concepts are important in that domain, and
- **creates a formal representation** of the objects and **relations** in the domain.





### Knowledge\_Engineering in FOL...

- **General purpose knowledge base**
  - Support queries about full range of human knowledge.
  - In this we can expect any kind of query, which knowledge base will have to infer.
- **Special purpose knowledge base**
  - Which has restricted domain (problem specific), here expected queries are known in advance.




## Steps in Knowledge Engineering Process

1. Identify the task
2. Assemble the relevant knowledge
3. Decide on a vocabulary of predicates, functions, and constants
4. Encode general knowledge about the domain
5. Encode a description of the specific problem instance
6. Pose queries to the inference procedure and get answers
7. Debug the knowledge base




## KE in FOL for Electronic Circuits Domain

- One-bit full adder

 

 
## 1. Identify the task.

- Identify the task similar to PEAS design.
- Knowledge engineer must describe the range of question that the KB will support
- Find the facts that available for each specific problem instance
  - Does the circuit actually add properly? (circuit verification)


 
## 2. Assemble the relevant knowledge


- Composed of wires and gates;
- Types of gates (AND, OR, XOR, NOT)
- Irrelevant: size, shape, color, cost of gates




 
## 3. Decide on a Vocabulary

- Translate the important domain level concepts into **logic level names**.
- Once the choice among predicates, functions and constants have been made, the result is **vocabulary, which is Ontology of domain**.



Type( $X_1$ ) = XOR  
 Type( $X_1$ , XOR)  
 XOR( $X_1$ )

Type( $X_2$ ) = XOR  
 Type( $X_2$ , XOR)  
 XOR( $X_2$ )


Type( $A_1$ ) = AND  
 Type( $A_1$ , AND)  
 AND( $A_1$ )

Type( $A_2$ ) = AND  
 Type( $A_2$ , AND)  
 AND( $A_2$ )

Type( $O_1$ ) = OR  
 Type( $O_1$ , OR)  
 OR( $O_1$ )
 
## 4. Encode General Knowledge Of The Domain

- $\forall t_1, t_2 \text{ Connected}(t_1, t_2) \Rightarrow \text{Signal}(t_1) = \text{Signal}(t_2)$  (t=terminal, g=gate)
- $\forall t \text{ Signal}(t) = 1 \vee \text{Signal}(t) = 0, 1 \neq 0$
- $\forall t_1, t_2 \text{ Connected}(t_1, t_2) \Rightarrow \text{Connected}(t_2, t_1)$
- $\forall g \text{ Type}(g) = \text{OR} \Rightarrow \text{Signal}(\text{Out}(1, g)) = 1 \Leftrightarrow \exists n \text{ Signal}(\text{In}(n, g)) = 1$
- $\forall g \text{ Type}(g) = \text{AND} \Rightarrow \text{Signal}(\text{Out}(1, g)) = 0 \Leftrightarrow \exists n \text{ Signal}(\text{In}(n, g)) = 0$
- $\forall g \text{ Type}(g) = \text{XOR} \Rightarrow \text{Signal}(\text{Out}(1, g)) = 1 \Leftrightarrow \text{Signal}(\text{In}(1, g)) \neq \text{Signal}(\text{In}(2, g))$
- $\forall g \text{ Type}(g) = \text{NOT} \Rightarrow \text{Signal}(\text{Out}(1, g)) \neq \text{Signal}(\text{In}(1, g))$





## 5. Encode The Specific Problem Instance

Type( $X_1$ ) = XOR

Type( $A_1$ ) = AND

Type( $O_1$ ) = OR

Type( $X_2$ ) = XOR

Type( $A_2$ ) = AND

Type( $C_1$ ) = Circuit

**Connected(Out(1, $X_1$ ),In(1, $X_2$ ))**

**Connected(Out(1, $X_1$ ),In(2, $A_2$ ))**

**Connected(Out(1, $A_2$ ),In(1, $O_1$ ))**

**Connected(Out(1, $A_1$ ),In(2, $O_1$ ))**

**Connected(Out(1, $X_2$ ),Out(1, $C_1$ ))**

**Connected(Out(1, $O_1$ ),Out(2, $C_1$ ))**

**Connected(In(1, $C_1$ ),In(1, $X_1$ ))**


**Connected(In(1, $C_1$ ),In(1, $A_1$ ))**

**Connected(In(2, $C_1$ ),In(2, $X_1$ ))**

**Connected(In(2, $C_1$ ),In(2, $A_1$ ))**

**Connected(In(3, $C_1$ ),In(2, $X_2$ ))**

 **Connected(In(3, $C_1$ ),In(1, $A_2$ ))**





## 6. Pose Queries To The Inference Procedure

- What are the possible sets of values of all the terminals for the adder circuit? ✓ values

$$\begin{aligned} \exists i_1, i_2, i_3, o_1, o_2 \text{ Signal(In}(1, C_1)) = i_1 \wedge \text{Signal(In}(2, C_1)) = i_2 \wedge \\ \text{Signal(In}(3, C_1)) = i_3 \wedge \text{Signal(Out}(1, C_1)) = o_1 \wedge \\ \text{Signal(Out}(2, C_1)) = o_2 \end{aligned}$$

- There are substitution of variables  $i_1, i_2, i_3$  with values (1/0).
- The final query will return complete with given Input and Output for the device.
- It should be used to check that add inputs correctly
- This is called as **circuit verification**.






# 7. Debug the knowledge base

- We have to see the knowledge base in different ways
  - System unable to give output in no signals
  - If all inputs are 000, then the output also 00,
  - And etc.
- May have omitted the assertions like  $1 \neq 0$



# Knowledge Engineering Overview

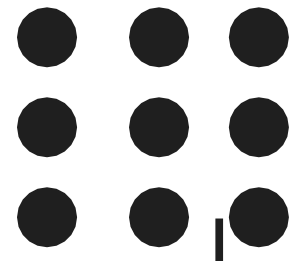

**THANK YOU**