



SNS COLLEGE OF ENGINEERING


(Autonomous)

DEPARTMENT OF INFORMATION TECHNOLOGY



23ITT201 – DIGITAL PRINCIPLES AND COMPUTER ORGANIZATION

UNIT -1 COMBINATIONAL LOGIC

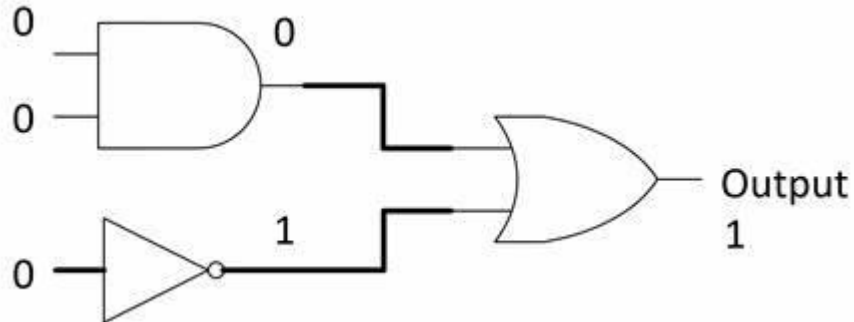




Introduction to Combinational Circuits



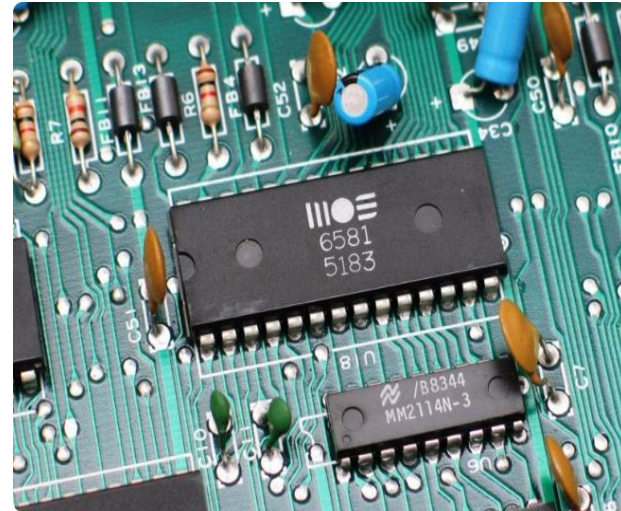- Combinational circuits are digital circuits where the output is determined solely by the current input.
- They are the building blocks of more complex digital systems, enabling efficient logic operations and decision-making capabilities.




Boolean Algebra and Logic Gates

1

AND Gate

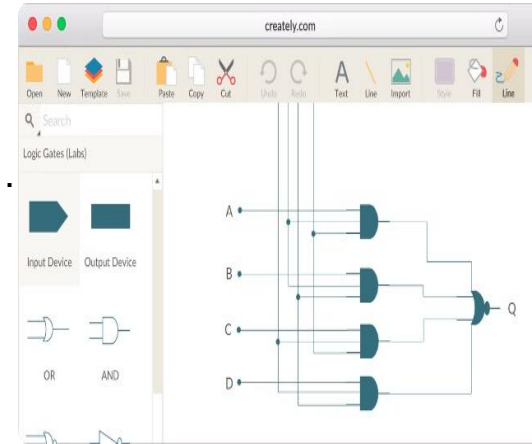Produces a 1 output only when all inputs are 1.



2

OR Gate

Produces a 1 output when any one or more inputs are 1.

3

NOT Gate

Inverts the input, producing a 1 output when the input is 0, and vice versa.





Truth Tables

Systematically mapping all possible input combinations to their corresponding outputs.

Boolean Expressions

Algebraic representations of the logic function, using AND, OR, and NOT operations.

Karnaugh Maps

Graphical method for simplifying Boolean expressions and minimizing logic circuits.





1

Input Identification

Determine the inputs that affect the output of a combinational circuit.

2

Truth Table Generation

Construct a truth table to represent the logic function of the circuit.

3

Output Determination

Analyze the truth table to identify the output for each input combination.





Combinational Circuit Optimization



Simplify Boolean Expressions

Use Boolean algebra and Karnaugh maps to minimize the number of logic gates required.

Reduce Propagation Delay

Arrange logic gates in a way that minimizes the time it takes for signals to propagate through the circuit.

Improve Power Efficiency

Design circuits that consume less power by reducing the number of active components.





Multiplexers and Demultiplexers



Multiplexer

Routes one of many input signals to a single output based on a select signal.



Demultiplexer

Connects a single input to one of many outputs based on a select signal.





Encoders and Decoders

1

Encoder

Converts a set of parallel inputs into a coded output, such as binary.

2

Binary to Seven-Segment Decoder

Converts a binary input into the appropriate signals to drive a seven-segment display.

3

Decoder

Converts a coded input into a set of parallel outputs, activating the corresponding output.





Applications of Combinational Circuits

Arithmetic Circuits

Adders, Subtractors,
Multipliers

Comparators

Greater Than, Less Than,
Equal To

Parity Generators

Detect errors in data
transmission

Code Converters

Binary to BCD, Binary to
Gray Code





Thank
you

