



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107



AN AUTONOMOUS INSTITUTION

Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai

I Semester

B.E-Mechanical and Mechatronics Engineering (Additive Manufacturing)

23EET101 – Basics of Electrical and Electronics Engineering

Regulations 2023


QUESTION BANK

UNIT I

PART A

- 1 State Kirchoff's Voltage Law.
- 2 State the limitations of ohms law.
- 3 List the essential requirements (torque) of an instrument.
- 4 Define Ohm's Law.
- 5 State Kirchoff's Current Law.
- 6


Find the average value of

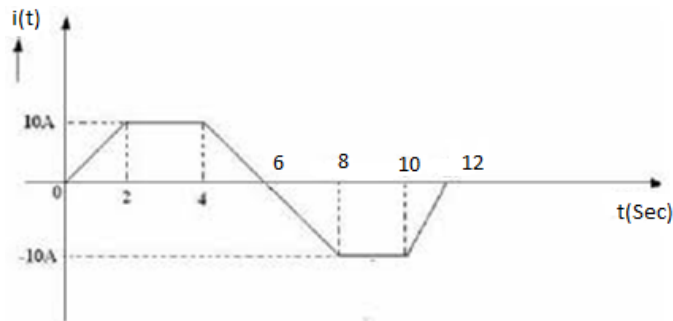


- 7 Distinguish between series and parallel circuit.
- 8 Compare Mesh and Loop.
- 9 Write current division rule.
- 10 State Kirchoff's Current Law.
- 11 Define average and RMS value.
- 12 Define form factor.
- 13 Limitations of MC instrument.

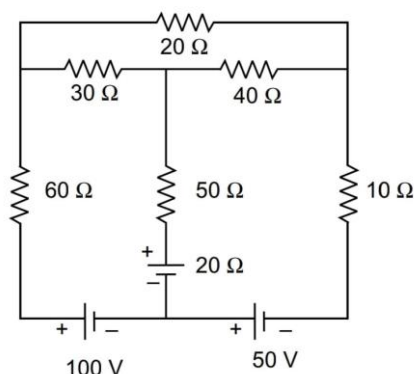PART B


- 1 Calculate the current in the $50\ \Omega$ resistor in the network shown in fig using mesh analysis. Also determine the voltage drop across the $20\ \Omega$ resistor.



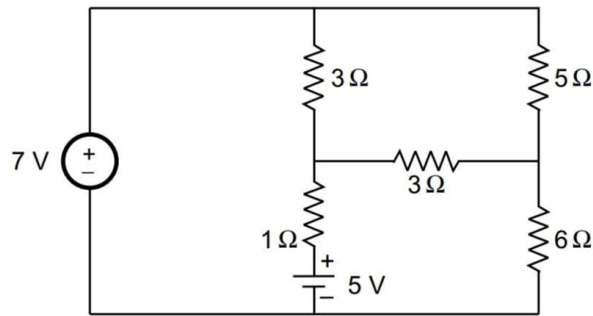
- 2 Illustrate the mesh currents and also the current through $1\ \Omega$ resistance in the circuit shown in fig.



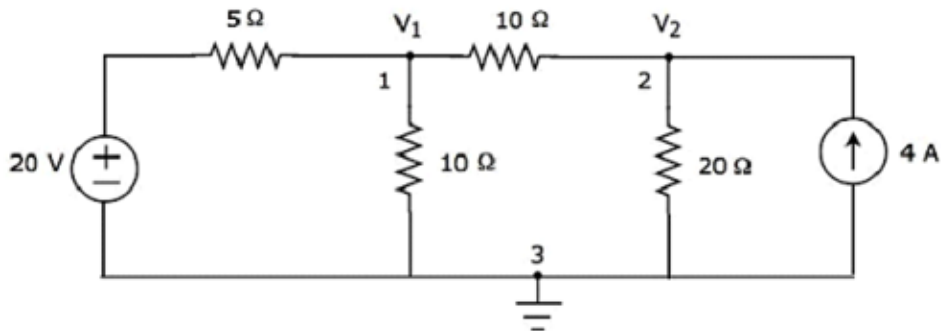- 3 Use Kirchoff's law to determine the node voltage V_1 and V_2 for shown in fig.



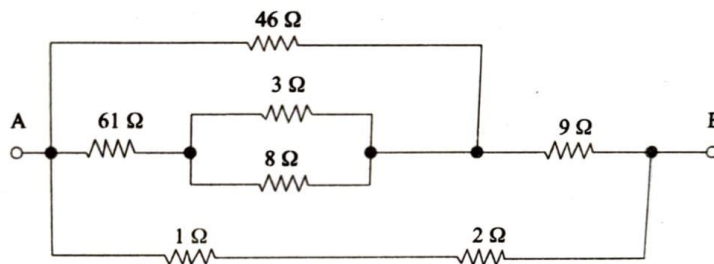- 4 With a neat schematic diagram explain the operation of single phase energy meter.
 5 Discuss the principle of operation of permanent magnet moving coil instruments with neat sketches.
 6 Determine the amount of total resistance between points A and B of the circuit shown in fig.



- 7 Discuss the principle of operation of dynamometer type wattmeter.
 8 With a suitable sketch explain the principle of operation of attraction type and repulsion type of moving iron instruments.
 9 Use circuit reduction technique, to determine the equivalent resistance between A and B for given circuit.

