



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

Accredited by NAAC-UGC with 'A' Grade

Approved by AICTE, Recognized by UGC & Affiliated to Anna University, Chennai

DEPARTMENT OF INFORMATION TECHNOLOGY


COURSE NAME: 23ITT201 DIGITAL PRINCIPLES AND

COMPUTER ORGANIZATION

II YEAR/ III SEM

Unit 4 : PROCESSOR

Hardwired control

 



Overview of Hardwired Control

- To execute instructions, the processor must have some means of generating the control signals needed in the proper sequence.
- Two categories for this purpose:
 1. Hardwired control
 2. Microprogrammed control
- Hardwired control is a method of **control unit design**
- The control-signals are generated by using logic circuits such as gates, flip-flops, decoders etc.



Overview of Hardwired Control


- Each step in the control sequence is completed in one clock period.
- Counter is used to keep track of control steps.
- Control signals are determined by

- Contents of the control step counter
- Contents of the IR
- Contents of the condition code flags
- External input signals like MFC and interrupt requests


Step	Action
1	PC_{out} , MAR_{in} , Read, Select4, Add, Z_{in}
2	Z_{out} , PC_{in} , Y_{in} WMF C
3	MDR_{out} , IR_{in}
4	$R3_{out}$, MAR_{in} , Read
5	$R1_{out}$, Y_{in} , WMFC
6	MDR_{out} , SelectY, Add, Z_{in}
7	Z_{out} , $R1_{in}$, End

Control Sequence

Control Unit Organization

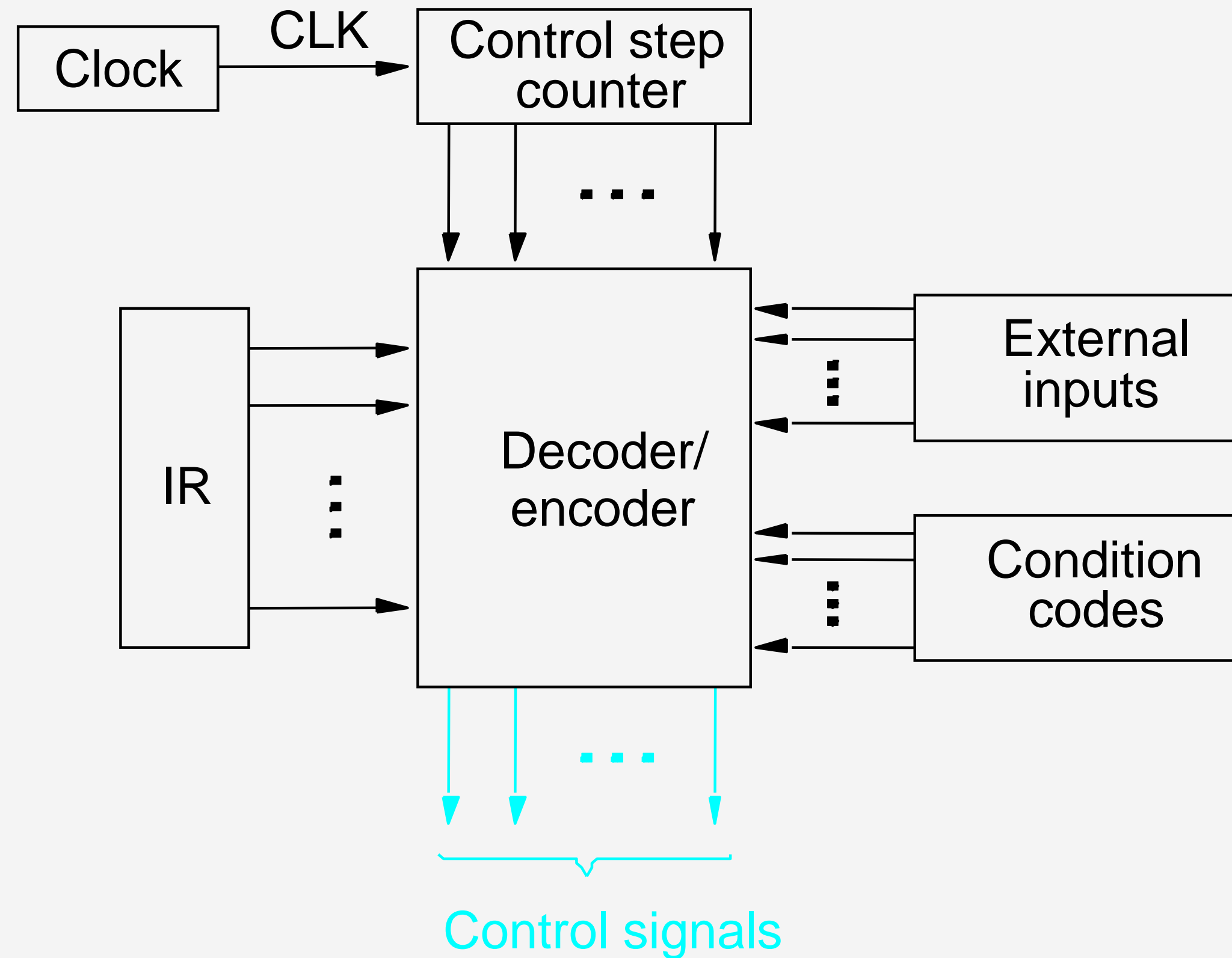


Detailed Block Description

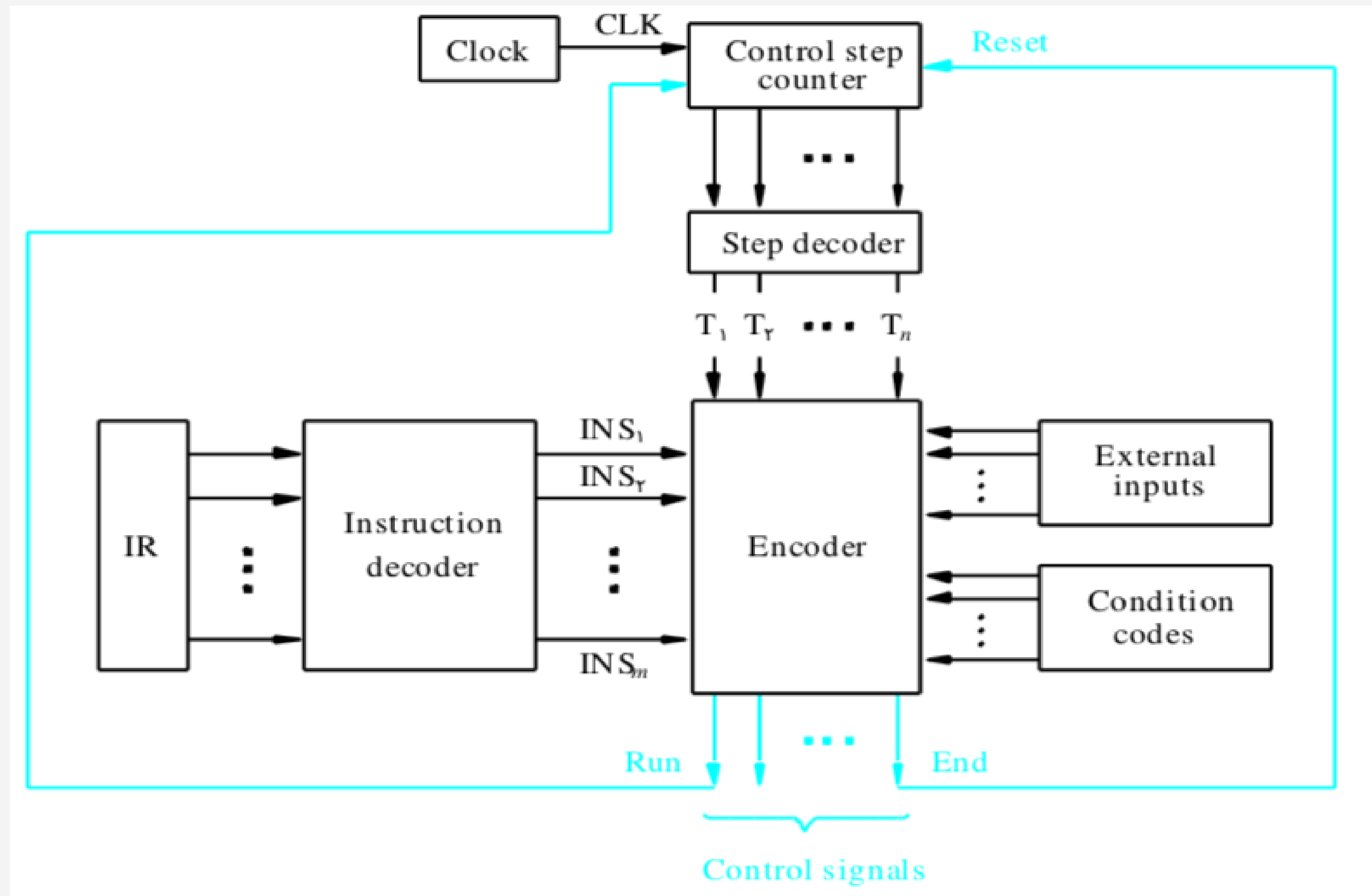


Generating Z_{in}
 
$$Z_{in} = T_1 + T_6 \cdot \text{ADD} + T_4 \cdot \text{BR} + \dots$$





Generating End
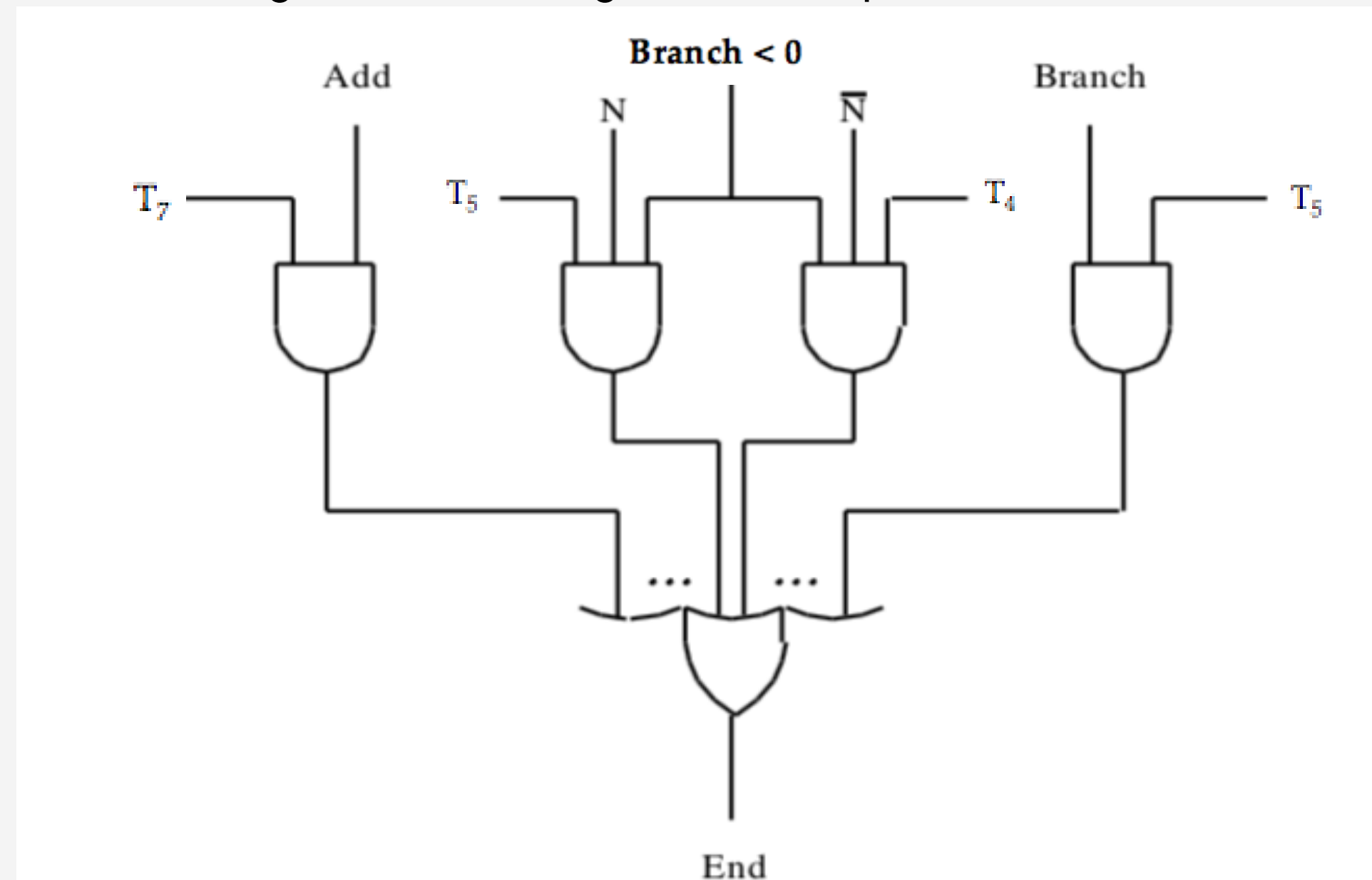
$$\text{End} = T_7 \cdot \text{ADD} + T_5 \cdot \text{BR} + (T_5 \cdot N + T_4 \cdot \bar{N}) \cdot \text{BRN} + \dots$$



- Sequence of operation is determined by wiring of the logic elements hence the name 'hardwired'
- Hardwired system can operate at high speed; but with little flexibility.

Complete Processor

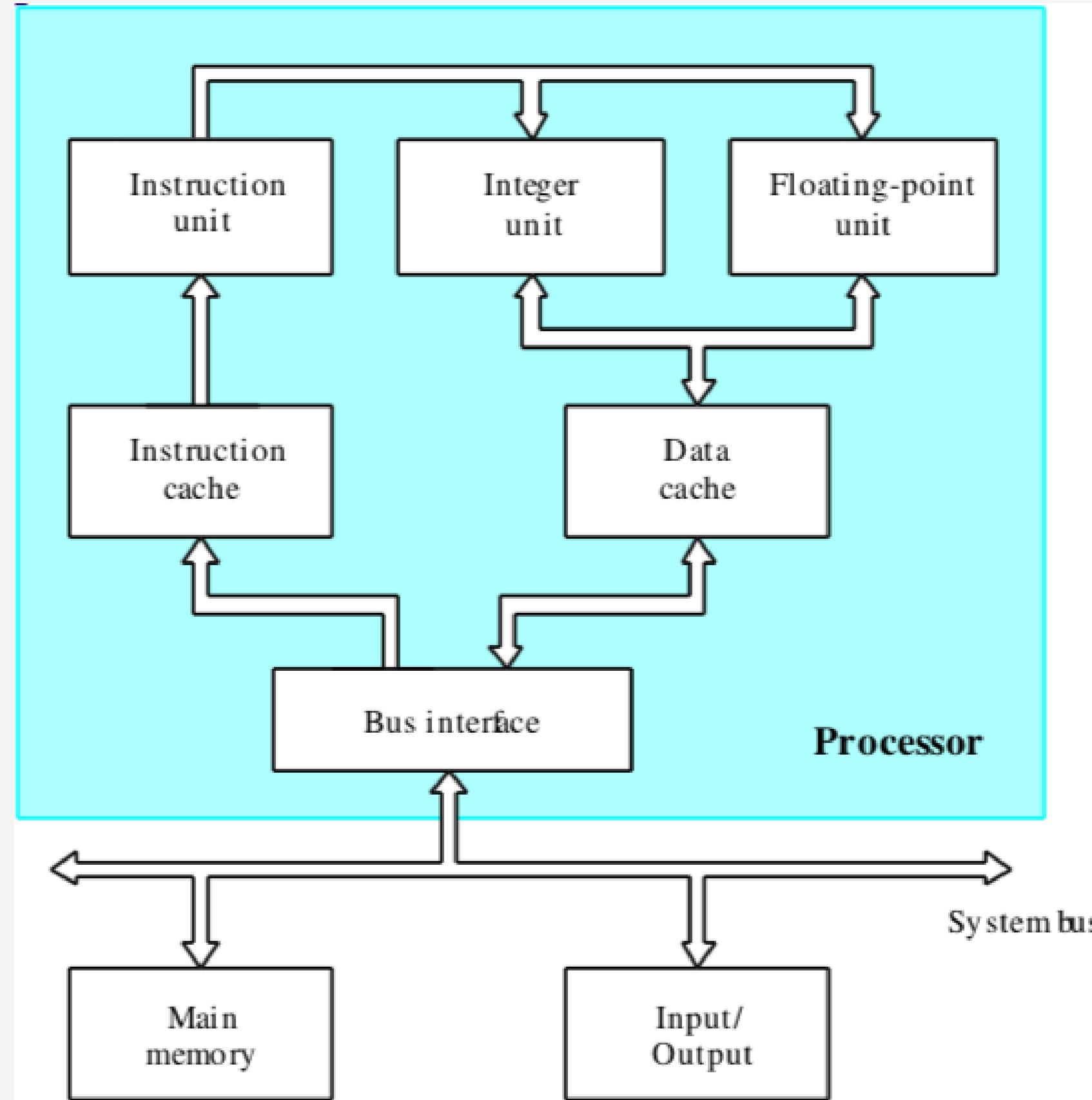 



Thank You