



### Transient response in RLC Circuit

#### Series RLC circuit

The circuit shown on Figure 1 is called the series RLC circuit. We will analyze this circuit in order to determine its transient characteristics once the switch  $S$  is closed.

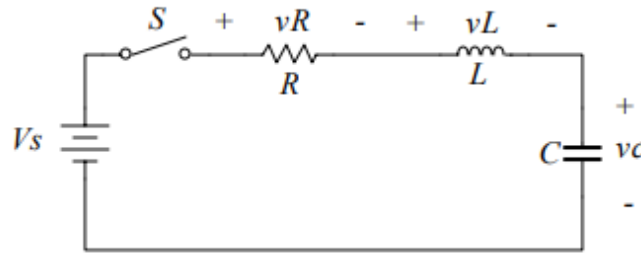


Figure 1

The equation that describes the response of the system is obtained by applying KVL around the mesh

$$vR + vL + vc = Vs \quad (1.1)$$

The current flowing in the circuit is

$$i = C \frac{dvc}{dt} \quad (1.2)$$

And thus the voltages  $vR$  and  $vL$  are given by

$$vR = iR = RC \frac{dvc}{dt} \quad (1.3)$$

$$vL = L \frac{di}{dt} = LC \frac{d^2vc}{dt^2} \quad (1.4)$$

Substituting Equations (1.3) and (1.4) into Equation (1.1) we obtain

$$\frac{d^2vc}{dt^2} + \frac{R}{L} \frac{dvc}{dt} + \frac{1}{LC} vc = \frac{1}{LC} Vs \quad (1.5)$$

The solution to equation (1.5) is the linear combination of the homogeneous and the particular solution  $vc = vc_p + vc_h$

The particular solution is



# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107



AN AUTONOMOUS INSTITUTION

$$vc_p = Vs \quad (1.6)$$

And the homogeneous solution satisfies the equation

$$\frac{d^2vc_h}{dt^2} + \frac{R}{L} \frac{dvc_h}{dt} + \frac{1}{LC}vc_h = 0 \quad (1.7)$$

Assuming a homogeneous solution is of the form  $Ae^{st}$  and by substituting into Equation (1.7) we obtain the characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (1.8)$$

By defining

$$\alpha = \frac{R}{2L}: \text{ Damping rate} \quad (1.9)$$

And

$$\omega_o = \frac{1}{\sqrt{LC}}: \text{ Natural frequency} \quad (1.10)$$

The characteristic equation becomes

$$s^2 + 2\alpha s + \omega_o^2 = 0 \quad (1.11)$$

The roots of the characteristic equation are

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} \quad (1.12)$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_o^2} \quad (1.13)$$

And the homogeneous solution becomes

$$vc_h = A_1e^{s_1t} + A_2e^{s_2t} \quad (1.14)$$

The total solution now becomes

$$vc = Vs + A_1e^{s_1t} + A_2e^{s_2t} \quad (1.15)$$



## AN AUTONOMOUS INSTITUTION

The parameters  $A_1$  and  $A_2$  are constants and can be determined by the application of the initial conditions of the system  $vc(t=0)$  and  $\frac{dvc(t=0)}{dt}$ .

The value of the term  $\sqrt{\alpha^2 - \omega_o^2}$  determines the behavior of the response. Three types of responses are possible:

1.  $\alpha = \omega_o$  then  $s_1$  and  $s_2$  are equal and real numbers: no oscillatory behavior  
**Critically Damped System**
2.  $\alpha > \omega_o$ . Here  $s_1$  and  $s_2$  are real numbers but are unequal: no oscillatory behavior  
**Over Damped System**  
 $vc = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$
3.  $\alpha < \omega_o$ .  $\sqrt{\alpha^2 - \omega_o^2} = j\sqrt{\omega_o^2 - \alpha^2}$  In this case the roots  $s_1$  and  $s_2$  are complex numbers:  $s_1 = -\alpha + j\sqrt{\omega_o^2 - \alpha^2}$ ,  $s_2 = -\alpha - j\sqrt{\omega_o^2 - \alpha^2}$ . System exhibits oscillatory behavior  
**Under Damped System**

Important observations for the series RLC circuit.

- As the resistance increases the value of  $\alpha$  increases and the system is driven towards an over damped response.
- The frequency  $\omega_o = \frac{1}{\sqrt{LC}}$  (rad/sec) is called the natural frequency of the system or the resonant frequency.
- The parameter  $\alpha = \frac{R}{2L}$  is called the damping rate and its value in relation to  $\omega_o$  determines the behavior of the response
  - $\alpha = \omega_o$  : Critically Damped
  - $\alpha > \omega_o$  : Over Damped
  - $\alpha < \omega_o$  : Under Damped
- The quantity  $\sqrt{\frac{L}{C}}$  has units of resistance