



# SNS COLLEGE OF TECHNOLOGY Coimbatore-35 **An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' (III Cycle) Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECT101 – CIRCUIT ANALYSIS** I YEAR/ II SEMESTER

#### **UNIT 1 – NODE ANALYSIS** **TOPIC - Nodal Analysis**



# Nodal Analysis



- There are two basic methods that are used for solving any electrical network: **Nodal analysis** and **Mesh analysis**.
- In Nodal analysis, we will consider the node voltages with respect to Ground. Hence, Nodal analysis is also called as **Node-voltage method**.




- Follow these steps while solving any electrical network or circuit using **Nodal analysis**.
  
- **Step 1** – Identify the **principal nodes** and choose one of them as **reference node**. We will treat that reference node as the Ground.
  
- **Step 2** – Label the **node voltages** with respect to Ground from all the principal nodes except the reference node.




- **Step 3** – Write **nodal equations** at all the principal nodes except the reference node. Nodal equation is obtained by applying KCL first and then Ohm's law.
- **Step 4** – Solve the nodal equations obtained in Step 3 in order to get the node voltages.
- Now, we can find the current flowing through any element and the voltage across any element that is present in the given network by using node voltages.



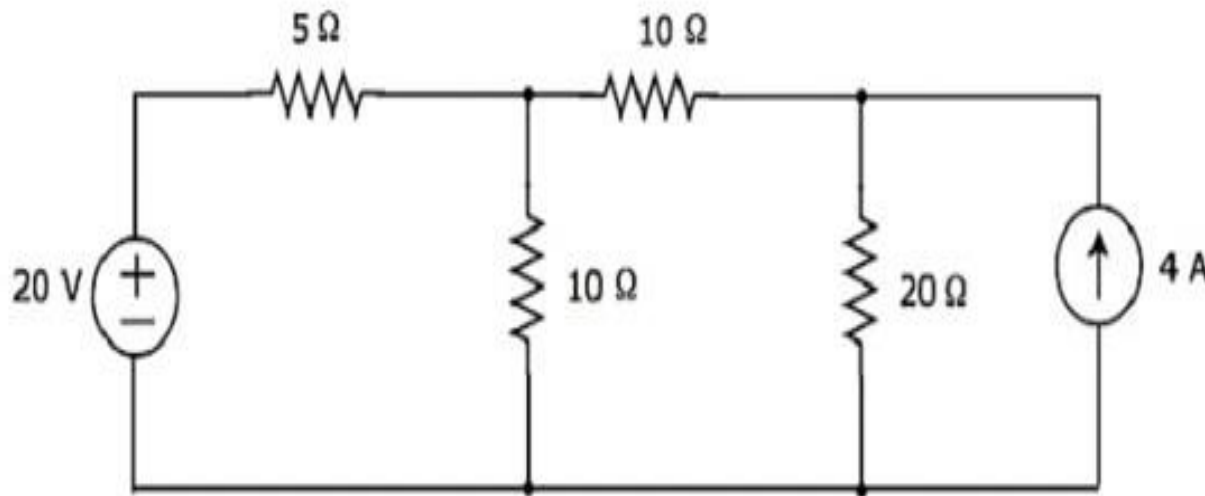- Find the current flowing through  $20\ \Omega$  resistor of the following circuit using **Nodal analysis**.




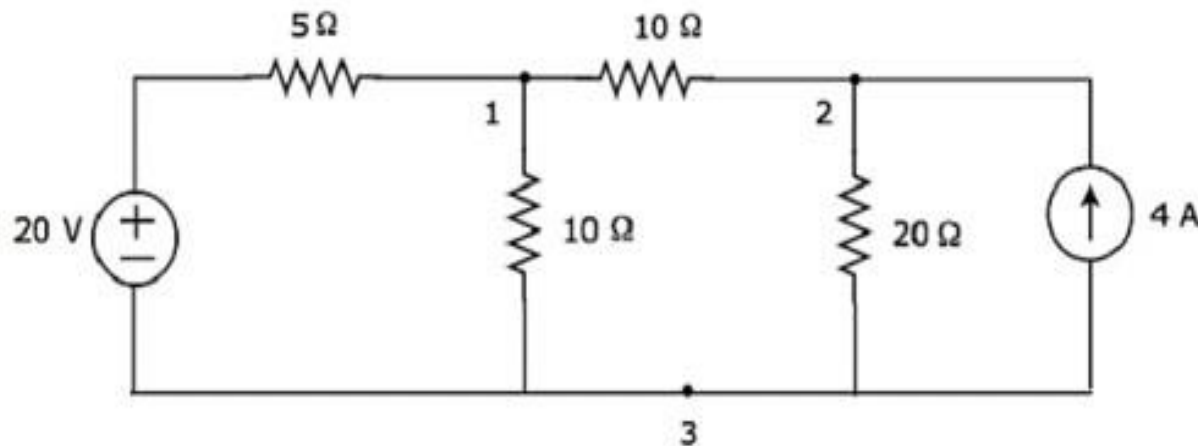- Step 1 – There are three principle nodes in the above circuit. Those are labelled as



In the above figure, consider **node 3** as reference node (Ground).

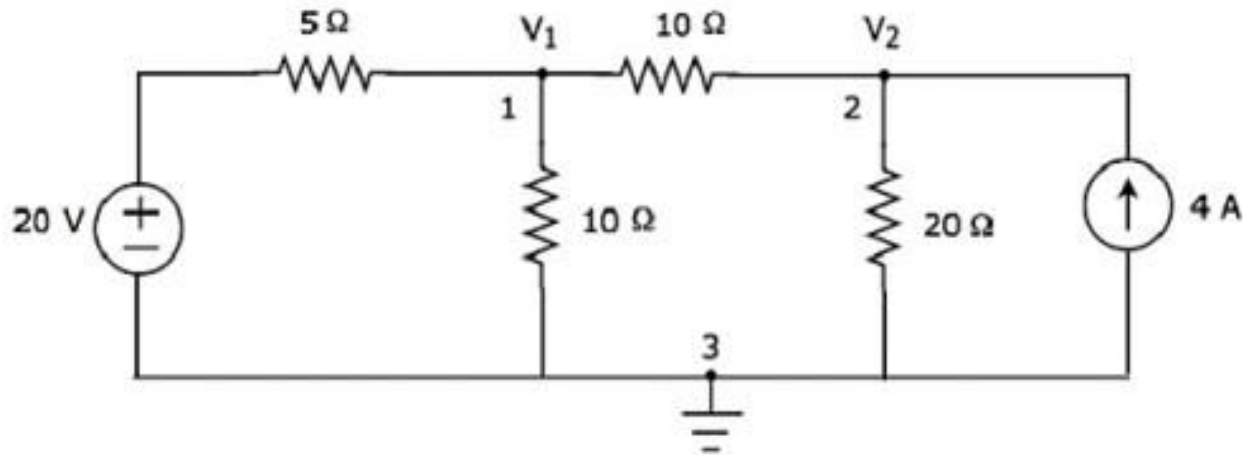Step 2 – The node voltages,  $V_1$  and  $V_2$ , are labelled in the following figure.



In the above figure,  $V_1$  is the voltage from node 1 with respect to ground and  $V_2$  is the voltage from node 2 with respect to ground.



## Step 3 : The nodal equation at node 1 is

The **nodal equation** at node 1 is

$$\frac{V_1 - 20}{5} + \frac{V_1}{10} + \frac{V_1 - V_2}{10} = 0$$

$$\Rightarrow \frac{2V_1 - 40 + V_1 + V_1 - V_2}{10} = 0$$

$$\Rightarrow 4V_1 - 40 - V_2 = 0$$

$$\Rightarrow V_2 = 4V_1 - 40$$

**Equation 1**





The **nodal equation** at node 2 is

$$-4 + \frac{V_2}{20} + \frac{V_2 - V_1}{10} = 0$$

$$\Rightarrow \frac{-80 + V_2 + 2V_2 - 2V_1}{20} = 0$$

$$\Rightarrow 3V_2 - 2V_1 = 80$$

**Equation 2**



**Step 4 – Finding node voltages,  $V_1$  and  $V_2$  by solving Equation 1 and Equation 2.  
substitute Equation 1 in Equation 2.**

$$3(4V_1 - 40) - 2V_1 = 80$$

$$\Rightarrow 12V_1 - 120 - 2V_1 = 80$$

$$\Rightarrow 10V_1 = 200$$

$$\Rightarrow V_1 = 20V$$

Substitute  $V_1 = 20V$  in Equation 1.

$$V_2 = 4(20) - 40$$

$$\Rightarrow V_2 = 40V$$



- **Step 5** – The voltage across  $20\ \Omega$  resistor is nothing but the node voltage  $V_2$  and it is equal to  $40\ \text{V}$ . Now, we can find the current flowing through  $20\ \Omega$  resistor by using Ohm's law.
  
- $I_{20\Omega} = V_2 / R$
  
- Substitute the values of  $V_2$  and  $R$  in the above equation.
  
- $I_{20\Omega} = 40 / 20 \Rightarrow I_{20\Omega} = 2\ \text{A}$



# Assessment

1. Nodal analysis is generally used to determine\_\_\_\_\_

- a) **Voltage**
- b) Current
- c) Resistance
- d) Power

2. If there are 10 nodes in a circuit, how many equations do we get?

- a) 10
- b) **9**
- c) 8
- d) 7

3. How many nodes are taken as reference nodes in a nodal analysis?

- a) **1**
- b) 2
- c) 3
- d) 4



THANK YOU