

REALIZATION OF GATES USING NOR GATE





SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

An Autonomous Institution

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

REALIZATION OF GATES USING NOR GATE

Dr.G.Arthy
Assistant Professor
Department of EEE
SNS College of Engineering



INTRODUCTION TO UNIVERSAL GATES



- What are Universal Gates?
- Why?



What are Universal Gates?



- NAND gate
- NOR gate

NOR Gate

2- Input NOR Gate



Truth Table

Input A	Input B	$0 = (A + B)'$
0	0	1
0	1	0
1	0	0
1	1	0

3 Input NOR Gate




Truth Table

Input A	Input B	Input C	$X = (A,B,C)$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

NOR as NOT


Input	Output	Rule
$(X+X)'$	$= X'$	Idempotent

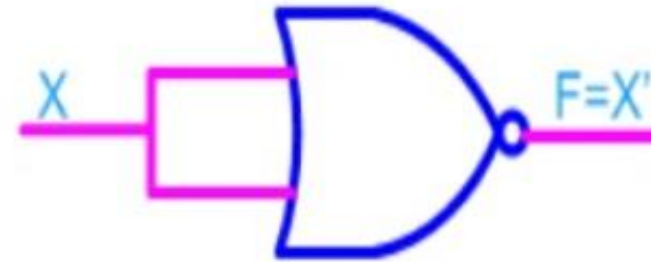

NOR as AND


Implementing AND using NOR gates

Input	Output	Rule
$((X+X)' + (Y+Y)')$	$= (X'+Y')$	Idempotent
	$= X'' \cdot Y''$	DeMorgan
	$= (X \cdot Y)$	Involution

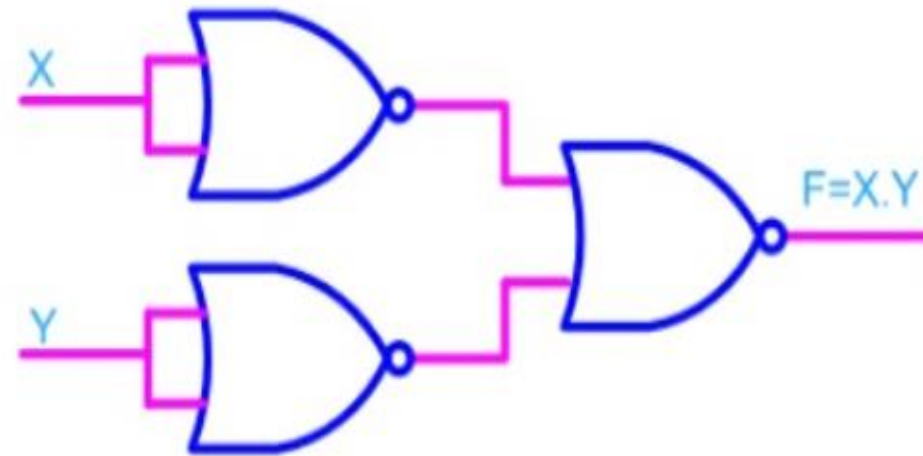


NOR as OR

Input	Output	Rule
$((X+Y)' + (X+Y)')$	$= ((X+Y)')$	Idempotent
	$= X+Y$	Involution

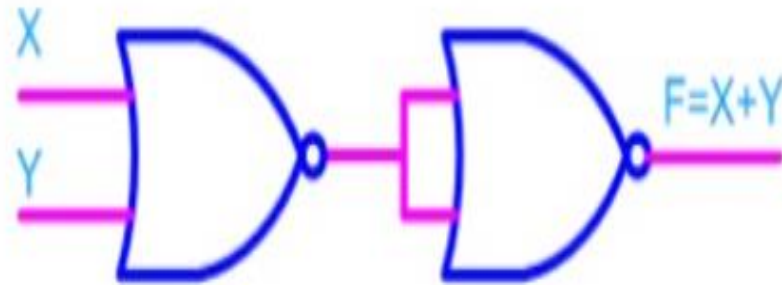

NAND USING NOR

Input	Output	Rule
$((X+Y)'+(X+Y)')'$	$= ((X+Y)')'$	Idempotent
	$= X+Y$	Involution
	$= (X+Y)'$	Idempotent

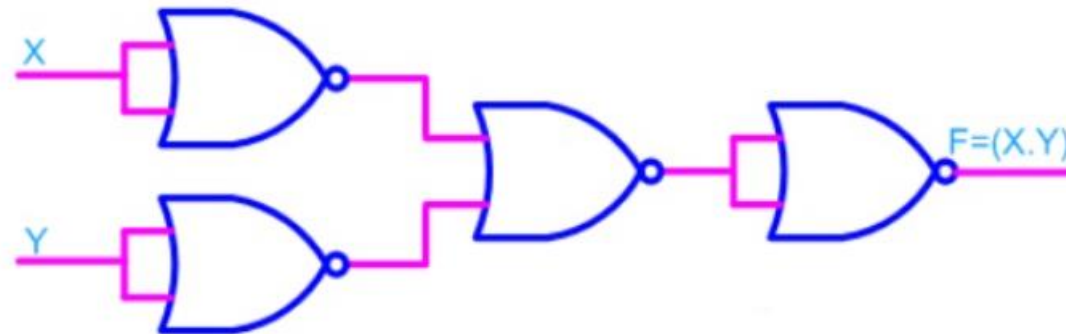

EXOR USING NOR

The output of the XOR gate is given by,

$$Y = \bar{A}B + A\bar{B} = A \oplus B$$

Taking the double complement on the right-hand side, we get,


$$Y = \overline{\overline{A \oplus B}} = \overline{A \odot B}$$

$$\Rightarrow Y = \overline{AB + \bar{A} \cdot \bar{B}}$$

$$\Rightarrow Y = \overline{AB + (\bar{A} + \bar{B})}$$

$$\Rightarrow Y = \overline{\bar{A}\bar{B} + (\bar{A} + \bar{B})}$$
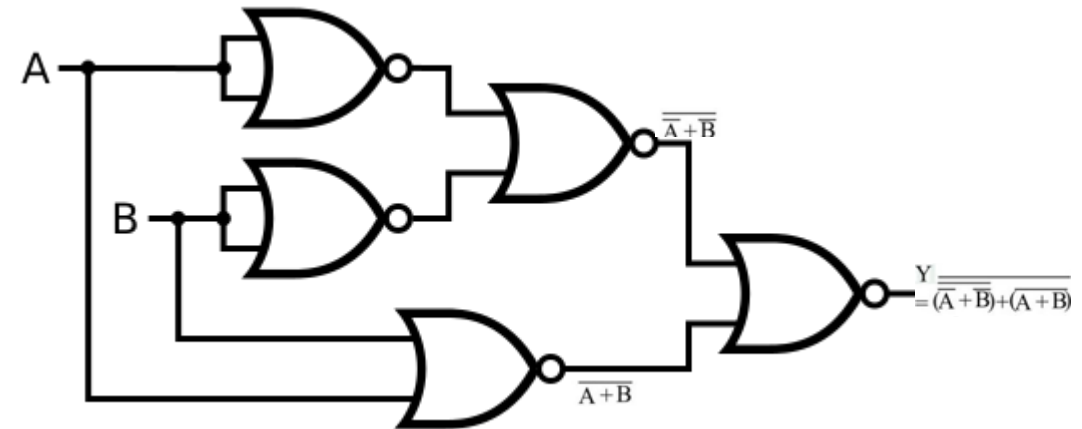
$$\Rightarrow Y = \overline{(\bar{A} + \bar{B}) + (\bar{A} + \bar{B})}$$



Hence, this Boolean expression is equivalent to the output of the XOR gate

EXNOR USING NOR

$$Y = \overline{\overline{A + (\overline{A + B})} + B + (\overline{A + B})}$$

$$Y = \overline{\overline{A + (\overline{A + B})} \cdot B + (\overline{A + B})}$$

$$Y = (A + \overline{A + B}) \cdot (B + \overline{A + B})$$


$$Y = (A + (\bar{A} \cdot \bar{B})) (B + (\bar{A} \cdot \bar{B}))$$

$$Y = (A + \bar{A})(A + \bar{B})(\bar{A} + B)(B + \bar{B})$$

$$Y = (A + \bar{B})(\bar{A} + B)$$

$$Y = A \cdot \bar{A} + \bar{A} \cdot \bar{B} + A \cdot B + B \cdot \bar{B}$$

$$\therefore Y = A \cdot B + \bar{A} \cdot \bar{B}$$

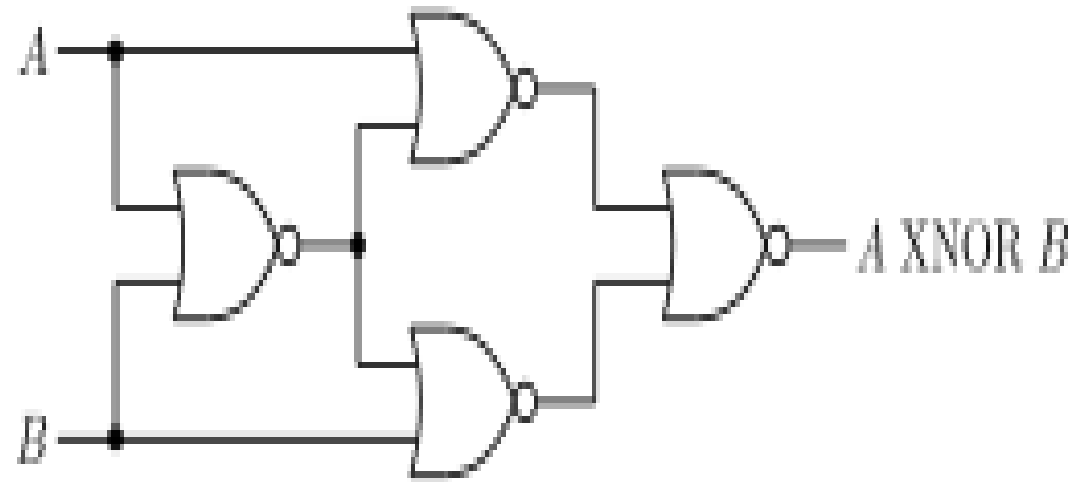



Assessment 1

1. How many NOR gates are required to implement one EXOR gate.

2. Draw the NAND gate using NOR gates.



*Thank
you*

