

DIGITAL ELECTRONICS:
HALF SUBTRACTOR





SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

An Autonomous Institution

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai





DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

HALF SUBTRACTOR

Dr.G.Arthy
Assistant Professor
Department of EEE
SNS College of Engineering

SUBTRACTORS

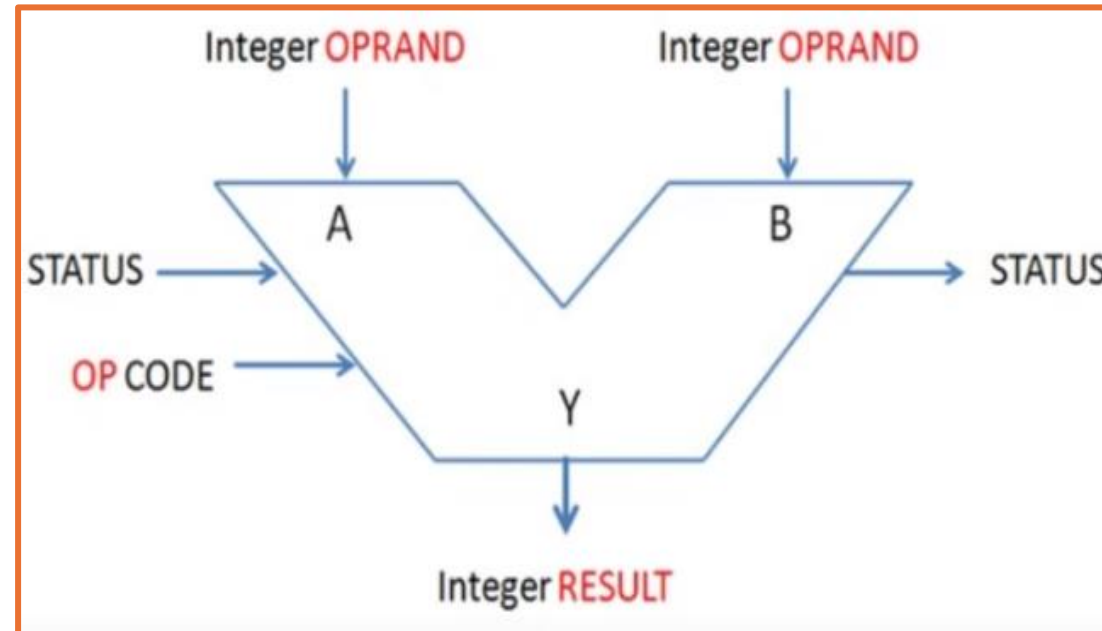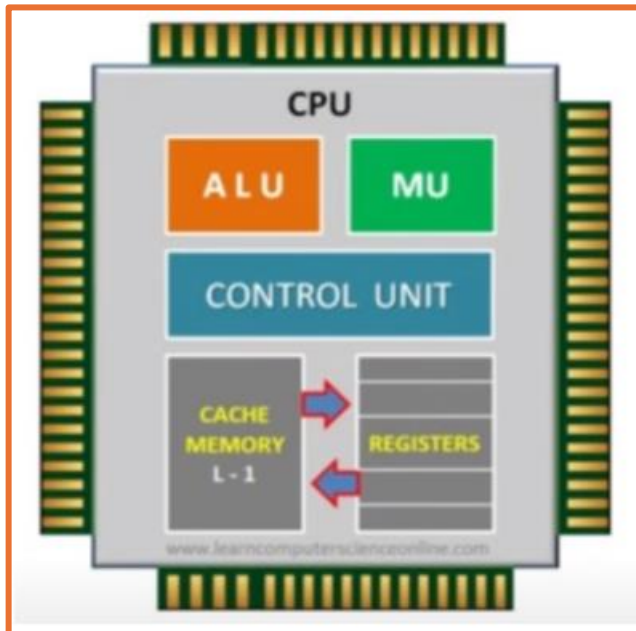- ✓ Subtractors are used to make arithmetical and logical Units(ALU).
- ✓ Types of Subtractor : Half Subtractor and Full Subtractor.





SUBTRACTORS




APPLICATIONS

- ✓ Half subtractor is used to reduce the force of audio or radio signals
- ✓ It can be used in amplifiers to reduce the sound distortion
- ✓ Half subtractor is used in ALU of processor
- ✓ It can be used to increase and decrease operators and also calculates the addresses

HALF SUBTRACTOR

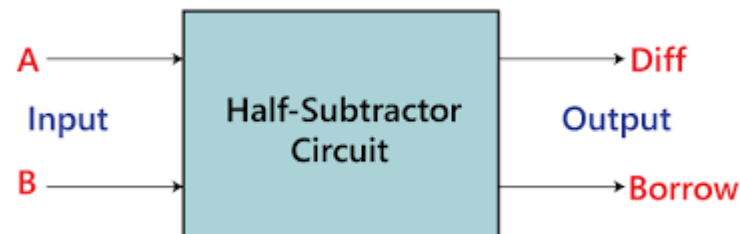
- ✓ A combinational logic circuit which is designed to subtract two binary digits is called as a **half subtractor**.
- ✓ It has two input terminals and two output terminals for difference and borrow.
- ✓ The half subtractor circuit is designed by connecting an one EX-OR gate, one AND and one NOT gate.



DESIGN OF HALF SUBTRACTOR

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Step 1 : Write the Truth Table

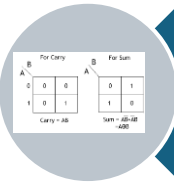


Step 2 : Draw K-Map

$$\text{Sum (S)} = A \oplus B$$

$$\text{Carry (C)} = A \cdot B$$

Step 3 : Form the Boolean Expression

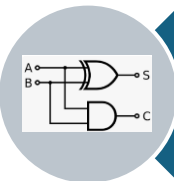

Step 4 : Draw the circuit Diagram




HALF SUBTRACTOR-TRUTH TABLE

Inputs		Outputs	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


HALF SUBTRACTOR – K MAP

For Difference

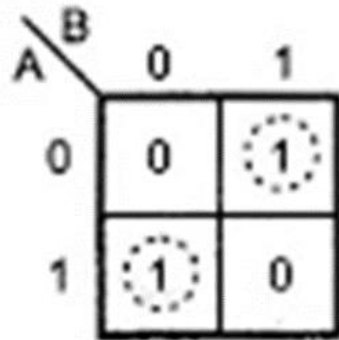

$$\begin{aligned} \text{Difference} &= A\bar{B} + \bar{A}B \\ &= A \oplus B \end{aligned}$$

For Borrow

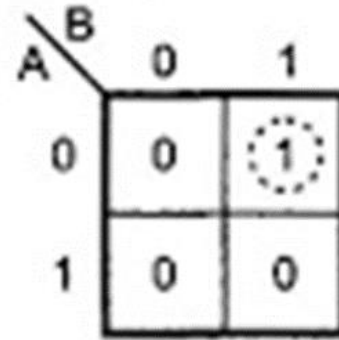

$$\text{Borrow} = \bar{A}B$$


Inputs		Outputs	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

HALF SUBTRACTOR- CIRCUIT

Boolean Expression

$$\begin{aligned} \text{Difference} &= A\bar{B} + \bar{A}B \\ &= A \oplus B \end{aligned}$$

$$\text{Borrow} = \bar{A}B$$

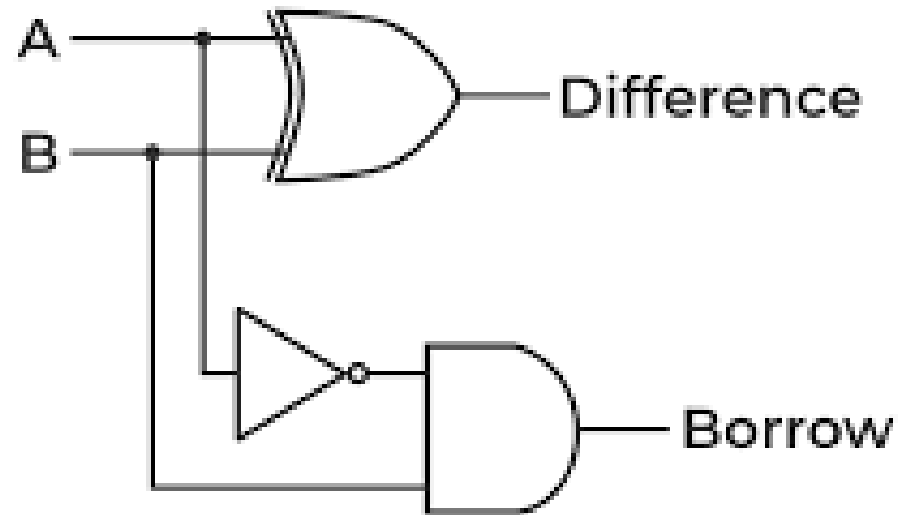



Assessment



1. How many gates are required to realize a half subtractor?

2. Write the equation for difference and borrow of half subtractor.



*Thank
you*

