

DIGITAL ELECTRONICS:
DEMULTIPLEXER





SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

An Autonomous Institution

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

DEMULTIPLEXER

*Dr.G.Arthy
Assistant Professor
Department of EEE
SNS College of Engineering*



DEMULTIPLEXER

De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer.


Demultiplexer is a **data distributor** which takes a single input and gives several outputs.

A Demultiplexer is a combinational circuit that has **one input line** , **2^n output lines** and **'n' selection lines**.

APPLICATIONS



- ✓ Demultiplexers are used in several input and output devices for data routing.
- ✓ Demultiplexers are used in digital control systems to select one signal from a mutual stream of signals.
- ✓ Demultiplexers are also employed for data transmission in synchronous systems.
- ✓ Demultiplexers are also utilized in data acquisition systems.
- ✓ Demultiplexers can be used for generating Boolean functions.
- ✓ Demultiplexers can be used in serial to parallel converters.
- ✓ Demultiplexers are used for broadcasting of ATM packets.
- ✓ Demultiplexers can also be used to design automatic test equipment, etc.

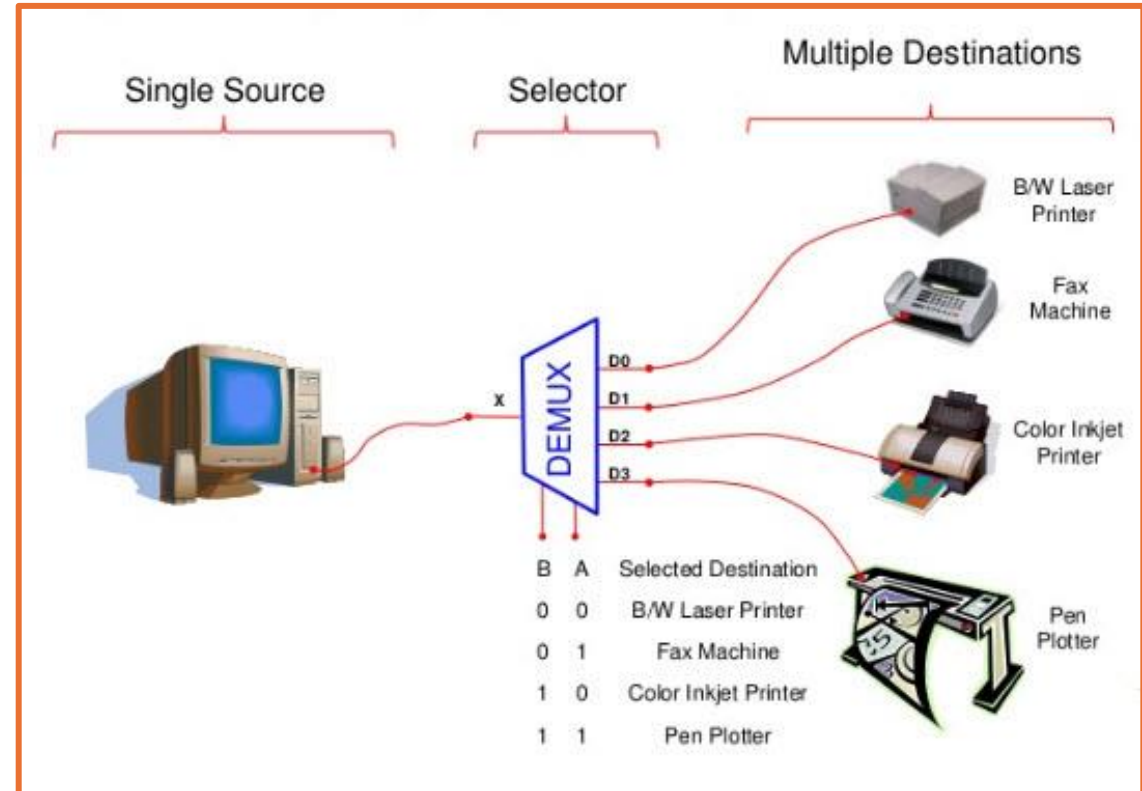




TYPES OF DEMULTIPLEXERS



- ✓ 1:2 Demultiplexer (1select line)
- ✓ 1:4 Demultiplexer (2 select lines)
- ✓ 1:8 Demultiplexer(3 select lines)
- ✓ 1:16 Demultiplexer (4 select lines)

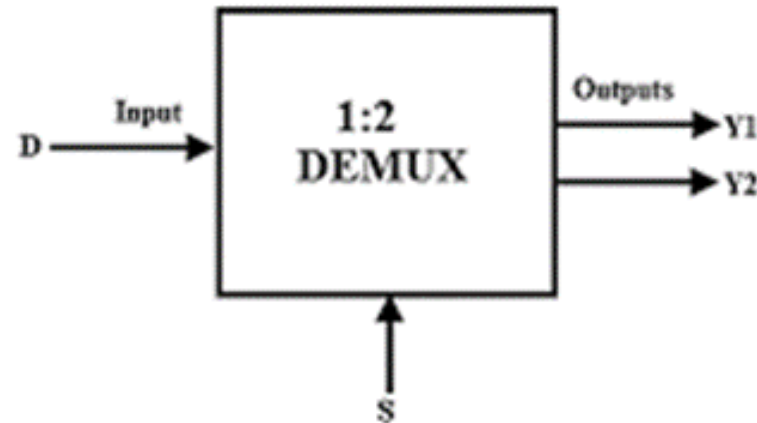1:2 DEMULTIPLEXER

There is one input (D), two outputs (Y_1 and Y_2), 1 selection line(S).



1:2 DEMULTIPLEXER


Truth Table

S (Selection line)	Y ₁	Y ₂
0	D	0
1	0	D

Boolean Expression

$$Y_1 = DS'$$

$$Y_2 = DS$$

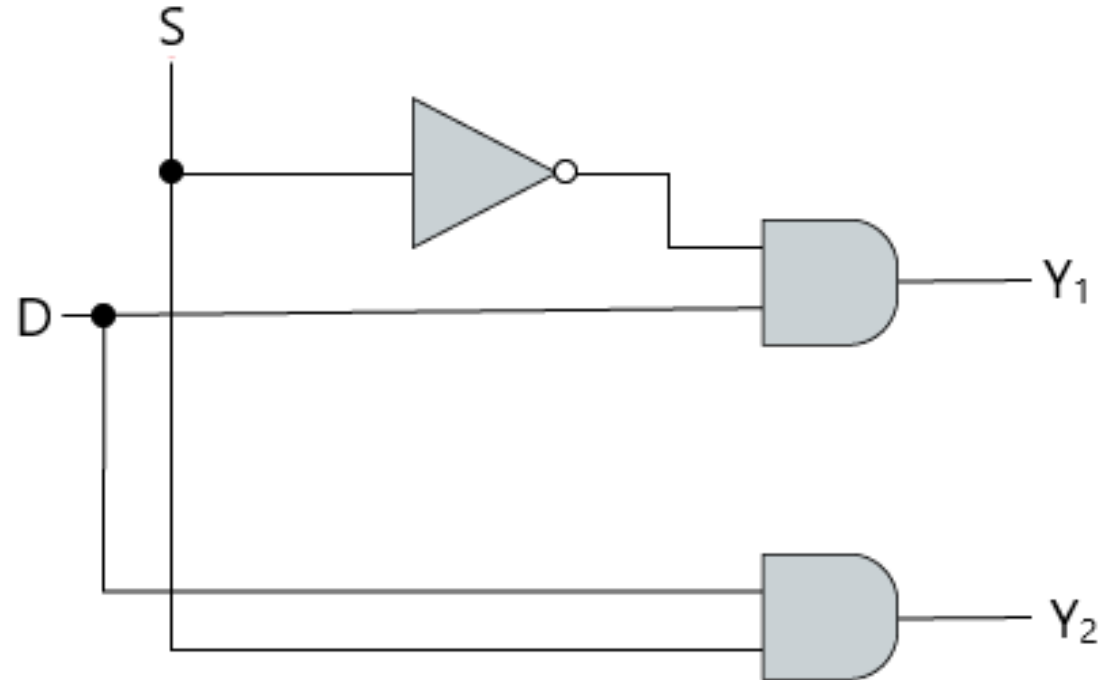




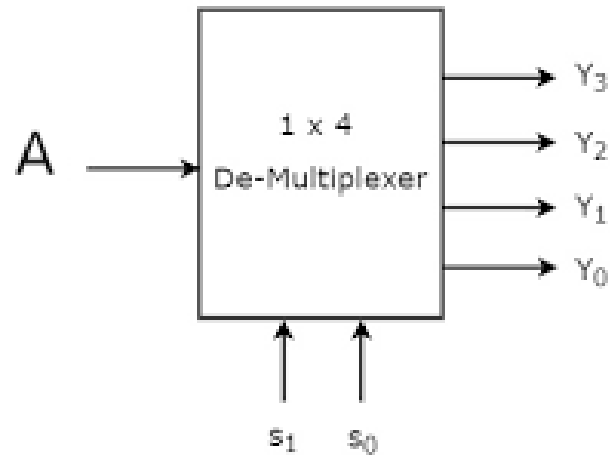1 : 4 DEMULTIPLEXER



There are four Outputs (Y_0, Y_1, Y_2, Y_3), 2 selection line(S_0, S_1) and single Input(A).



1:4 DEMULTIPLEXER

Truth Table

S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	A
0	1	0	0	A	0
1	0	0	A	0	0
1	1	A	0	0	0


Boolean Expression

$$Y_0 = A S_0' S_1'$$

$$Y_1 = A S_1' S_0$$


$$Y_2 = A S_1 S_0'$$

$$Y_3 = A S_1 S_0$$

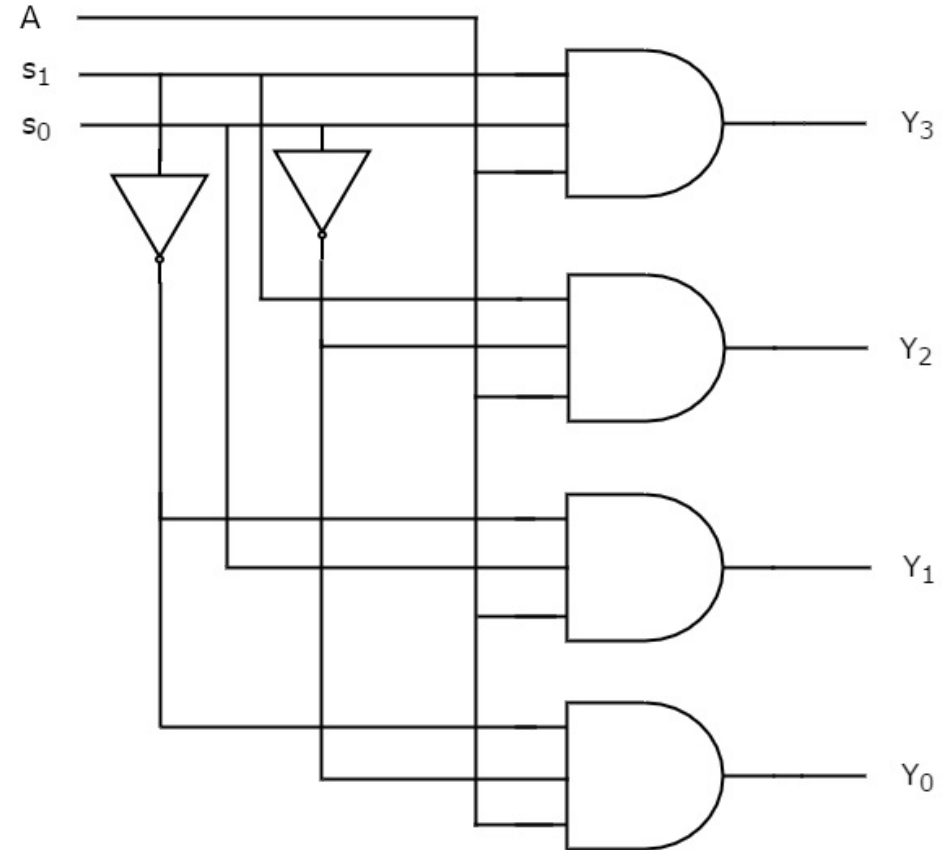

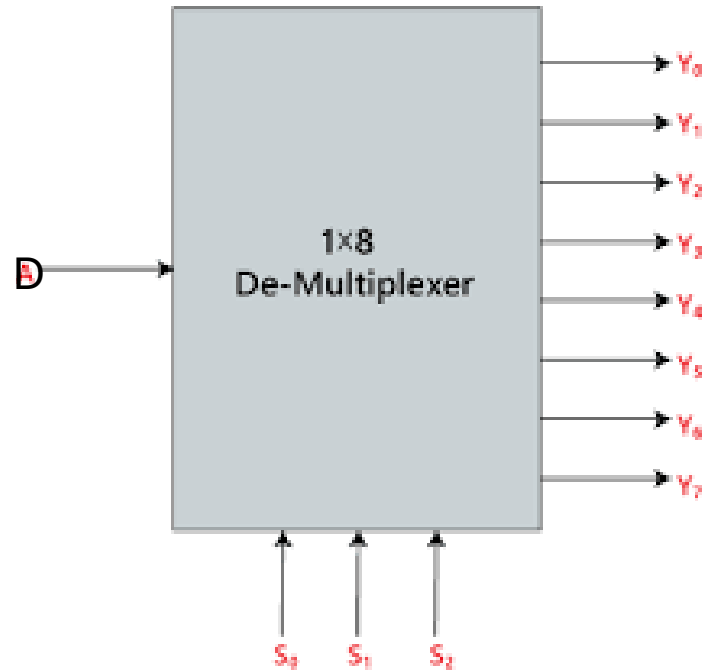1 : 8 DEMULTIPLEXER

There are eight outputs, ($Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6,$ and Y_7), 3 selection line (S_0, S_1, S_2) and single Input (D).



1 : 8 DEMULTIPLEXER

Data Input	Select Inputs			Outputs							
D	S ₂	S ₁	S ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
D	0	0	0	0	0	0	0	0	0	0	D
D	0	0	1	0	0	0	0	0	0	D	0
D	0	1	0	0	0	0	0	0	D	0	0
D	0	1	1	0	0	0	0	D	0	0	0
D	1	0	0	0	0	0	D	0	0	0	0
D	1	0	1	0	0	D	0	0	0	0	0
D	1	1	0	0	D	0	0	0	0	0	0
D	1	1	1	D	0	0	0	0	0	0	0

$$Y_0 = S_0' \cdot S_1' \cdot S_2' \cdot D$$

$$Y_1 = S_0 \cdot S_1' \cdot S_2' \cdot D$$

$$Y_2 = S_0' \cdot S_1 \cdot S_2' \cdot D$$


$$Y_3 = S_0 \cdot S_1 \cdot S_2' \cdot D$$

$$Y_4 = S_0' \cdot S_1' \cdot S_2 \cdot D$$

$$Y_5 = S_0 \cdot S_1' \cdot S_2 \cdot D$$

$$Y_6 = S_0' \cdot S_1 \cdot S_2 \cdot D$$
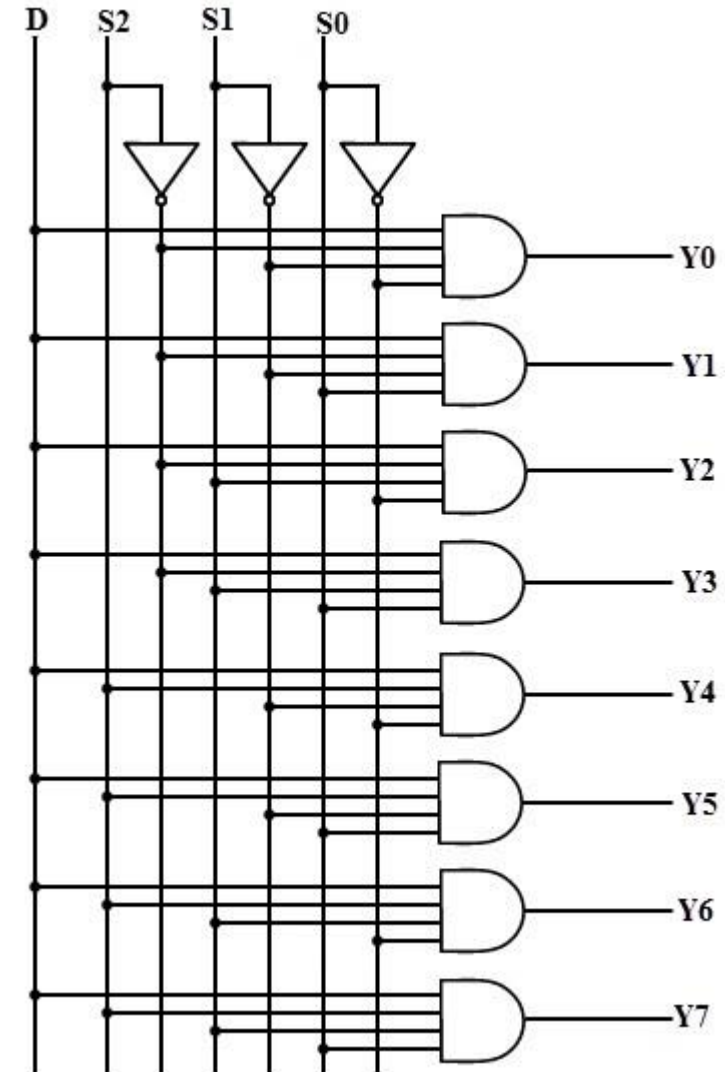
$$Y_7 = S_0 \cdot S_1 \cdot S_2 \cdot D$$





Assessment

1. For a 8:1 Demultiplexer, how many selection lines are required?

2. Name the device that converts serial data to parallel data .



*Thank
you*

