

DIGITAL ELECTRONICS:
MULTIPLEXER





SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

An Autonomous Institution

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

MULTIPLEXER

***Dr.G.Arthy
Assistant Professor
Department of EEE
SNS College of Engineering***




MULTIPLEXER

A device that selects between several analog or digital input signals and forwards the selected input to a single output line. It is also known as a data selector.

A multiplexer is a combinational circuit that has **2^n input lines**, '**n**' **selection lines** and a **single output line**.

APPLICATIONS

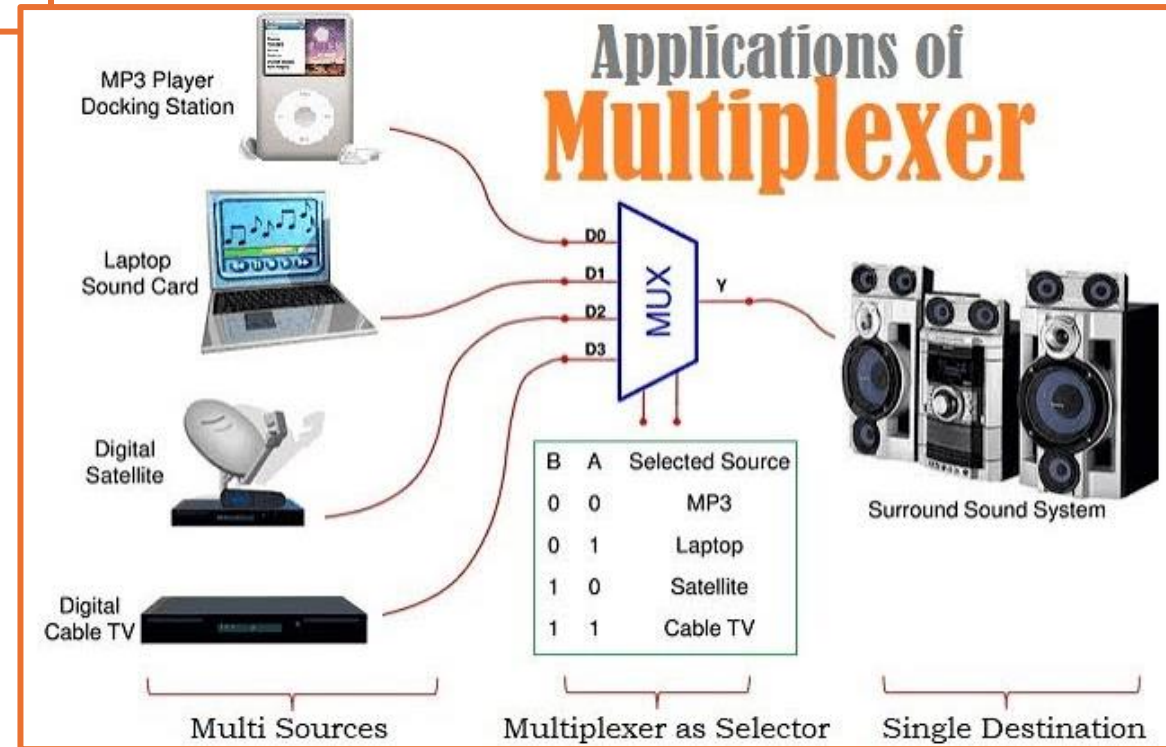- ✓ Communication System
- ✓ Arithmetic Logic Unit
- ✓ Parallel to Serial Converter






TYPES OF MULTIPLEXERS



- ✓ 2:1 multiplexer (1select line)
- ✓ 4:1 multiplexer (2 select lines)
- ✓ 8:1 multiplexer(3 select lines)
- ✓ 16:1 multiplexer (4 select lines)

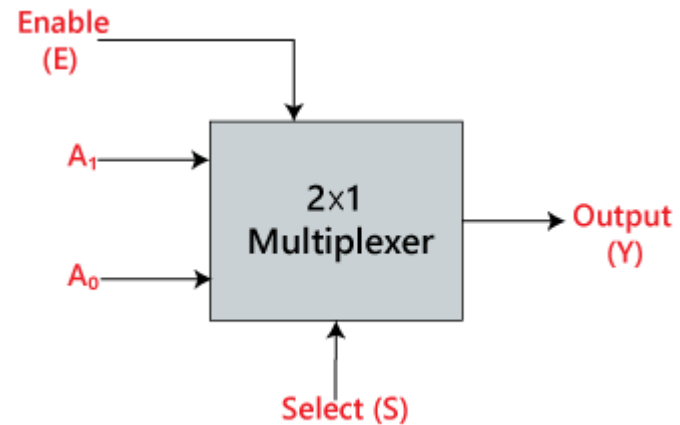2: 1 MULTIPLEXER


There are two inputs, (A_0 and A_1), 1 selection line (S) and single output (Y).



2: 1MULTIPLEXER


INPUTS	Output
S	Y
0	A_0
1	A_1

$$Y = S'.A_0 + S.A_1$$

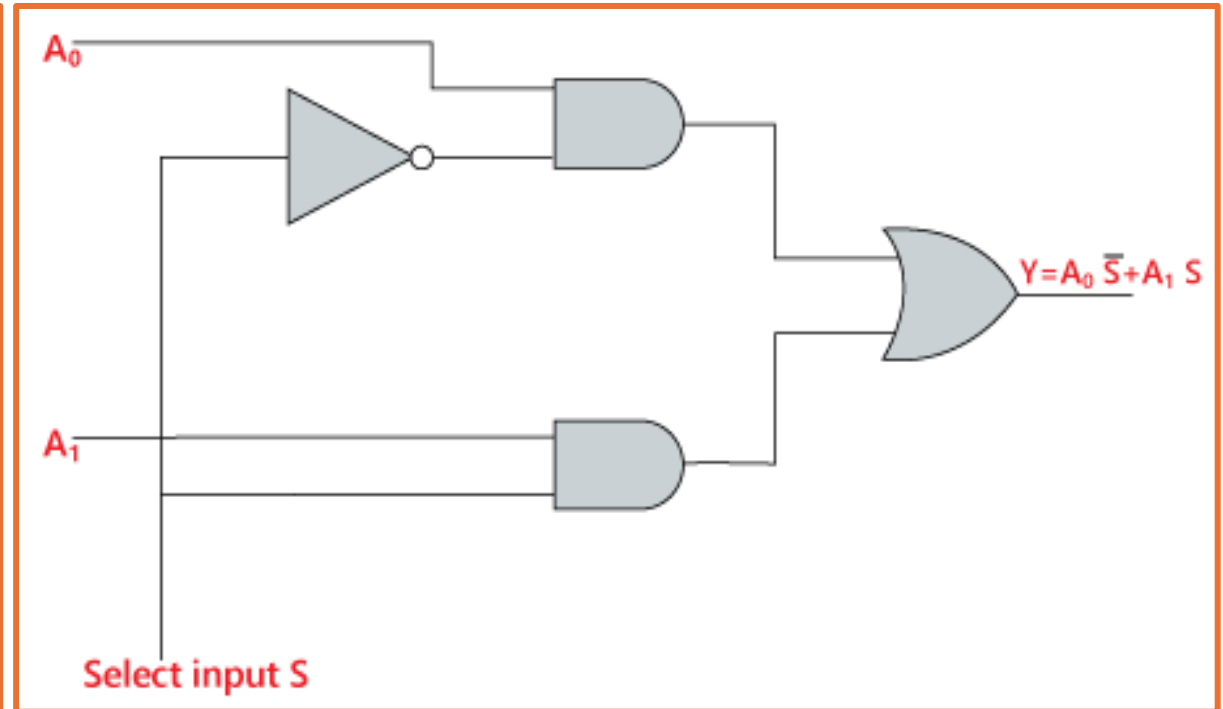

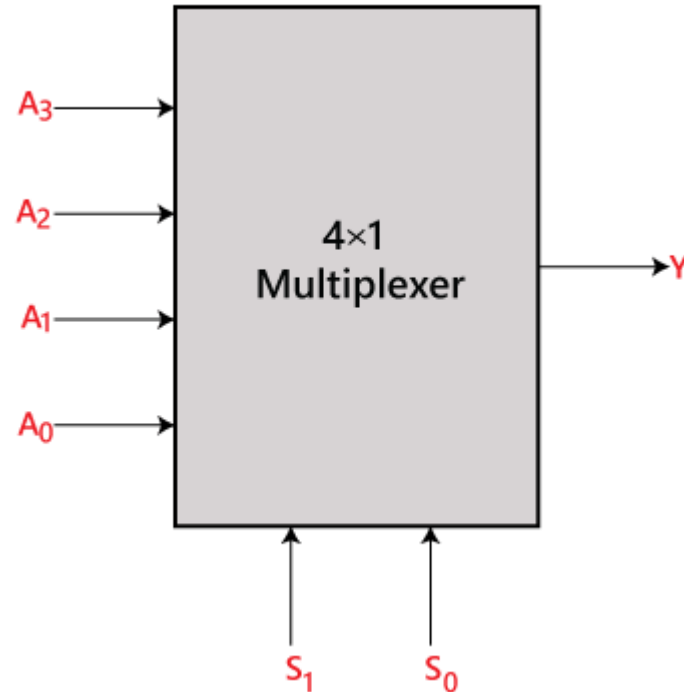4 : 1 MULTIPLEXER

There are four inputs, (A_0, A_1, A_2, A_3), 2 selection line (S_0, S_1) and single output (Y).




4 : 1 MULTIPLEXER

INPUTS		Output
S ₁	S ₀	Y
0	0	A ₀
0	1	A ₁
1	0	A ₂
1	1	A ₃

The logical expression of the term Y is as follows:

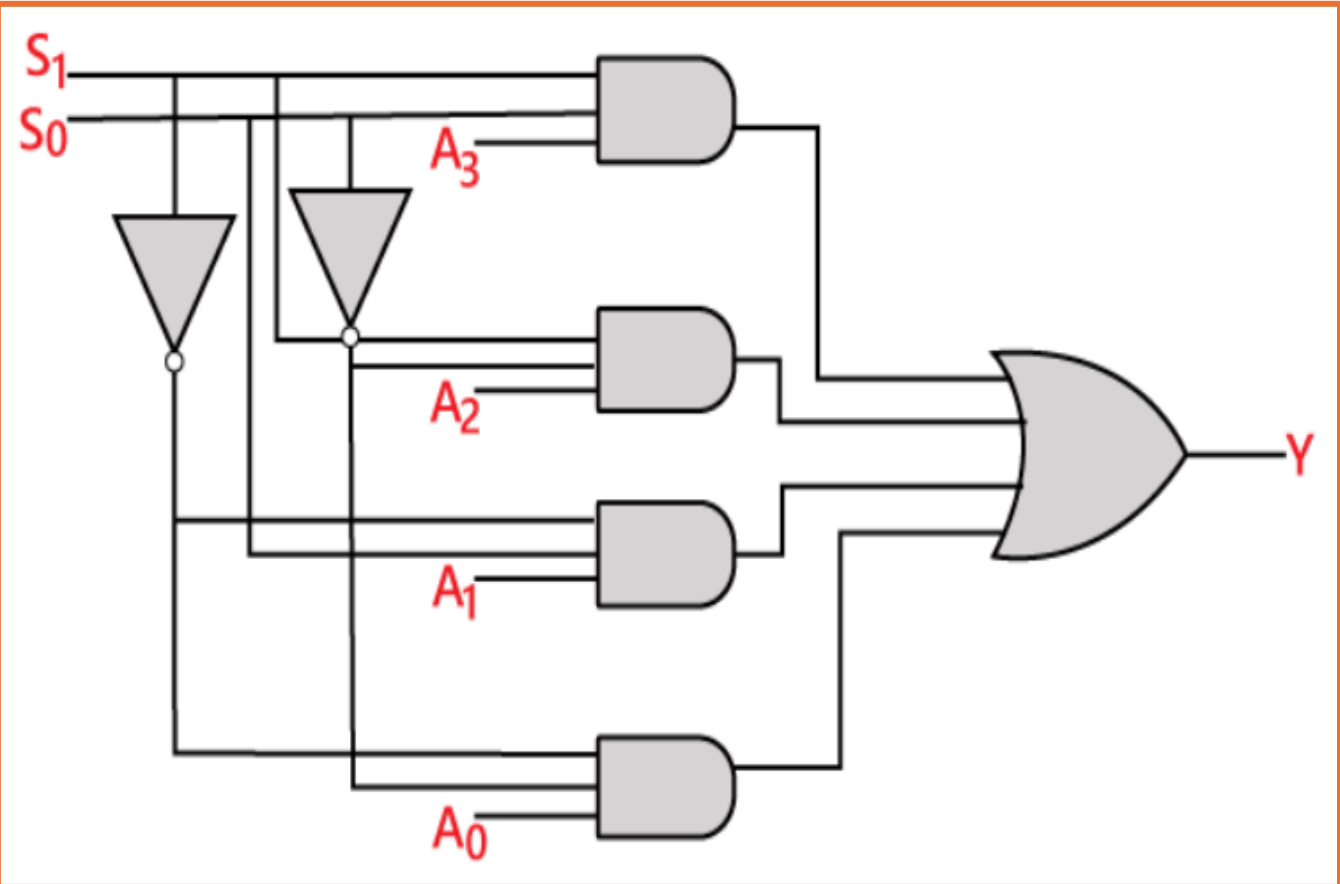
$$Y = S_1' S_0' A_0 + S_1' S_0 A_1 + S_1 S_0' A_2 + S_1 S_0 A_3$$





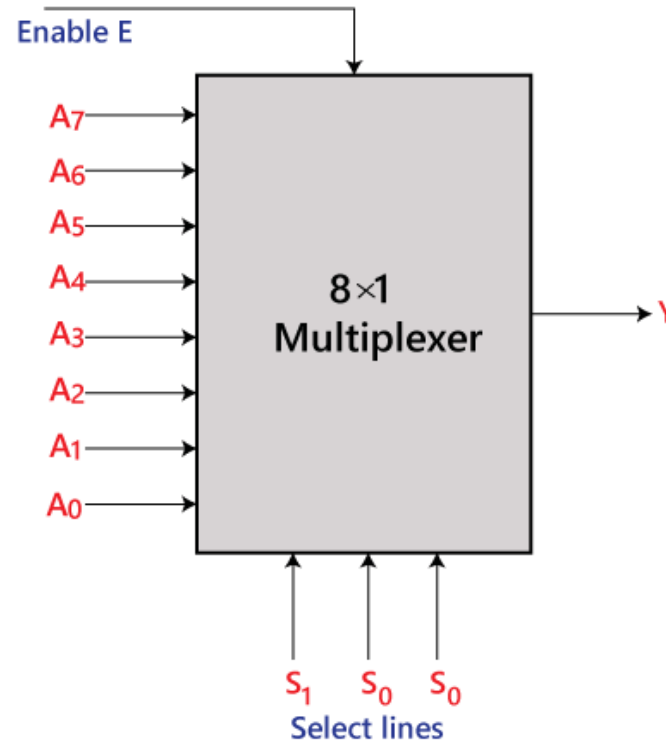8 : 1 MULTIPLEXER


There are eight inputs, ($A_0, A_1, A_2, A_3, A_4, A_5, A_6,$ and A_7), 3 selection line (S_0, S_1, S_2) and single output (Y).



8 : 1 MULTIPLEXER

INPUTS			Output
S ₂	S ₁	S ₀	Y
0	0	0	A ₀
0	0	1	A ₁
0	1	0	A ₂
0	1	1	A ₃
1	0	0	A ₄
1	0	1	A ₅
1	1	0	A ₆
1	1	1	A ₇
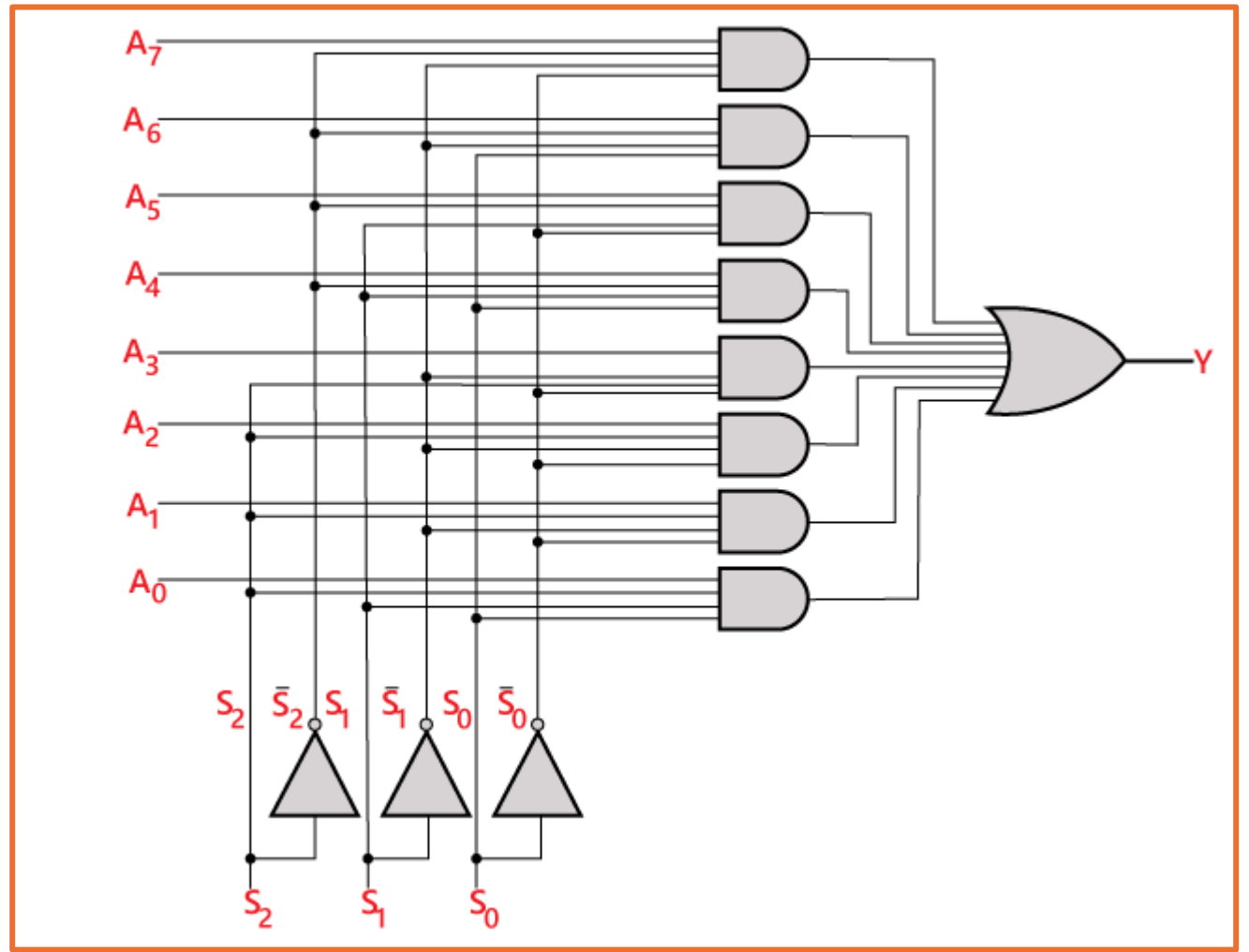
$$Y = S_0' \cdot S_1' \cdot S_2' \cdot A_0 + S_0 \cdot S_1' \cdot S_2' \cdot A_1 + S_0' \cdot S_1 \cdot S_2' \cdot A_2 + S_0 \cdot S_1 \cdot S_2' \cdot A_3 + S_0' \cdot S_1' \cdot S_2 \cdot A_4 + S_0 \cdot S_1' \cdot S_2 \cdot A_5 + S_0' \cdot S_1 \cdot S_2 \cdot A_6 + S_0 \cdot S_1 \cdot S_2 \cdot A_7$$





Assessment

1. For a 16:1 Multiplexer, how many selection lines are required?

2. Name the device that converts parallel data to serial data.



*Thank
you*

