

***DIGITAL ELECTRONICS:  
DECODER***





# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai




## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

### DECODERS


*Dr.G.Arthy*  
*Assistant Professor*  
*Department of EEE*  
*SNS College of Engineering*
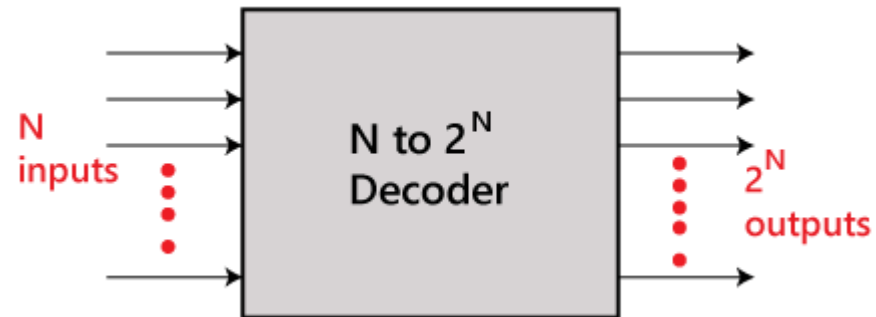
# DECODERS

- ✓ The combinational circuit that change the binary information into  $2^N$  output lines is known as Decoders.
- ✓ The binary information is passed in the form of  $N$  input lines.
- ✓ The output lines define the  $2^N$ -bit code for the binary information.



# APPLICATIONS

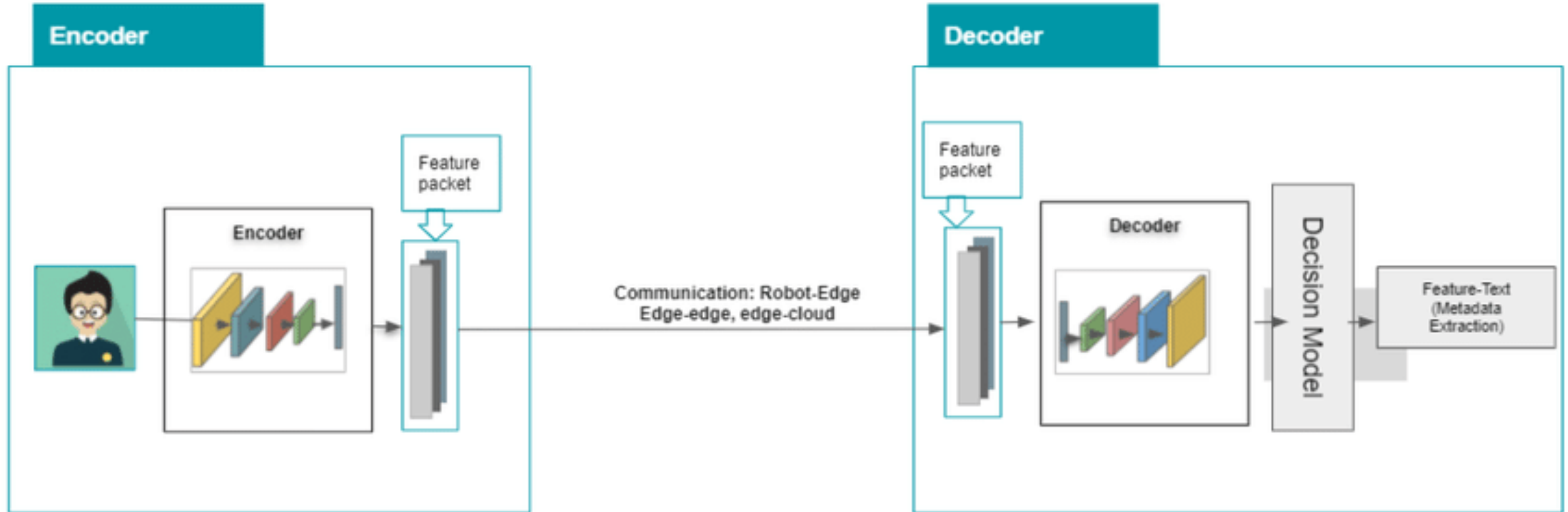




# TYPES OF ENCODERS



- ✓ 2 to 4 Decoder
- ✓ 3 to 8 Decoder
- ✓ 4 to 16 Decoder
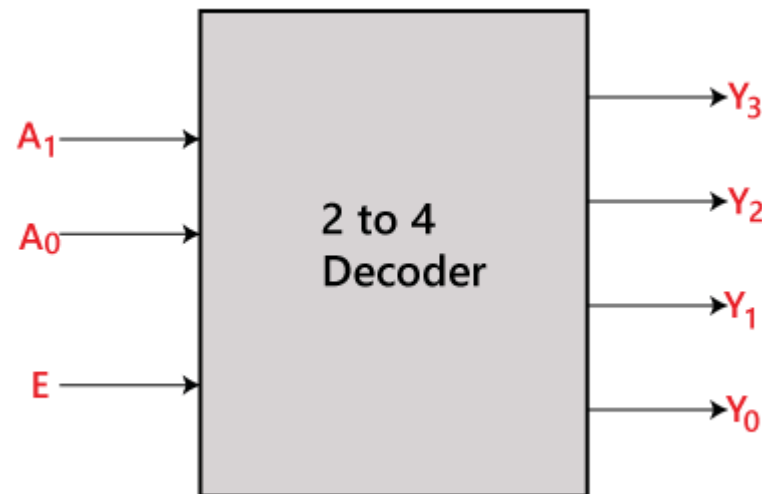
## 2:4 LINE DECODER

In the 2 to 4 line decoder, there is a total of three inputs, i.e.,  $A_0$ , and  $A_1$  and  $E$  and four outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$ . For each combination of inputs, when the enable 'E' is set to 1, one of these four outputs will be 1.



# 2: 4 LINE DECODER


Enable	INPUTS		OUTPUTS				
	E	A <sub>1</sub>	A <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	X	X	0	0	0	0	0
1	0	0	0	0	0	0	1
1	0	1	0	0	1	0	0
1	1	0	0	1	0	0	0
1	1	1	1	0	0	0	0

$$Y_3 = E \cdot A_1 \cdot A_0$$

$$Y_2 = E \cdot A_1 \cdot A_0'$$


$$Y_1 = E \cdot A_1' \cdot A_0$$

$$Y_0 = E \cdot A_1' \cdot A_0'$$

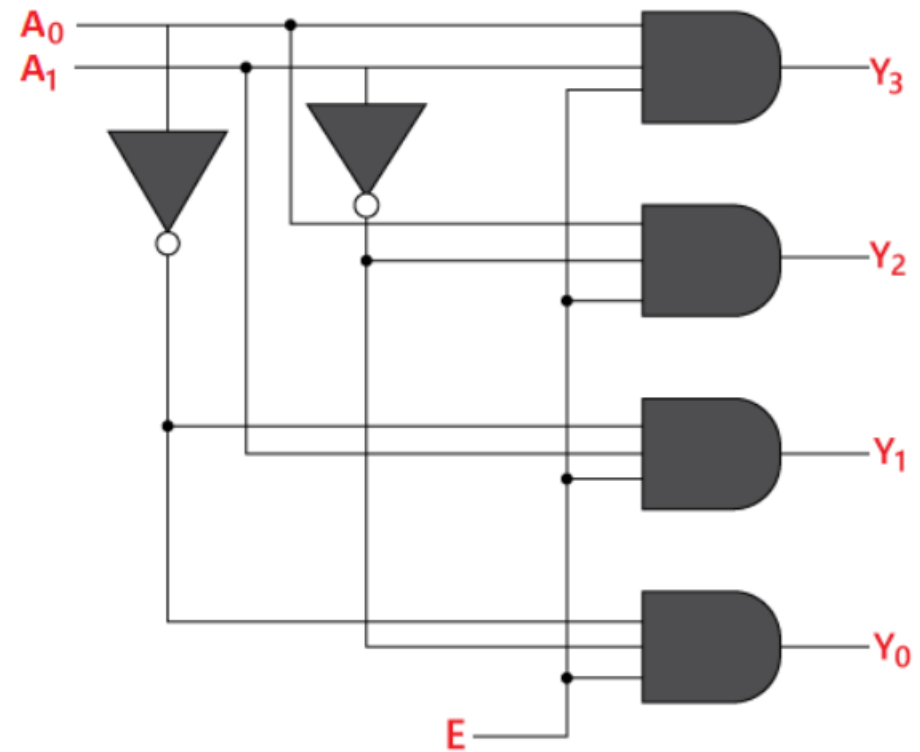
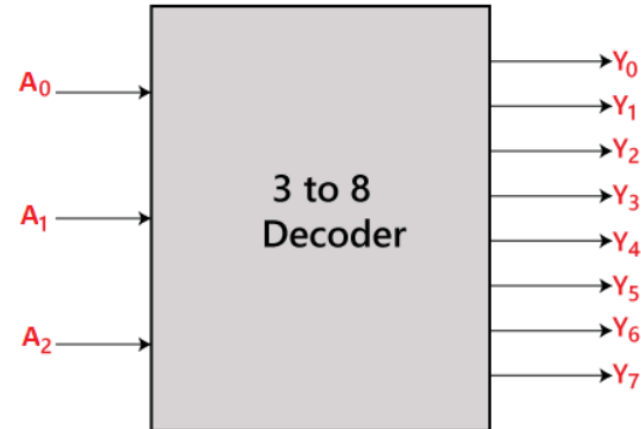
## 3: 8 LINE DECODER

The 3 to 8 line decoder is also known as Binary to Octal Decoder. In a 3 to 8 line decoder, there is a total of eight outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ ,  $Y_3$ ,  $Y_4$ ,  $Y_5$ ,  $Y_6$ , and  $Y_7$  and three outputs, i.e.,  $A_0$ ,  $A_1$ , and  $A_2$ . This circuit has an enable input 'E'. Just like 2 to 4 line decoder, when enable 'E' is set to 1, one of these four outputs will be 1.





# 3:8 LINE DECODER

Enable	INPUTS			Outputs							
	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

$$Y_0 = A_0' \cdot A_1' \cdot A_2'$$

$$Y_1 = A_0 \cdot A_1' \cdot A_2'$$

$$Y_2 = A_0' \cdot A_1 \cdot A_2'$$


$$Y_3 = A_0 \cdot A_1 \cdot A_2'$$

$$Y_4 = A_0' \cdot A_1' \cdot A_2$$

$$Y_5 = A_0 \cdot A_1' \cdot A_2$$

$$Y_6 = A_0' \cdot A_1 \cdot A_2$$

$$Y_7 = A_0 \cdot A_1 \cdot A_2$$

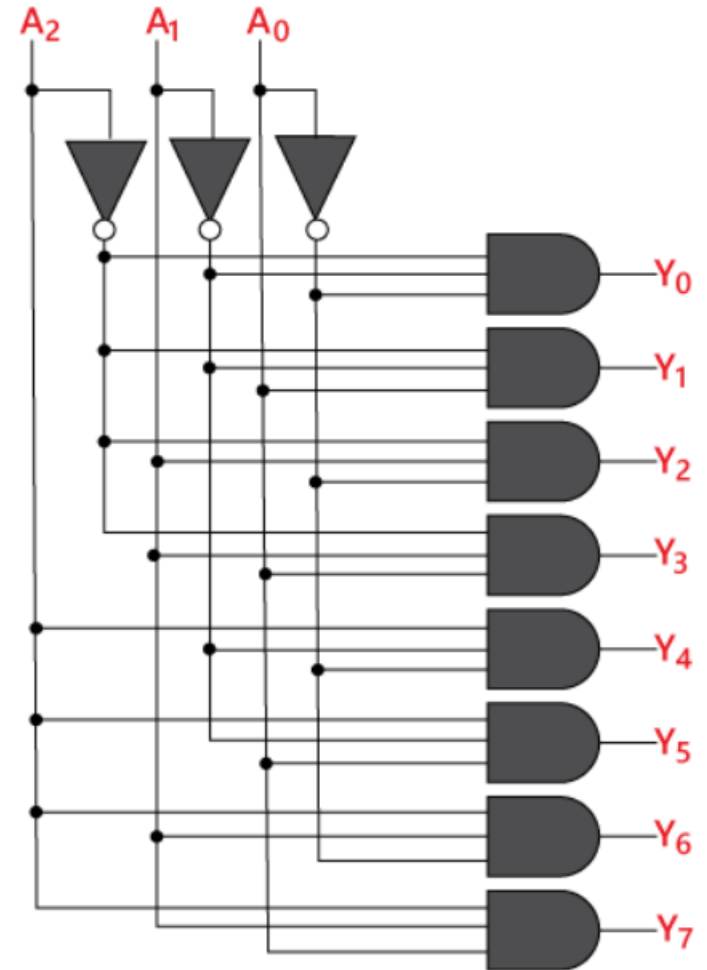



# Assessment

1. A 4 to 16 decoder has \_\_\_\_ number of inputs.
  2. Write any two applications of Decoder.
-



*Thank  
you*

