

***DIGITAL ELECTRONICS:***  
***SR LATCH***





# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

### SR LATCH

*Dr.G.Arthy  
Assistant Professor  
Department of EEE  
SNS College of Engineering*



# SR LATCH



- ✓ Latches are digital circuits that store a single bit of information and hold its value until it is updated by new input signals.
- ✓ They are used in digital systems as temporary storage elements to store binary information.
- ✓ Latches are level-sensitive devices. Latches are useful for the design of the asynchronous sequential circuit. Latches are sequential circuit with two stable states.


# SR LATCH

## APPLICATIONS


- ✓ Latches are widely used in digital systems for various applications, including data storage, control circuits, and flip-flop circuits. They are often used in combination with other digital circuits to implement sequential circuits, such as state machines and memory elements.
 
# SR LATCH

- ✓ SR (Set-Reset) Latch – They are also known as preset and clear states. The SR latch forms the basic building blocks of all other types of flip-flops.




# SR LATCH WITH NOR GATE

 

SR Latch is a circuit with:

- ✓ (i) 2 cross-coupled NOR gate or 2 cross-coupled NAND gate.
- ✓ (ii) 2 input S for SET and R for RESET.
- ✓ (iii) 2 output Q,  $\bar{Q}$ .

# SR LATCH WITH NOR GATE

 

When  $S=0, R=1 \rightarrow Q = 0$  and  $Q' = 1$

When  $S=0, R=0 \rightarrow Q = 0$  and  $Q' = 1$  (Memory)

When  $S=1, R=0 \rightarrow Q = 1$  and  $Q' = 0$


When  $S=0, R=0 \rightarrow Q = 1$  and  $Q' = 0$  (Memory)

When  $S=1, R=1 \rightarrow Q = 0$  and  $Q' = 0$  (Invalid)

SR Latch Truth Table

Inputs		Outputs	
$S$	$R$	$Q$	$\bar{Q}$
0	0	unchanged	
0	1	0	1
1	0	1	0
1	1	unstable	

# SR LATCH WITH NAND GATE

 

When  $S=0, R=1 \rightarrow Q = 1$  and  $Q' = 0$

When  $S=1, R=1 \rightarrow Q = 1$  and  $Q' = 0$  (Memory)

When  $S=1, R=0 \rightarrow Q = 0$  and  $Q' = 1$

When  $S=1, R=1 \rightarrow Q = 0$  and  $Q' = 1$  (Memory)

When  $S=0, R=0 \rightarrow Q = 1$  and  $Q' = 1$  (Invalid)

SR Latch Truth Table

Inputs		Outputs	
$S$	$R$	$Q$	$\bar{Q}$
0	0	unstable	
0	1	1	0
1	0	0	1
1	1	unchanged	





# Assessment

1. What is the purpose of a Set-Reset (SR) latch in digital electronics?

---

2. In an SR latch, what is the state when both the Set (S) and Reset (R) inputs are asserted simultaneously?

---



*Thank  
you*

