

***DIGITAL ELECTRONICS:***  
***SR FLIPFLOP***





# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

### SR FlipFlop

*Dr.G.Arthy*  
*Assistant Professor*  
*Department of EEE*  
*SNS College of Engineering*



# SR FLIPFLOP

- ✓ FlipFlops are digital circuits that store a single bit of information and hold its value until it is updated by new input signals.
- ✓ They are used in digital systems as temporary storage elements to store binary information.
- ✓ FlipFlops are latches with clocks. They are commonly edge-sensitive devices. FlipFlops are useful for the design of the synchronous sequential circuit.




# SR FLIPFLOP

## APPLICATIONS


- ✓ Flip Flops are used as the basic storage unit.
- ✓ Flip Flops are used as counters.
- ✓ flip flop is its use as Frequency Dividers
- ✓ Flip Flops also find their application in digital signal processing which is very crucial in electronics. In DSP, flip flops are used for data sampling, buffering, and synchronization of data.
- ✓ Flip Flops are largely used as shift registers
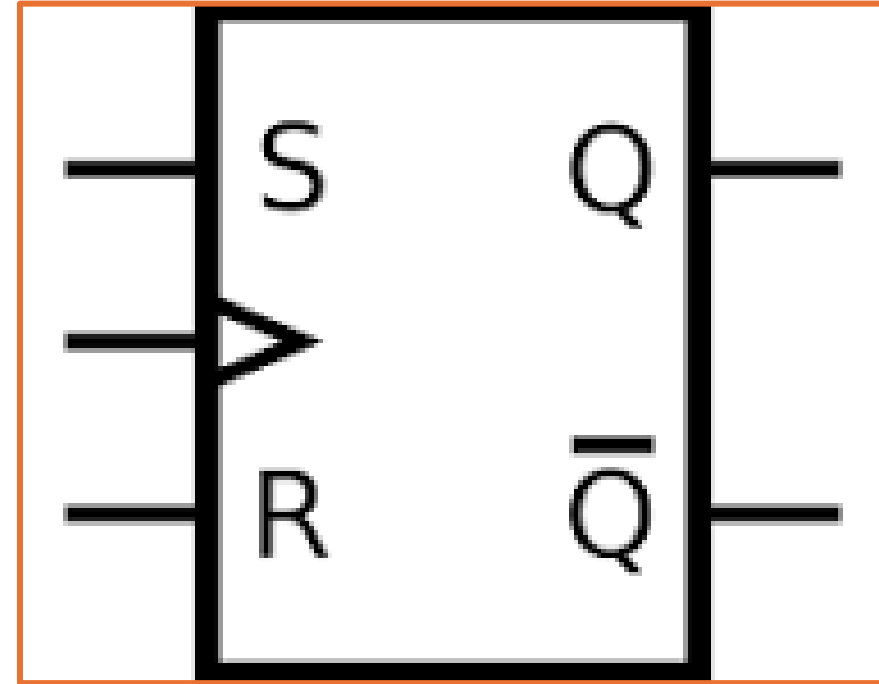
# SR FLIP FLOP

- ✓ It consists of two inputs namely 'Set' and 'Reset' pin and it has corresponding output pins Q and Q'. When the input of 'S' pin is high, the output 'Q' is high and Q' is low.



# SR FLIPFLOP WITH NAND GATE

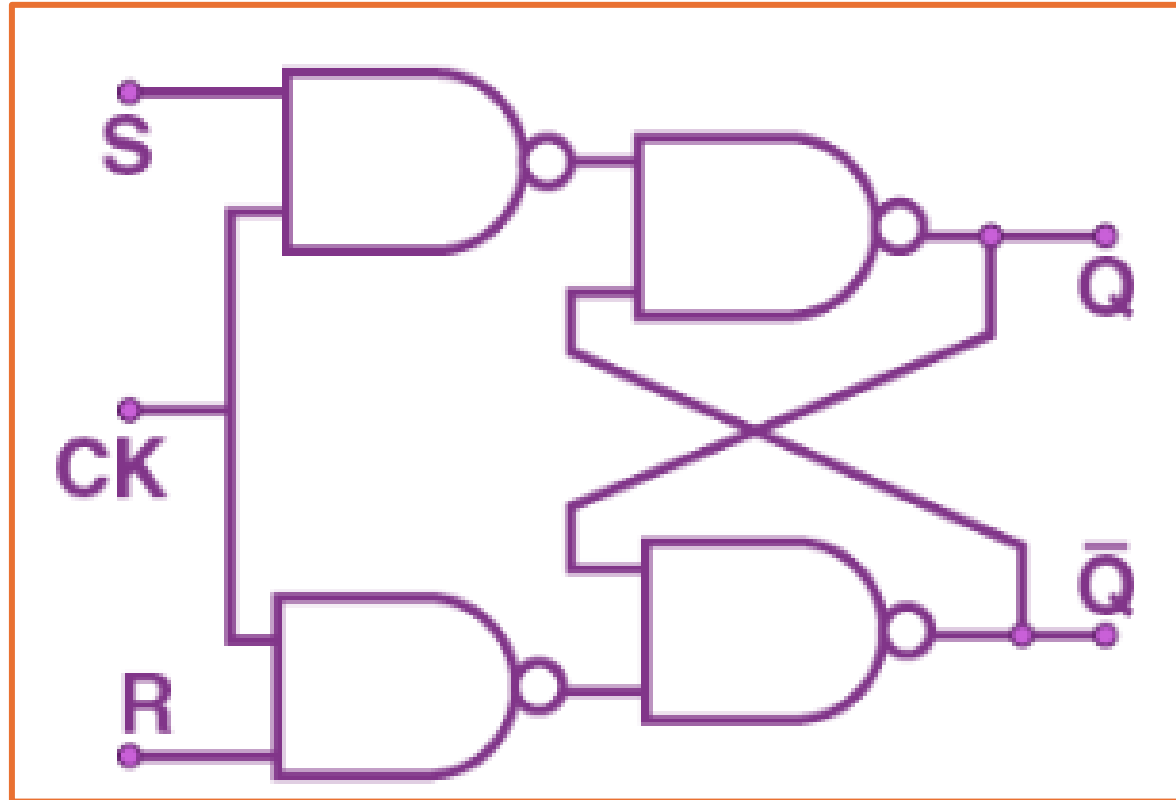

# SR FLIPFLOP TRUTH TABLE

INPUTS			OUTPUT	STATE
CLK	S	R	Q	
X	0	0	No Change	Previous
↑	0	1	0	Reset
↑	1	0	1	Set
↑	1	1	-	Forbidden

# SR FLIPFLOP CHARACTERISTIC TABLE

The characteristic table for this type of flip-flop exhibits the transition of present state to next state based on the input conditions and clock triggers.

SR Flip-Flop Characteristic Table			
S	R	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X





# SR FLIPFLOP EXCITATION TABLE



The excitation table of SR flip-flop indicate the excitations required to take the flip-flop from the present state to the next state.

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0



# SR FLIPFLOP CHARACTERISTIC EQUATION



The characteristic equation is an algebraic expression for the characteristic table's binary information. It specifies the value of the next state of a flip-flop in terms of its present state and present excitation.

		$RQ_n$			
$S$		00	01	11	10
0			1		
1		1	1	x	x

The characteristic equation of SR flip-flop from the above K-map is

$$Q_{n+1} = S + \bar{R}Q_n$$



# Assessment

1. What is the difference between latch and Flipflop?

---

2. List few applications of Flipflop.

---



*Thank  
you*

