

***DIGITAL ELECTRONICS:***  
***T FLIPFLOP***





# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai




## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

### T FlipFlop

*Dr.G.Arthy*  
*Assistant Professor*  
*Department of EEE*  
*SNS College of Engineering*
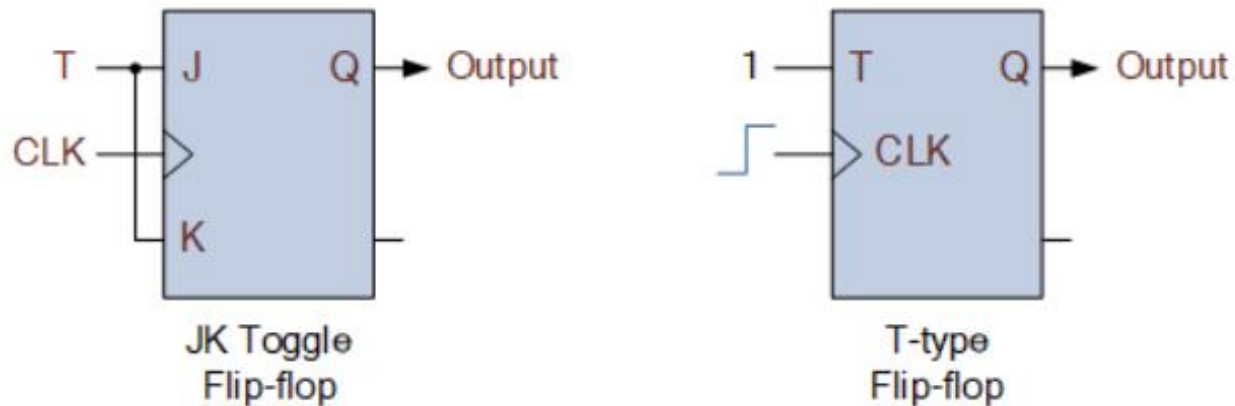
# T FLIPFLOP

- ✓ The “T flip flop,” is a single input version of JK flipflop.
- ✓ T Flipflop is obtained from the JK type if both inputs are tied together.
- ✓ The output of the T flipflop “toggles” with each clock pulse.






# T FLIPFLOP

## APPLICATIONS


- ✓ Counters
- ✓ Shift Registers
- ✓ Memory Units
- ✓ Frequency Division
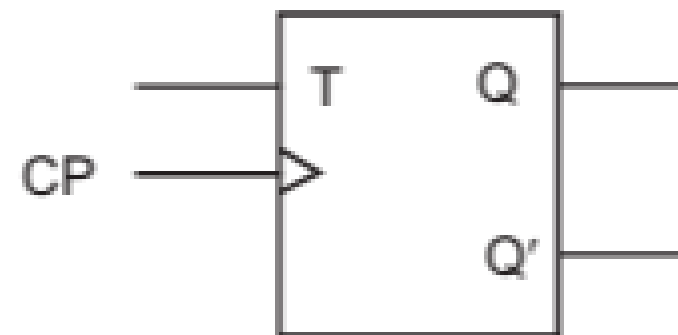
# T FLIP FLOP

- ✓The inputs will affect the output only when the clock signal changes from low to high for positive, or from high to low for negative.
- ✓However, when an edge applied to the clock input, the Flip-Flop will hold or latch the last output (Q) if  $T=0$ , and will toggle it to its complement if  $T=1$ .



# T FLIPFLOP WITH NAND GATE

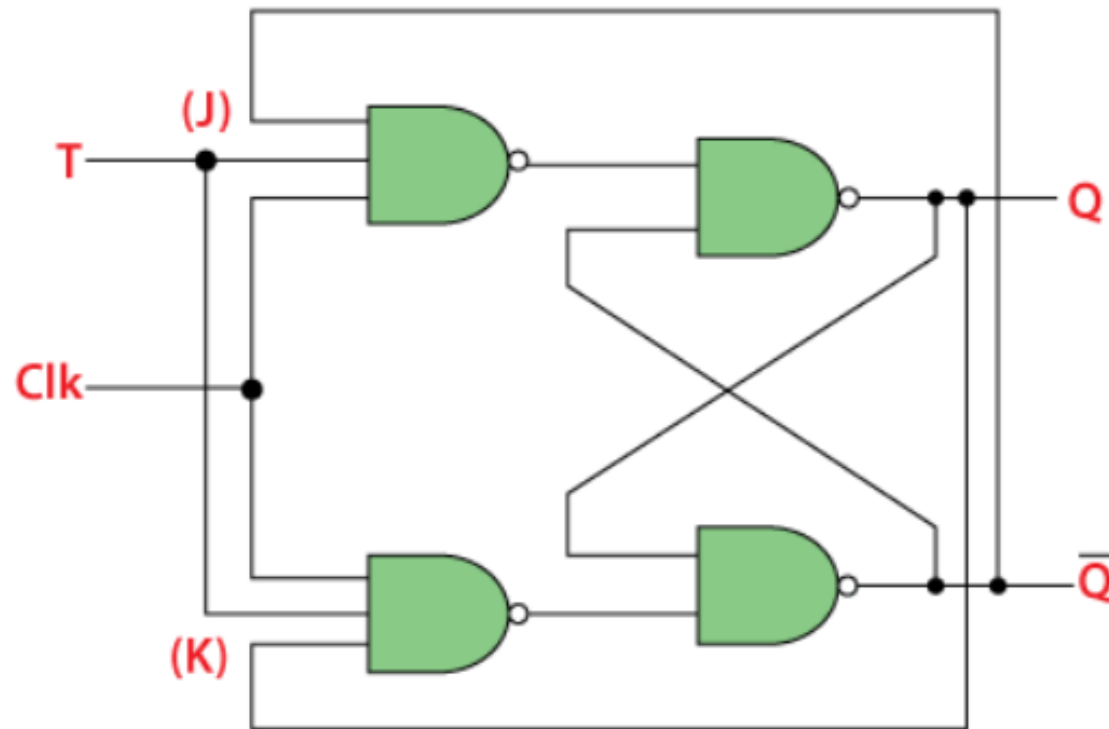

# T FLIPFLOP TRUTH TABLE

T	$Q_n$	$Q_{n+1}$	
0	0	0	Unchanged/hold
0	1	1	Unchanged/hold
1	0	1	Toggle
1	1	0	Toggle

# T FLIPFLOP CHARACTERISTIC TABLE

The characteristic table for this type of flip-flop exhibits the transition of present state to next state based on the input conditions and clock triggers.

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0





# T FLIPFLOP EXCITATION TABLE



The excitation table of T flip-flop indicate the excitations required to take the flip-flop from the present state to the next state.

T	$Q_n$	$Q_{n+1}$	
0	0	0	Unchanged/hold
0	1	1	Unchanged/hold
1	0	1	Toggle
1	1	0	Toggle



# T FLIPFLOP CHARACTERISTIC EQUATION



The characteristic equation is an algebraic expression for the characteristic table's binary information. It specifies the value of the next state of a flip-flop in terms of its present state and present excitation.

T \ Q <sub>n</sub>	0	1
0	0	1
1	1	0

The table is annotated with the following terms:

- $TQ_n'$  (blue arrow) points to the cell where T=0 and Q<sub>n</sub>=1 (value 1).
- $T'Q_n$  (red arrow) points to the cell where T=1 and Q<sub>n</sub>=0 (value 1).
- Cells are numbered 0, 1, 2, 3 in red.
- Cells containing '1' are circled in blue and red.

$$Q(n+1) = TQ_n' + T'Q_n = T \text{ XOR } Q_n$$



# Assessment

1. How many input terminal does T FF has?

a) 1

b) 2

c) 3

2. Write the Characteristic Equation of T FF

---



*Thank  
you*

