

DIGITAL ELECTRONICS:
SYNCHRONOUS UP COUNTERS





SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

An Autonomous Institution

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SYNCHRONOUS UP COUNTERS

Dr.G.Arthy
Assistant Professor
Department of EEE
SNS College of Engineering



SYNCHRONOUS UP COUNTERS



- ✓ A counter is a device which can count any particular event on the basis of how many times the particular event(s) is occurred.
- ✓ Counters are implemented using Flipflops.
- ✓ In synchronous counter, the clock input across all the flip-flops use the same source and create the same clock signal at the same time. So, a counter which is using the same clock signal from the same source at the same time is called Synchronous counter.



SYNCHRONOUS UP COUNTERS

APPLICATIONS

- ✓ Machine Motion control
- ✓ Motor RPM counter
- ✓ Rotary Shaft Encoders
- ✓ Digital clock or pulse generators.
- ✓ Digital Watch and Alarm systems.



DESIGN PROCEDURE



- ✓ **Step 1:** Select the required number of flipflops and the type of flipflops.
- ✓ **Step 2:** Draw the excitation table for the Flipflop.
- ✓ **Step 3:** Draw the state diagram.
- ✓ **Step 4:** Draw the excitation table for the logic diagram.
- ✓ **Step 5:** Draw K Map to find the minimal Boolean expression.
- ✓ **Step 6:** Draw the logic diagram for the up counter.



Problem Statement



Design a Synchronous 3 bit Up Counter



Step 1 :Select the required number of flipflops and the type of flipflops.

- Let us consider JK Flip Flop
- Since it is a 3 bit counter we need 3 flip flops.




Step 2: Draw the excitation table for the Flipflop.



Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	0
1	0	X	1
1	1	X	0

Step 3: Draw the state diagram

 

Step 4: Draw the excitation table for the logic diagram

Clock	Present State			Next State			Flip flop Inputs					
	Q_C	Q_B	Q_A	Q_{C+1}	Q_{B+1}	Q_{A+1}	J_C	K_C	J_B	K_B	J_A	K_A
1	0	0	0	0	0	1	0	X	0	X	1	X
2	0	0	1	0	1	0	0	X	1	X	X	1
3	0	1	0	0	1	1	0	X	X	0	1	X
4	0	1	1	1	0	0	1	X	X	1	X	1
5	1	0	0	1	0	1	X	0	0	X	1	X
6	1	0	1	1	1	0	X	0	1	X	X	1
7	1	1	0	1	1	1	X	0	X	0	1	X
8	1	1	1	0	0	0	X	1	X	1	X	1

Step 5: Draw K Map to find the minimal Boolean expression.

For J_c

$Q_2 Q_1$	Q_c	00	01	11	10
0	0	0	1	0	0
1	1	X	X	X	X

$$J_c = Q_2 Q_1$$

For K_c

$Q_2 Q_1$	Q_c	00	01	11	10
0	0	X	X	X	X
1	1	0	0	1	0

$$K_c = Q_2 Q_1$$

For J_b

$Q_2 Q_1$	Q_c	00	01	11	10
0	0	0	1	X	X
1	1	0	1	X	X

$$J_b = Q_1$$

For K_b

$Q_2 Q_1$	Q_c	00	01	11	10
0	0	X	X	1	0
1	1	X	X	1	0

$$K_b = Q_1$$

For J_a

$Q_2 Q_1$	Q_c	00	01	11	10
0	0	1	X	X	1
1	1	1	X	X	1

$$J_a = 1$$

For K_a

$Q_2 Q_1$	Q_c	00	01	11	10
0	0	X	1	1	X
1	1	X	1	1	X

$$K_a = 1$$

Step 6: Draw the logic diagram for the up counter.

$$J_A = 1$$


$$K_A = 1$$

$$J_B = Q_A$$

$$K_B = Q_A$$

$$J_C = Q_B Q_A$$

$$K_C = Q_B Q_A$$

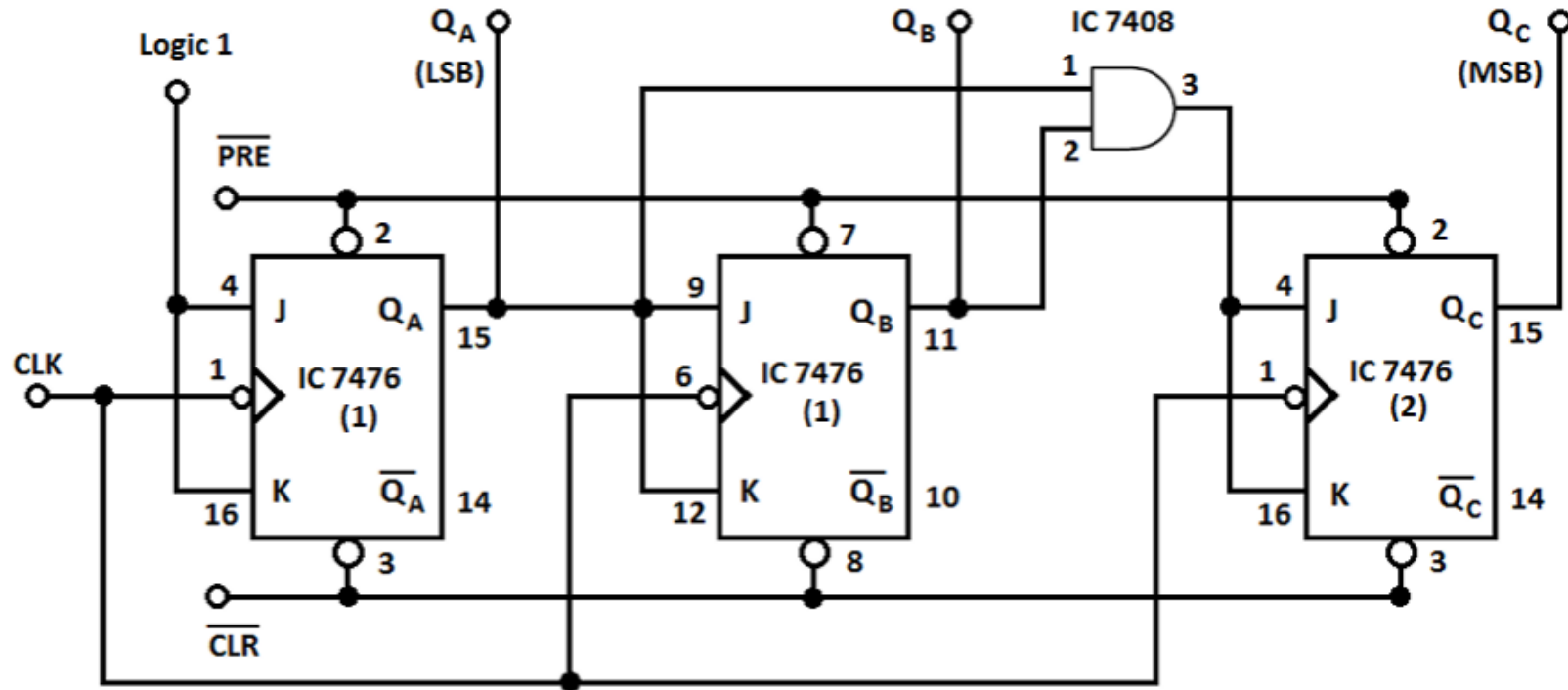



Assessment

1. How many Flipflops are required to design a 4 bit Counter?

2. How many states will be there for a 3 bit counter?



*Thank
you*

