

DIGITAL ELECTRONICS:
SYNCHRONOUS UP DOWN COUNTERS





SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

An Autonomous Institution

Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SYNCHRONOUS UP DOWN COUNTERS

***Dr.G.Arthy
Assistant Professor
Department of EEE
SNS College of Engineering***



SYNCHRONOUS UP DOWN COUNTERS



- ✓ A counter is a device which can count any particular event on the basis of how many times the particular event(s) is occurred.
- ✓ Counters are implemented using Flipflops.
- ✓ In synchronous counter, the clock input across all the flip-flops use the same source and create the same clock signal at the same time. So, a counter which is using the same clock signal from the same source at the same time is called Synchronous counter.



SYNCHRONOUS UP DOWN COUNTERS



APPLICATIONS

- ✓ Microprocessors
- ✓ Timers
- ✓ Digital clock or pulse generators.
- ✓ Frequency dividers



DESIGN PROCEDURE



- ✓ **Step 1:** Select the required number of flipflops and the type of flipflops.
- ✓ **Step 2:** Draw the excitation table for the Flipflop.
- ✓ **Step 3:** Draw the state diagram.
- ✓ **Step 4:** Draw the excitation table for the logic diagram.
- ✓ **Step 5:** Draw K Map to find the minimal Boolean expression.
- ✓ **Step 6:** Draw the logic diagram for the up Down counter.



Problem Statement



Design a Synchronous 3 bit Up Down Counter



Step 1 :Select the required number of flipflops and the type of flipflops.

- To perform 3 bit Up Down counting, 3 Flip Flops are required, which can count up to $2^3-1 = 7$.
- Here T Flip Flop is used.



Step 2: Draw the excitation table for the Flipflop.




Previous state(Q_n)	Next state(Q_{n+1})	T
0	0	0
0	1	1
1	0	1
1	1	0

Step 3: Draw the state diagram

Mode control input M

When $M=0$, then the counter will perform up counting.

 When $M=1$, then the counter will perform down counting.



Step 4: Draw the excitation table for the logic diagram

M	Q ₃	Q ₂	Q ₁	Q ₃ [*]	Q ₂ [*]	Q ₁ [*]	T ₃	T ₂	T ₁
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	0	1	0	0	0	1

Step 5: Draw K Map to find the minimal Boolean expression.

		Q_2Q_1			
		00	01	11	10
MQ_3	00	0	0	1	0
	01	0	0	1	0
	11	1	0	0	0
	10	1	0	0	0

$$T_3 = M'Q_2Q_1 + MQ_2'Q_1'$$

		Q_2Q_1			
		00	01	11	10
MQ_3	00	0	1	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	0	0	1

$$T_2 = M'Q_1 + MQ_1'$$

		Q_2Q_1			
		00	01	11	10
MQ_3	00	1	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1


$$T_1 = 1$$

Step 6: Draw the logic diagram for the up down counter.

$$T_3 = M'Q_2Q_1 + MQ_2'Q_1'$$

$$T_2 = M'Q_1 + MQ_1'$$

$$T_1 = 1$$

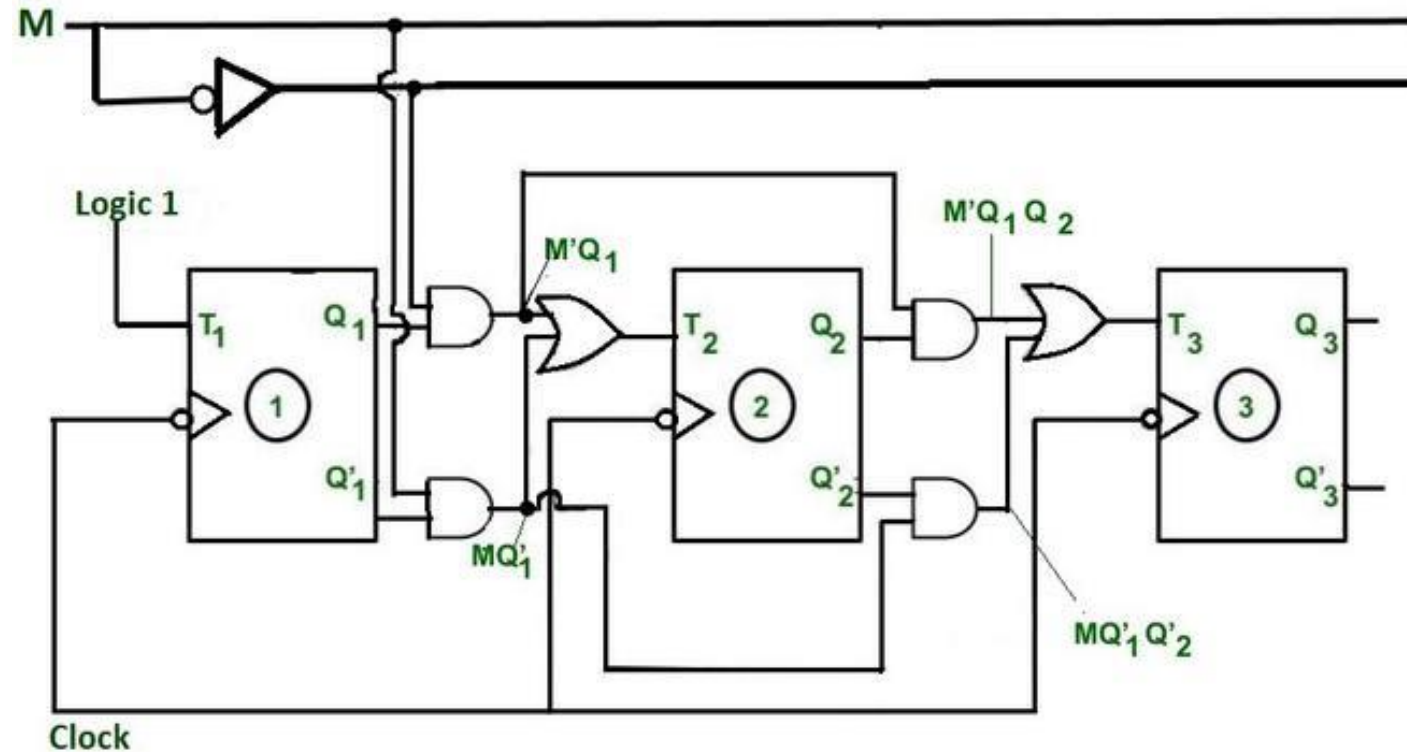



Assessment

1. How many Flipflops are required to design a 4 bit Counter?

2. How many states will be there for a 3 bit counter?



*Thank
you*

