



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF COMPUTER SCIENCE AND DESIGN

COURSE NAME : 19EE01 BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

I YEAR /II SEMESTER - COMPUTER SCIENCE AND DESIGN

Unit 1 – Electrical Circuits and Measurements

Topic 2 : Ohms' Law

DEFINITION


- The potential difference (voltage) across an ideal conductor is proportional to the current through it. The constant of proportionality is called the "resistance", R .

- $I = V/R$
- $V = IR$
- $R = V/I$


I = Current

V = Voltage


R = Resistance

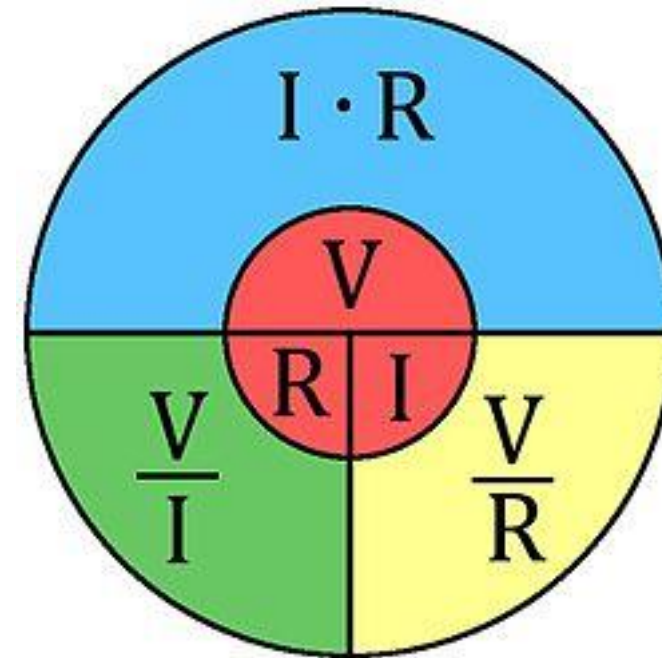


Simple Circuits with Ohm's Law

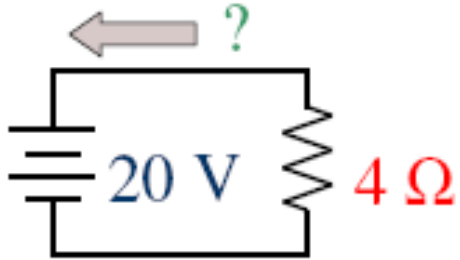

$$I = (20/4) = 5 \text{ A}$$

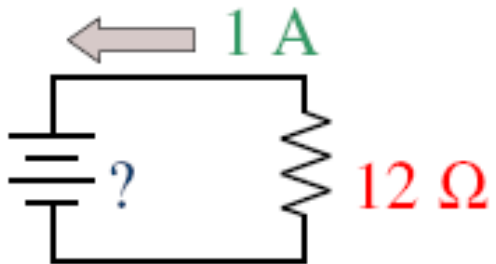

$$V = 1 \times 12 = 12 \text{ V}$$

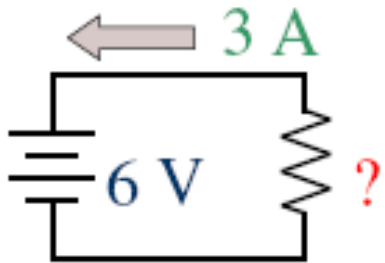



$$R = (6 / 3) = 2 \text{ ohms}$$

Can you solve?

1. $V = 14 \text{ V}, I = 2 \text{ A}, R = ?$
2. $V = 25 \text{ V}, I = 5 \text{ A}, R = ?$
3. $V = 6 \text{ V}, I = 1.5 \text{ A}, R = ?$
4. $V = 24 \text{ V}, I = 4 \text{ A}, R = ?$



LINEAR PROPORTION BETWEEN V & I

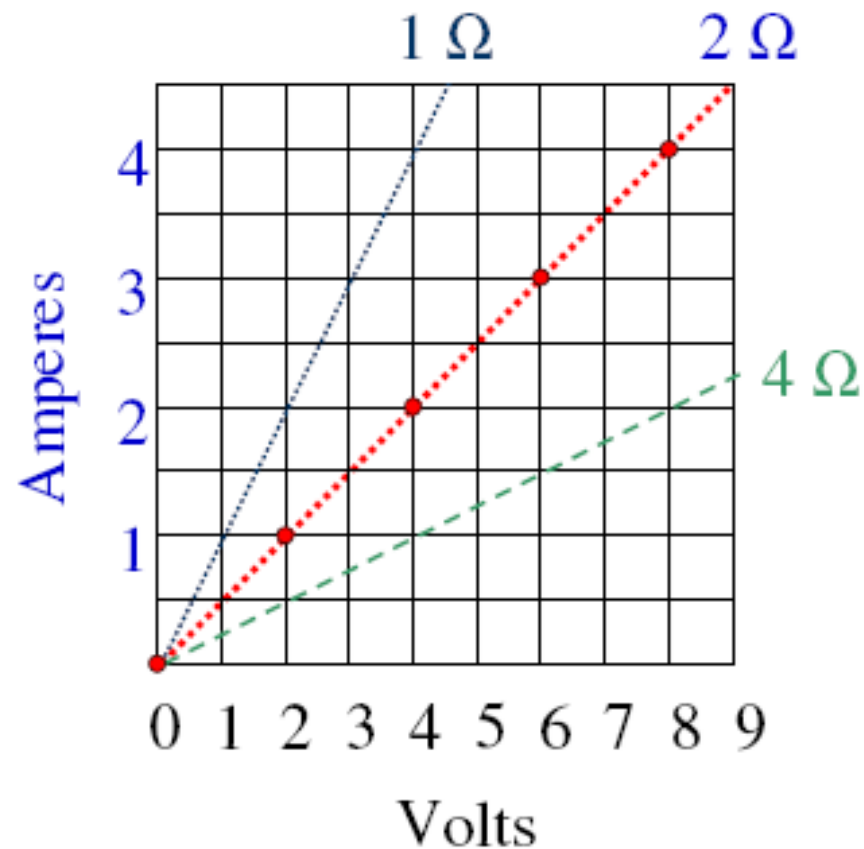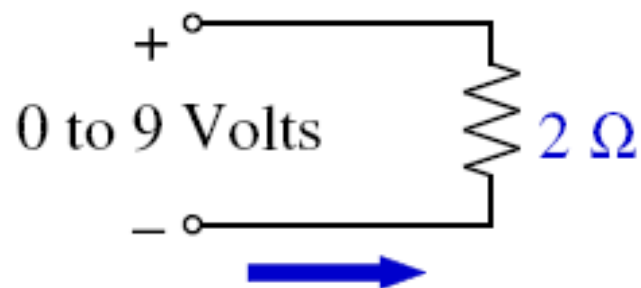



Power Dissipation in Resistance

- The amount of power dissipated in a resistance may be calculated using any one of three formulas, depending on which factors are known
- $P = I^2 \times R$
- $P = V^2 / R$
- $P = V \times I$



Assessment 2

1. Solve for the power, P , dissipated by the resistance, R

a. $I = 1 \text{ A}$, $R = 100\Omega$, $P = ?$

b. $I = 20 \text{ mA}$, $R = 1\Omega$, $P = ?$

c. $V = 5 \text{ V}$, $R = 150\Omega$, $P = ?$

d. $V = 22.36 \text{ V}$, $R = 1\Omega$, $P = ?$

2. How much power is dissipated by an 8Ω load if the current in the load is 200 mA ?



Limitations of Ohm's Law

- 1) This law cannot be applied to unilateral networks.
- 2) Ohm's law is also not applicable for non – linear elements.





REFERENCES

1. Bhattacharya. S.K, “Basic Electrical and Electronics Engineering”, Pearson Education , (2017)
2. Muthu Subramanian R, Salivahanan S,“ Basic Electrical and Electronics Engineering”, Tata McGraw Hill Publishers, (2009)
3. V.Mittle“ Basic Electrical Engineering”, Tata McGraw Hill Publishers, (2017)
4. Nagrath. I.J, “Electronics: Analog and Digital”, Prentice Hall India Pvt. Ltd., (2013)

THANK YOU