

## **UNIT 1: ELECTRICAL CIRCUITS & MEASUREMENTS**

### **Two-Mark Questions:**

1. **What is Ohm's Law?**
2. **State Kirchhoff's Current Law (KCL).**
3. **State Kirchhoff's Voltage Law (KVL).**
4. **Explain the difference between RMS value and peak value in AC circuits.**
5. **What is power factor in an AC circuit?**
6. **Explain the principle of a moving coil ammeter.**
7. **What are the limitations of a moving iron instrument?**
8. **Describe the operation of a dynamometer type wattmeter.**
9. **What is the function of an energy meter?**
10. **Derive the expression for the RMS value of a sinusoidal voltage.**
11. **What is the significance of the power factor in AC circuits?**
12. **What is the difference between active power and apparent power?**
13. **State the working principle of a moving iron voltmeter.**
14. **How does an ammeter measure current?**
15. **What are the main components of an energy meter?**
16. **Explain how a wattmeter measures power in AC circuits.**
17. **Explain the principle of operation of a dynamometer type wattmeter.**
18. **Calculate the power consumed by a resistive load of  $10\ \Omega$  in an AC circuit with a voltage of 230 V and power factor 1.**
19. **What is the role of a capacitor in an AC circuit?**
20. **What is the significance of the voltage-current characteristics of a diode?**
21. **How is power calculated in an AC circuit with a given current and voltage?**
22. **What is meant by the energy consumed by a system?**
23. **What is a phase shift in an AC circuit, and how is it measured?**

24. Calculate the apparent power in an AC circuit where the active power is 300 W and the power factor is 0.8.
25. What is the difference between direct current (DC) and alternating current (AC)?

**Problems:**

- Problem 1:**  
A  $10\ \Omega$  resistor is connected across a 100 V DC supply. Calculate the current flowing through the resistor using Ohm's Law.
- Problem 2:**  
In a series AC circuit, the resistance is  $10\ \Omega$  and the reactance is  $20\ \Omega$ . Calculate the total impedance and current if the applied voltage is 100 V.
- Problem 3:**  
Calculate the RMS value of a sinusoidal current of peak value 5 A.
- Problem 4:**  
A coil has a resistance of  $10\ \Omega$  and an inductance of 0.2 H. If the frequency of the AC source is 50 Hz, calculate the impedance of the coil.
- Problem 5:**  
A 10 W light bulb is connected to an AC circuit with a voltage of 110 V and a power factor of 0.9. Calculate the current flowing through the circuit.