

UNIT 4: ANALOG ELECTRONICS

Two-Mark Questions:

- 1. What is the working principle of a diode?**
- 2. Explain the function of a Zener diode.**
- 3. What are the applications of a diode in electronic circuits?**
- 4. Explain the working of a Half-Wave Rectifier.**
- 5. What is the difference between a half-wave and full-wave rectifier?**
- 6. Explain the operation of a BJT (Bipolar Junction Transistor).**
- 7. What is the application of a Zener diode as a voltage regulator?**
- 8. What is the working of a MOSFET?**
- 9. What is the principle of a voltage regulator circuit?**
- 10. State the applications of a UPS (Uninterruptible Power Supply).**
- 11. What are the advantages of a full-wave rectifier over a half-wave rectifier?**
- 12. Explain the input and output characteristics of a BJT.**
- 13. What is the significance of the threshold voltage in a MOSFET?**
- 14. What are the advantages of using a Zener diode for voltage regulation?**
- 15. How does a capacitor filter work in a rectifier circuit?**
- 16. What are the key parameters of a diode?**
- 17. What is the principle of operation of a rectifier?**
- 18. What is a rectified signal, and how does it relate to the input AC signal?**
- 19. Explain the working principle of a UPS system.**
- 20. What is the role of a diode in a half-wave rectifier?**
- 21. Explain the difference between an ideal diode and a real diode.**
- 22. What is the function of the load resistor in a rectifier circuit?**
- 23. What is the significance of the cut-in voltage of a diode?**
- 24. How does a BJT amplify a small signal?**

25. What are the advantages of a voltage regulator in electronic circuits?

Problems:

1. Problem 1:

Design a full-wave bridge rectifier circuit. Calculate the DC output voltage if the AC input is 10 V RMS.

2. Problem 2:

Calculate the efficiency of a half-wave rectifier with a resistive load of 100 Ω and an input voltage of 120 V RMS.

3. Problem 3:

A diode has a forward voltage of 0.7 V and a current of 20 mA. Calculate the power dissipated in the diode.

4. Problem 4:

Design a voltage regulator using a Zener diode for a 12 V output with a 15 V input.

5. Problem 5:

Calculate the current flowing through a 10 Ω resistor connected to a 12 V battery with a forward-biased silicon diode in series.