UNIT 1: ELECTRICAL CIRCUITS & MEASUREMENTS

1. What does Ohm's Law state?

- a) Voltage is proportional to current
- b) Current is proportional to resistance
- c) Voltage is proportional to resistance
- d) Voltage is equal to current times resistance

2. Which of the following is the unit of resistance?

- a) Ampere
- b) Volt
- c) Ohm
- d) Watt

3. What is the formula for calculating the total resistance in a series circuit?

- a) R_total = R1 + R2
- b) R_total = R1 R2
- c) R_total = 1 / (R1 + R2)
- d) R_total = (R1 * R2) / (R1 + R2)

4. What does the RMS value of an AC voltage represent?

- a) Peak voltage
- b) Average voltage
- c) Equivalent DC voltage
- d) Instantaneous voltage

5. In AC circuits, power factor is defined as the ratio of:

- a) Active power to reactive power
- b) Apparent power to reactive power
- c) Active power to apparent power
- d) Reactive power to apparent power

6. Which type of instrument is used for measuring very high voltages?

- a) Moving iron voltmeter
- b) Moving coil voltmeter
- c) Induction wattmeter
- d) Digital voltmeter

7. The back EMF in a DC motor depends on:

- a) Speed of the motor
- b) Resistance of the armature

- c) Magnetic flux
- d) All of the above

8. Which of the following is the principle of operation of a moving coil ammeter?

- a) Electromagnetic induction
- b) Electrostatic force
- c) Magnetic torque
- d) Thermoelectric effect

9. The power factor in an AC circuit is zero when the load is:

- a) Resistive
- b) Capacitive
- c) Inductive
- d) Reactive

10. What is the unit of electric power?

- a) Ampere
- b) Volt
- c) Watt
- d) Ohm

11. Which of the following laws applies to current distribution in a parallel circuit?

- a) Ohm's Law
- b) Kirchhoff's Current Law
- c) Kirchhoff's Voltage Law
- d) Faraday's Law

12. Which type of wattmeter is used for measuring power in a three-phase system?

- a) Induction wattmeter
- b) Dynamometer wattmeter
- c) Digital wattmeter
- d) Moving coil wattmeter

13. What is the total impedance of a series R-L circuit where R = 5 Ω and L = 0.1 H at a frequency of 50 Hz?

- a) 10 Ω
- b) 15 Ω
- c) 5.5 Ω
- d) 6.5 Ω
- 14. A 100 V RMS sinusoidal AC voltage produces a current of 5 A. The average power delivered to the load is:

- a) 500 W
- b) 700 W
- c) 450 W
- d) 250 W

15. Which of the following instruments measures both AC and DC voltage?

- a) Moving coil voltmeter
- b) Digital voltmeter
- c) Moving iron voltmeter
- d) Galvanometer

16. The average value of a sinusoidal current is:

- a) 0.637 times the peak value
- b) 0.707 times the peak value
- c) 0.9 times the RMS value
- d) Zero

17. What is the principle of operation of a dynamometer-type wattmeter?

- a) Electromagnetic induction
- b) Magnetic coupling
- c) Electrostatic force
- d) Electric torque

18. In a power measurement system, if the power factor is less than 1, it indicates:

- a) A purely resistive load
- b) A purely capacitive load
- c) A reactive load
- d) No power loss

19. Which of the following devices is used to measure the energy consumption in an electrical circuit?

- a) Ammeter
- b) Voltmeter
- c) Energy meter
- d) Wattmeter

20. The total current in a parallel circuit is the sum of the currents through each branch. This statement is related to:

- a) Ohm's Law
- b) Kirchhoff's Current Law

c) Kirchhoff's Voltage Lawd) Faraday's Law