



# **SNS COLLEGE OF ENGINEERING**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A’ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF COMPUTER SCIENCE AND DESIGN**

**COURSE NAME : 19EE01 BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

**I YEAR /II SEMESTER**

**Unit 5 – LINEAR AND DIGITAL ELECTRONICS**

**Topic 5 : Logic Gates**



## Logic Gates: AND, OR, NOT, NAND, NOR

The basic digital electronic circuit that has one or more inputs and single output is known as **Logic gate**. Hence, the Logic gates are the building blocks of any digital system. We can classify these Logic gates into the following three categories.

- Basic gates
- Universal gates
- Special gates

### Basic Gates

In earlier chapters, we learnt that the Boolean functions can be represented either in sum of products form or in product of sums form based on the requirement. So, we can implement these Boolean functions by using basic gates. The basic gates are AND, OR & NOT gates.

### AND gate


An AND gate is a digital circuit that has two or more inputs and produces an output, which is the **logical AND** of all those inputs. It is optional to represent the **Logical AND** with the symbol ‘..’.

The following table shows the **truth table** of 2-input AND gate.

A	B	$Y = A.B$
0	0	0
0	1	0
1	0	0
1	1	1

Here A, B are the inputs and Y is the output of two input AND gate. If both inputs are '1', then only the output, Y is '1'. For remaining combinations of inputs, the output, Y is '0'.

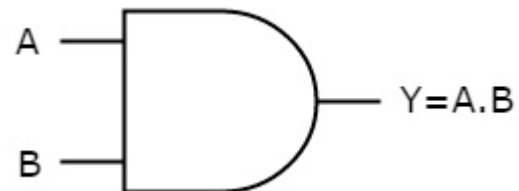The following figure shows the **symbol** of an AND gate, which is having two inputs A, B and one output, Y.






## OR gate

An OR gate is a digital circuit that has two or more inputs and produces an output, which is the logical OR of all those inputs. This **logical OR** is represented with the symbol '+’.

The following table shows the **truth table** of 2-input OR gate.

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

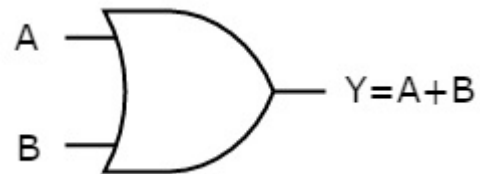Here A, B are the inputs and Y is the output of two input OR gate. If both inputs are '0', then only the output, Y is '0'. For remaining combinations of inputs, the output, Y is '1'. The following figure shows the **symbol** of an OR gate, which is having two inputs A, B and one output, Y.





## NOT gate


A NOT gate is a digital circuit that has single input and single output. The output of NOT gate is the **logical inversion** of input. Hence, the NOT gate is also called as inverter.

The following table shows the **truth table** of NOT gate.

A	$Y = A'$
0	1
1	0

Here A and Y are the input and output of NOT gate respectively. If the input, A is '0', then the output, Y is '1'. Similarly, if the input, A is '1', then the output, Y is '0'.

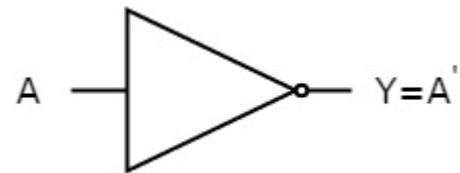The following figure shows the **symbol** of NOT gate, which is having one input, A and one output, Y.



## Universal gates


NAND & NOR gates are called as **universal gates**. Because we can implement any Boolean function, which is in sum of products form by using NAND gates alone. Similarly, we can implement any Boolean function, which is in product of sums form by using NOR gates alone.

### NAND gate

NAND gate is a digital circuit that has two or more inputs and produces an output, which is the **inversion of logical AND** of all those inputs.

The following table shows the **truth table** of 2-input NAND gate.

A	B	$Y = A \cdot B'$
0	0	1
0	1	1
1	0	1
1	1	0

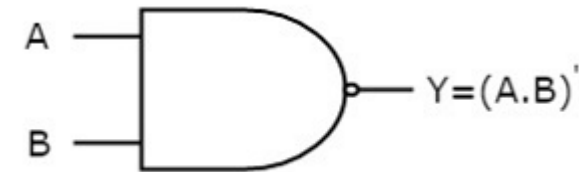

Here A, B are the inputs and Y is the output of two input NAND gate. When both inputs are '1', the output, Y is '0'. If at least one of the input is zero, then the output, Y is '1'. This is just opposite to that of two input AND gate operation.

The following image shows the **symbol** of NAND gate, which is having two inputs A, B and one output, Y.

## NOR gate


NOR gate is a digital circuit that has two or more inputs and produces an output, which is the **inversion of logical OR** of all those inputs.

The following table shows the **truth table** of 2-input NOR gate

A	B	$Y = A + B '$
0	0	1
0	1	0
1	0	0
1	1	0

Here A, B are the inputs and Y is the output. If both inputs are '0', then the output, Y is '1'. If at least one of the input is '1', then the output, Y is '0'. This is just opposite to that of two input OR gate operation.

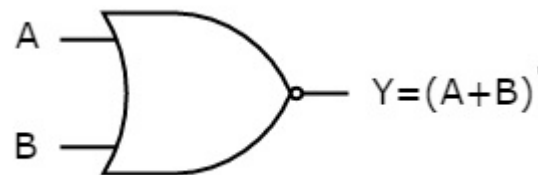The following figure shows the **symbol** of NOR gate, which is having two inputs A, B and one output, Y.




## Special Gates

Ex-OR & Ex-NOR gates are called as special gates. Because, these two gates are special cases of OR & NOR gates.

### Ex-OR gate

The full form of Ex-OR gate is **Exclusive-OR** gate. Its function is same as that of OR gate except for some cases, when the inputs having even number of ones. The following table shows the **truth table** of 2-input Ex-OR gate.

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

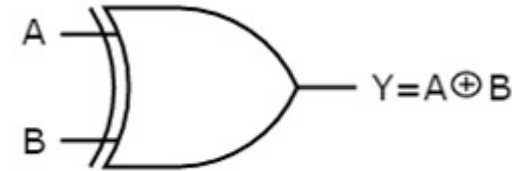

Here A, B are the inputs and Y is the output of two input Ex-OR gate. The truth table of Ex-OR gate is same as that of OR gate for first three rows. The only modification is in the fourth row. That means, the output  $y$  is zero instead of one, when both the inputs are one, since the inputs having even number of ones. Therefore, the output of Ex-OR gate is '1', when only one of the two inputs is '1'. And it is zero, when both inputs are same. Below figure shows the **symbol** of Ex-OR gate, which is having two inputs A, B and one output, Y.




## Ex-NOR gate

The full form of Ex-NOR gate is **Exclusive-NOR** gate. Its function is same as that of NOR gate except for some cases, when the inputs having even number of ones.

The following table shows the **truth table** of 2-input Ex-NOR gate.

A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

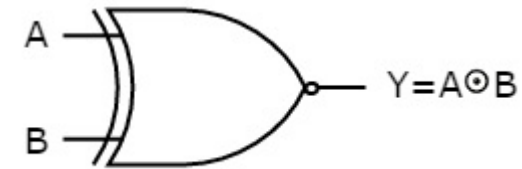

Here A, B are the inputs and Y is the output. The truth table of Ex-NOR gate is same as that of NOR gate for first three rows. The only modification is in the fourth row. That means, the output is one instead of zero, when both the inputs are one.

Therefore, the output of Ex-NOR gate is '1', when both inputs are same. And it is zero, when both the inputs are different.

The following figure shows the **symbol** of Ex-NOR gate, which is having two inputs A, B and one output, Y.


# Implementation of Logic Functions Using Only NAND Gates

## Logic Gates using only NAND Gates


NAND Gate Symbol




AND Gate

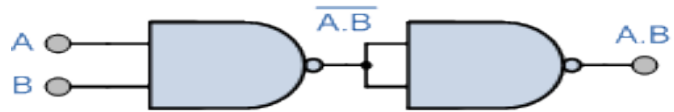


OR Gate

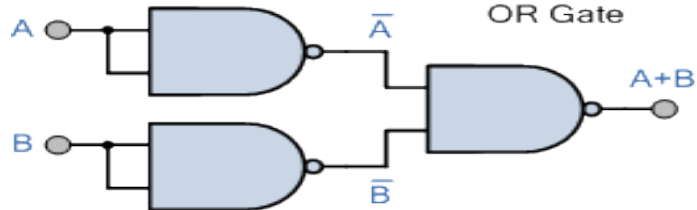


NOR Gate

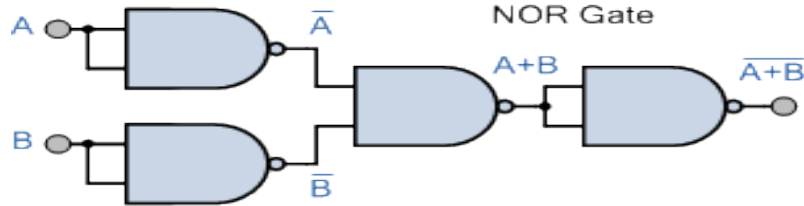


NOT Gate  
(Inverter)

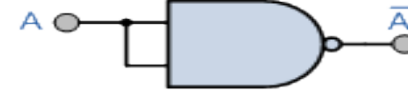


Buffer

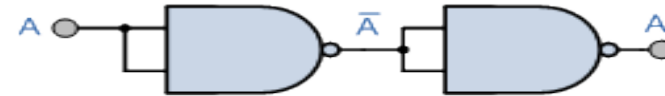


Exclusive-OR

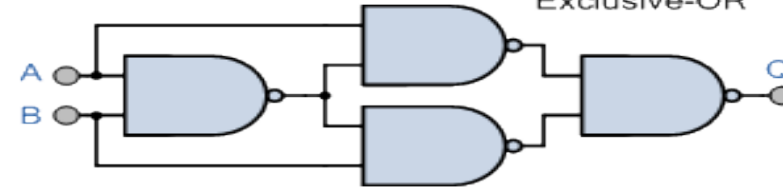

Exclusive-NOR

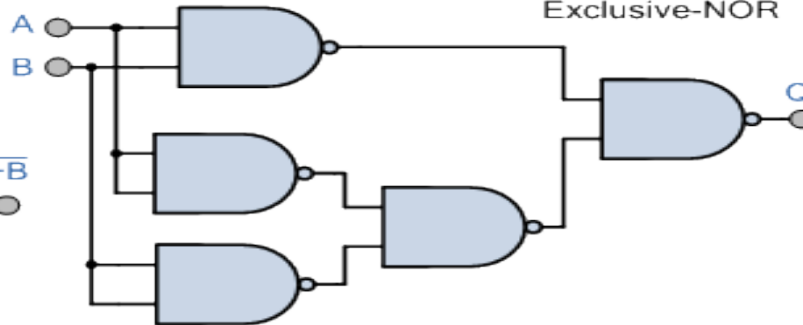

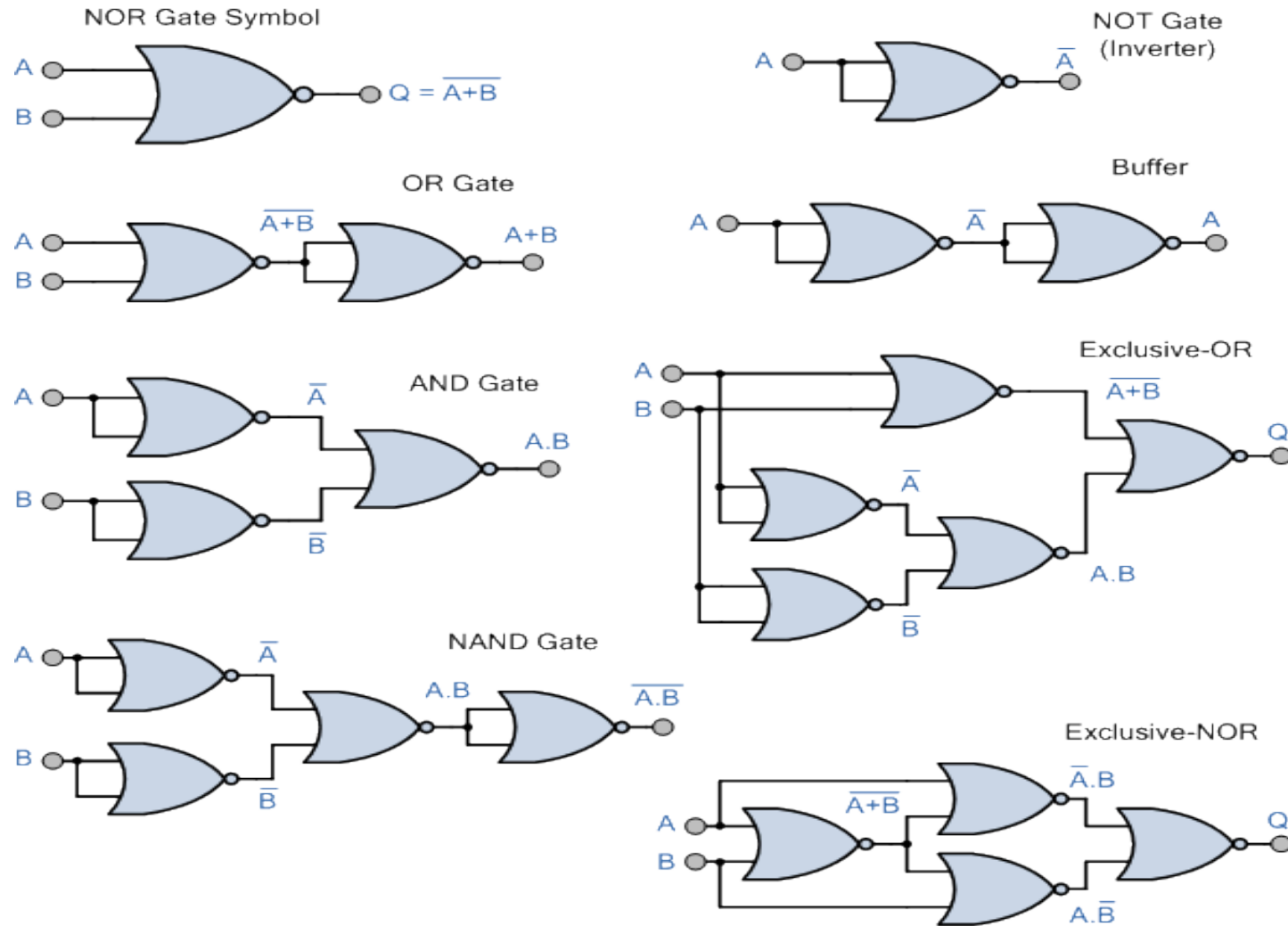



Any Query????

Thank you.....