



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF COMPUTER SCIENCE AND DESIGN

**COURSE NAME : 19EE01 BASIC ELECTRICAL AND ELECTRONICS
ENGINEERING**

I YEAR /II SEMESTER - COMPUTER SCIENCE AND DESIGN


Topic 7 : Full Adders

Design procedure – **Full Adders** / **19EE01 / BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**
/Mr.S.HARIBABU/ECE/SNSCE



Full Adder

- Full Adder is the adder that adds three inputs and produces two outputs. The first two inputs are A and B and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM. The C-OUT is also known as the majority 1's detector, whose output goes high when more than one input is high. A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to another. we use a full adder because when a carry-in bit is available, another 1-bit adder must be used since a 1-bit half-adder does not take a carry-in bit. A 1-bit full adder adds three operands and generates 2-bit results.

 




Adder Truth Table:

Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Logical Expression for SUM: $= A' B' C-IN + A' B C-IN' + A B' C-IN' + A B C-IN = C-IN (A' B' + A B) + C-IN' (A' B + A B') = C-IN \text{ XOR } (A \text{ XOR } B) = (1,2,4,7)$


Logical Expression for C-OUT: $= A' B C-IN + A B' C-IN + A B C-IN' + A B C-IN = A B + B C-IN + A C-IN = (3,5,6,7)$

Another form in which C-OUT can be implemented: $= A B + A C\text{-IN} + B C\text{-IN} (A + A') = A B C\text{-IN} + A B + A C\text{-IN} + A' B C\text{-IN} = A B (1 + C\text{-IN}) + A C\text{-IN} + A' B C\text{-IN} = A B + A C\text{-IN} + A' B C\text{-IN} = A B + A C\text{-IN} (B + B') + A' B C\text{-IN} = A B C\text{-IN} + A B + A B' C\text{-IN} + A' B C\text{-IN} = A B (C\text{-IN} + 1) + A B' C\text{-IN} + A' B C\text{-IN} = A B + A B' C\text{-IN} + A' B C\text{-IN} = AB + C\text{-IN} (A' B + A B')$
 Therefore $COUT = AB + C\text{-IN} (A \text{ EX - OR } B)$

 

Implementation of Full Adder using Half Adders:

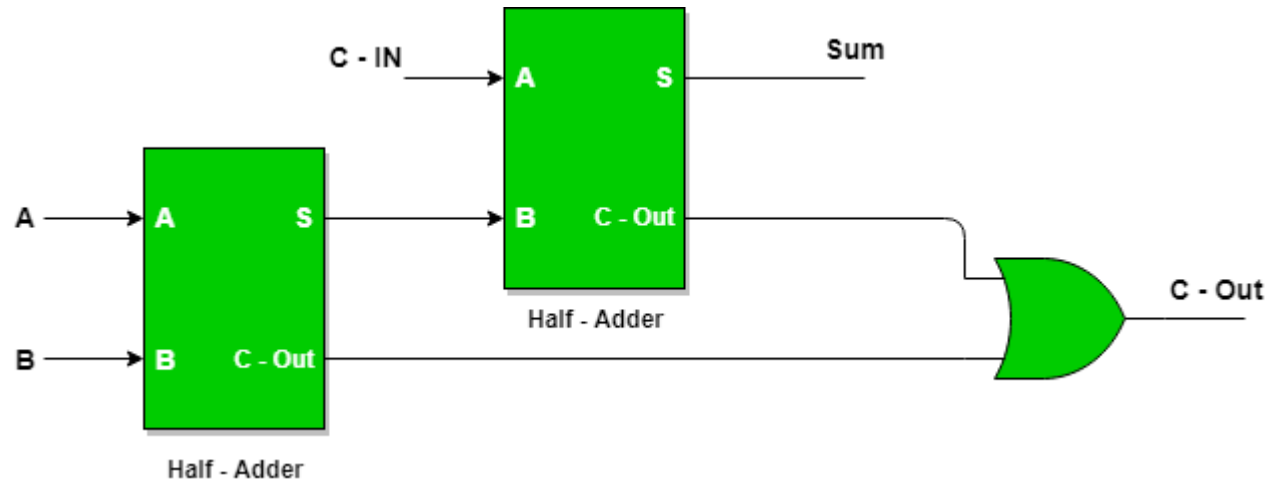2 Half Adders and an OR gate is required to implement a Full Adder.



With this logic circuit, two bits can be added together, taking a carry from the next lower order of magnitude, and sending a carry to the next higher order of magnitude.



Any Query????

Thank you.....