



# SNS COLLEGE OF ENGINEERING

**Coimbatore-35**

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade Approved by AICTE,  
New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

I ECE / II SEMESTER

### Unit 2 –NETWORK REDUCTION AND THEOREMS FOR DC AND

#### AC CIRCUITS

Topic 1 –Network reduction: voltage and current division,

23ECT101/Circuit Theory /V.Pavithra AP/ECE

## Introduction:

- Kirchhoff's Voltage Law states that that “The algebraic sum of all the voltages in a loop must equal zero”. A practical application of this law is the voltage divider rule.
- Kirchhoff's Current Law states that “The algebraic sum of all currents entering and exiting a node must equal zero.” A practical Application of this law is current divider rule.
- A parallel circuit acts as a current divider as the current divides in all the branches in a parallel circuit.
- A series circuit act as a voltage divider as the voltage divides in all the branches in a series circuit.

## Voltage Divider Rule:

- Calculate equivalent resistance.
- In series:

$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$

- Calculate current by applying Ohm's Law ( $I = V/R_{eq}$ ).
- Current remains same in series

$$I = I_1 = I_2 = I_3$$

- As voltage divides in series, So Voltage Divider Rule states that;

$$V_x = V \left( \frac{R_x}{R_x + R_y + R_z} \right)$$

## Example:

- $V_1 = (5/5+10+7.5) \times 45$   
 $= 5/22.5 \times 45$


$$V_1 = 10V$$

- $V_2 = (10/5+10+7.5) \times 45$   
 $= 10/22.5 \times 45$

$$V_2 = 20V$$

- $V_3 = (7.5/5+10+7.5) \times 45$

$$V_3 = 15V$$

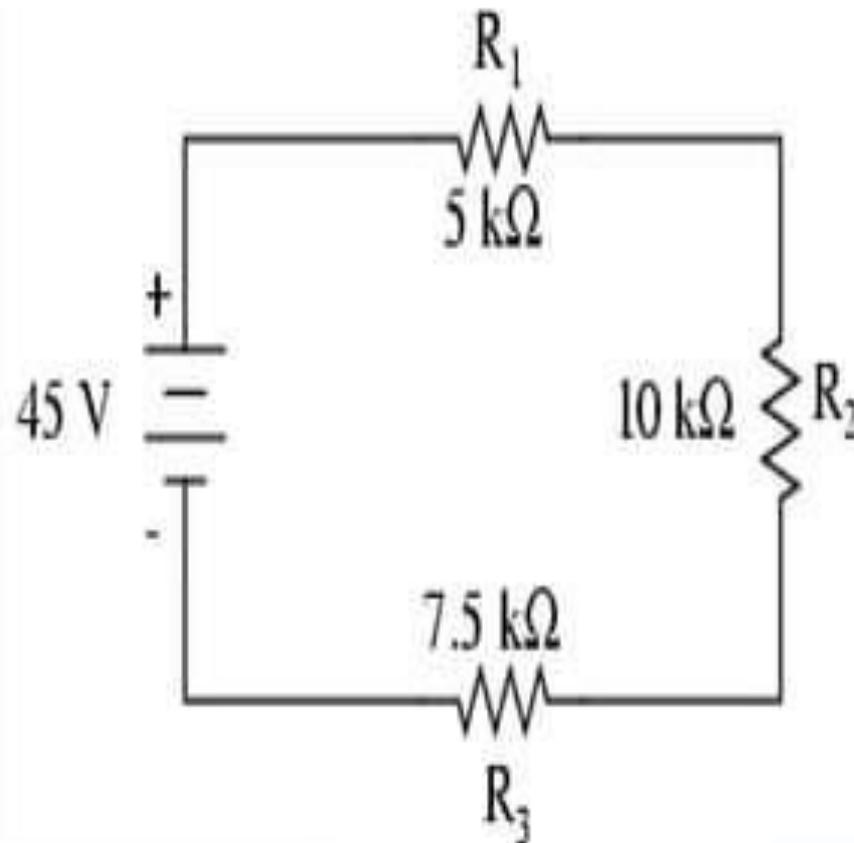

## Application:

- The voltage divider is used only there where the voltage is regulated by dropping a particular voltage in a circuit. It mainly used in such systems where energy efficiency does not necessary to be considered seriously.
- In our daily life, most commonly the voltage divider is used in potentiometers.
- The best examples for the potentiometers are the volume tuning knob attached to our music systems and radio transistors, etc

## Current Divider Rule:

- Calculate equivalent resistance.
- In parallel circuit;

$$R_{eq} = R_1 R_2 R_3 / R_2 R_3 + R_1 R_3 + R_2 R_1$$

- Calculate current by applying Ohm's Law ( $I = V / R_{eq}$ ).
- As voltage remains same in parallel circuit;

$$V_1 = V_2 = V_3 = V$$

- As current divides in parallel circuit, So according to current divider rule:

$$I_x = (R_t / R_x) \times I$$

## Example:

- $1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$

- $R_{eq} = 0.54\Omega$

- $I_t = V/R_{eq}$

$$I_t = 11.11A$$

- $I_1 = (R_t/R_1) \times I_t$


$$I_1 = (0.54/1) \times 11.11$$

$$I_1 = 6A$$

- $I_2 = (R_t/R_2) \times I_t$

$$I_2 = 2A$$

- $I_3 = 3.11A$

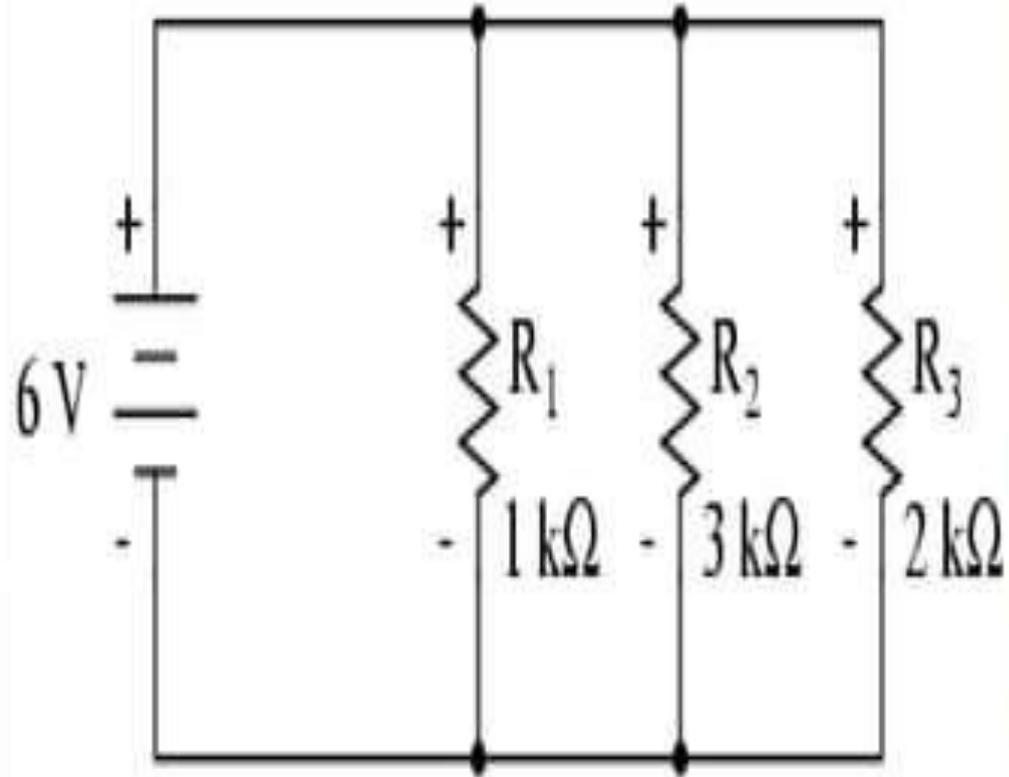

## Method 2:

- $I_1 = (R_2 \parallel R_3 / R_1 + R_2 \parallel R_3) \times I_t$

$$I_1 = 6A$$

- $I_2 = (R_1 \parallel R_3 / R_2 + R_1 \parallel R_3) \times I_t$

$$I_2 = 2A$$


- $I_3 = (R_1 \parallel R_2 / R_3 + R_1 \parallel R_2) \times I_t$

$$I_3 = 2.97A$$

## Application:

- Current divider circuits also find application in electric meter circuits, where a fraction of measured current is desired to be routed through a sensitive detection device.
- Using the current divider formula, the proper shunt resistor can be sized to proportion just the right amount of current for the device in any given instance

# Complex Circuit:

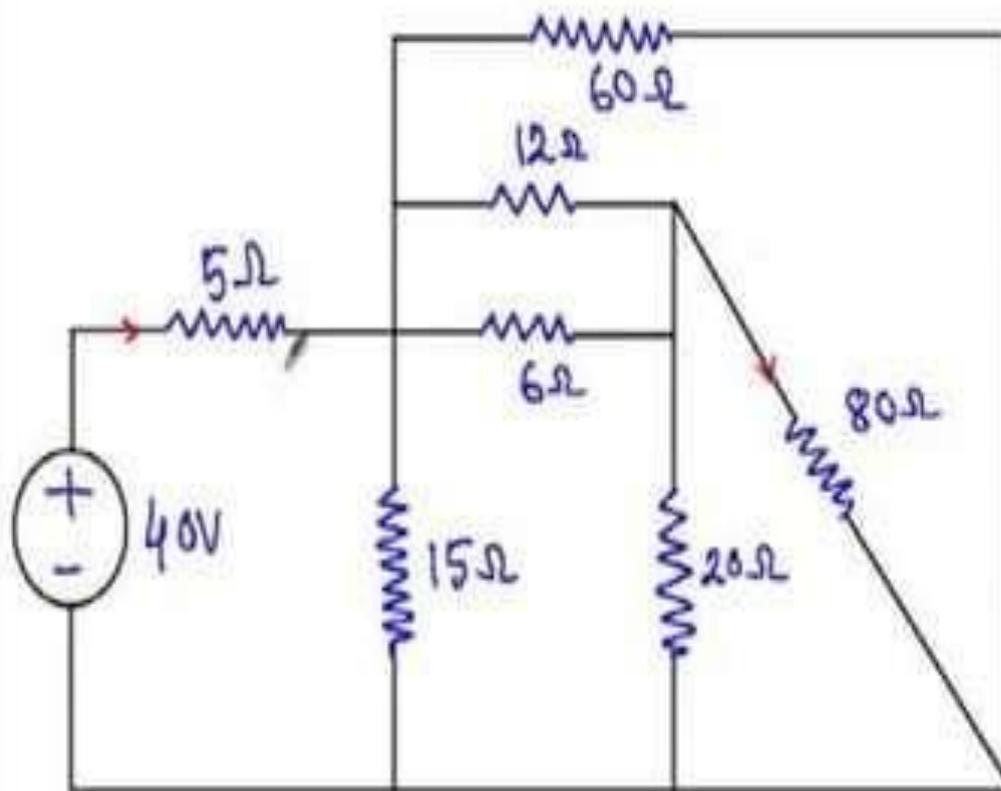

*Thank  
you*

