



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

AN AUTONOMOUS INSTITUTION



Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai

II Semester

B.E – Department of Computer Science and Engineering

(Internet of Things & Cyber Security including Block Chain Technology)

23ECT102 – ELECTRONIC DEVICES AND CIRCUITS

Regulations -2023

PUZZLES

☒ UNIT I – Transistor Biasing and Stabilisation

1. Match the Terms

Term	Definition Letter
------	-------------------

A. Q-point	a. Graphical method to find transistor operation
------------	--

B. Fixed Bias	b. Collector current stable against temperature
---------------	---

C. Self Bias	c. Set operating point of the transistor
--------------	--

D. Load Line	d. Uses one resistor from base to Vcc
--------------	---------------------------------------

Answer: A→c, B→d, C→b, D→a

2. Fill in the Blanks

1. The _____ bias offers the best thermal stability.
2. _____ is the point of intersection of DC and AC load lines.
3. Stabilization factor denotes the change in _____ current due to temperature.
4. In fixed bias, base resistor connects between _____ and base.

Answer:

1. Voltage divider

2. Q-point
 3. Collector
 4. Vcc
-

3. True or False

1. Self-bias requires only one resistor. ✗
 2. DC load line is independent of the transistor parameters. ✓
 3. Operating point should lie in saturation region. ✗
 4. Stabilization factor S should be as low as possible. ✓
-

4. Word Search

Find these hidden words: **QPOINT, BIAS, STABILITY, FIXED, THERMAL**

5. Anagram Puzzle

Unscramble the biasing method:

1. DEXFI = _____
2. LOLVAGET RIVEDID = _____
3. LECTROLOC-OT-BASE = _____

Answer: Fixed, Voltage Divider, Collector-to-Base

✓ UNIT II – P-N Junction Diode

1. Crossword Puzzle Clues

- **Across:**
 2. Sharp increase in current under reverse bias (**Zener**)
- **Down:**
 1. Diode used for tuning circuits (**Varactor**)

2. Region where no free carriers exist (**Depletion**)
-

2. Word Match

Diode Type Use Case

- A. Zener a. Light detection
- B. Varactor b. Voltage regulation
- C. Photodiode c. Tuning circuits

Answer: A→b, B→c, C→a

3. True or False

1. A diode conducts in reverse bias. ✗
 2. Varactor diodes work as variable capacitors. ✓
 3. Photodiode requires forward bias to operate. ✗
 4. Zener diodes can regulate voltage. ✓
-

4. Fill in the Blanks

1. Zener diode operates in _____ breakdown region.
2. The _____ voltage is the threshold for conduction.
3. _____ diodes emit light when forward biased.
4. In reverse bias, the current is due to _____ carriers.

Answer:

1. Zener
2. Knee
3. LED
4. Minority

5. Find the Odd One Out

Which is not a special-purpose diode?

- A. Zener
- B. Varactor
- C. Resistor
- D. Photodiode

Answer: C. Resistor

✓ UNIT III – BJT and Amplifier Analysis

1. Label the Configuration

Given a transistor circuit with the base as common terminal, identify:

- Input between ____ and ____
- Output between ____ and ____

Answer: Emitter and Base, Collector and Base (Common Base configuration)

2. Matching

Parameter	Symbol
A. Current gain	a. β
B. Input impedance	b. Z_{in}
C. Voltage gain	c. A_v
D. Output impedance	d. Z_{out}

Answer: A→a, B→b, C→c, D→d

3. Word Search

Find these: **HYBRID, GAIN, BETA, CE, SATURATION**

4. Crossword Clues

- **Across:**

1. Current gain in CE configuration

- **Down:**

2. Region where both junctions are forward biased
3. Base current is minimal in this configuration

Answer: Beta, Saturation, CB

5. True or False

1. $\beta = I_C/I_E$. ✗
 2. Hybrid model simplifies amplifier analysis. ✓
 3. Common collector has highest voltage gain. ✗
 4. CB configuration is used in RF amplifiers. ✓
-

✓ UNIT IV – FET and FET Amplifier

1. Fill in the Blanks

1. FETs are _____ controlled devices.
2. In JFET, drain current becomes constant after _____ voltage.
3. The region where FET behaves like a resistor is called _____ region.
4. MOSFET has _____ input impedance.

Answer: Voltage, Pinch-off, Ohmic, High

2. Word Match

Term	Description
A. JFET	a. Uses gate voltage for control
B. MOSFET	b. Insulated gate
C. Pinch-off	c. Voltage at which current saturates

Answer: A→a, B→b, C→c

3. Word Search

Find: **PINCHOFF, MOSFET, SOURCE, GATE, ENHANCEMENT**

4. Crossword Clues

- **Across:**
 1. Terminal of FET controlling current (**Gate**)
 2. Output terminal (**Drain**)
 - **Down:**
 1. Region after which current saturates (**Saturation**)
 2. FET where gate is insulated (**MOSFET**)
-

5. True or False

1. FETs have low input impedance. ✗
 2. MOSFET can operate in enhancement mode. ✓
 3. Source and drain are interchangeable in all FETs. ✗
 4. Pinch-off voltage is important in JFETs. ✓
-

✓ UNIT V – Rectifiers and Filters

1. Matching

Component	Function
-----------	----------

A. Rectifier	a. Smooth output voltage
--------------	--------------------------

B. Filter	b. Converts AC to DC
-----------	----------------------

C. Zener Diode	c. Regulates voltage
----------------	----------------------

Answer: A→b, B→a, C→c

2. Fill in the Blanks

1. A _____ rectifier allows current in one half cycle.
2. Ripple factor indicates _____ in output.
3. π -filter contains _____ and _____.
4. Bridge rectifier uses _____ diodes.

Answer: Half-wave, AC components, Inductor, Capacitor, 4

3. True or False

1. A capacitor filter charges during conduction. ☒
 2. Full-wave rectifiers have higher ripple than half-wave. ☐
 3. Zener diodes work in forward bias for regulation. ☐
 4. PIV is maximum voltage a diode can block in reverse bias. ☒
-

4. Word Search

Find: **RECTIFIER, FILTER, RIPPLE, ZENER, BRIDGE**

5. Crossword Clues

- **Across:**

1. Diode used in voltage regulation

2. Filter using L and C components
- **Down:**
 1. Converts AC to pulsating DC
 2. Output of full-wave rectifier is _____ than half-wave

Answer: Zener, LC, Rectifier, Smoother