

UNIT IV OPERATIONAL AMPLIFIER

Syllabus


Ideal OPAMP characteristics, DC performance characteristics, Basic applications of OPAMP- Sign Changer, Scale Changer, Phase Shift Circuits, Voltage Follower, adder, subtractor, Integrator, Differentiator

BASICS OF OPERATIONAL AMPLIFIER

Operational Amplifier, also called as an Op-Amp, is an integrated circuit, which can be used to perform various linear, non-linear, and mathematical operations. An op-amp is a **direct coupled high gain amplifier**. We can operate op-amp both with AC and DC signals.

Construction of Operational Amplifier

An op-amp consists of a differential amplifier(s), a level translator and an output stage. A differential amplifier is present at the input stage of an op-amp and hence an op-amp consists of **two input terminals**. One of those terminals is called as the **inverting terminal** and the other one is called as the **non-inverting terminal**. The terminals are named based on the phase relationship between their respective inputs and outputs.

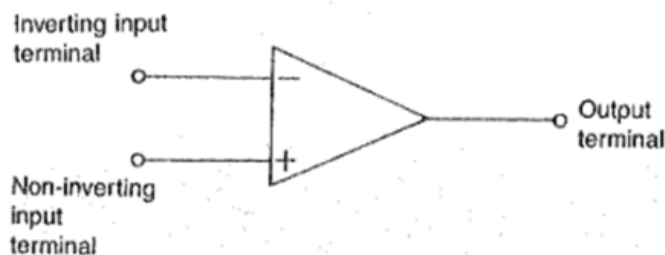

Characteristics of Operational Amplifier

The important characteristics or parameters of an operational amplifier are as follows –

- Open loop voltage gain
- Output offset voltage
- Common Mode Rejection Ratio
- Slew Rate

Open loop voltage gain

The open loop voltage gain of an op-amp is its differential gain without any feedback path.

Mathematically, the open loop voltage gain of an op-amp is represented as –

$$A_v = \frac{v_0}{v_1 - v_2}$$

Output offset voltage

The voltage present at the output of an op-amp when its differential input voltage is zero is called as **output offset voltage**.

Common Mode Rejection Ratio

Common Mode Rejection Ratio (**CMRR**) of an op-amp is defined as the ratio of the closed loop differential gain, A_d and the common mode gain, A_c .

Mathematically, CMRR can be represented as –

$$CMRR = \frac{A_d}{A_c}$$

Note that the common mode gain, A_c of an op-amp is the ratio of the common mode output voltage and the common mode input voltage.

Slew Rate

Slew rate of an op-amp is defined as the maximum rate of change of the output voltage due to a step input voltage.

Mathematically, slew rate (SR) can be represented as –

$$SR = \text{Maximum of } \frac{dV_0}{dt}$$

Where, V_0 is the output voltage.

In general, slew rate is measured in either $V/\mu\text{Sec}$ or $V/m\text{Sec}$.


TYPES OF OPERATIONAL AMPLIFIERS

An op-amp is represented with a triangle symbol having two inputs and one output.

Op-amps are of two types: **Ideal Op-Amp** and **Practical Op-Amp**.

IDEAL OP-AMP

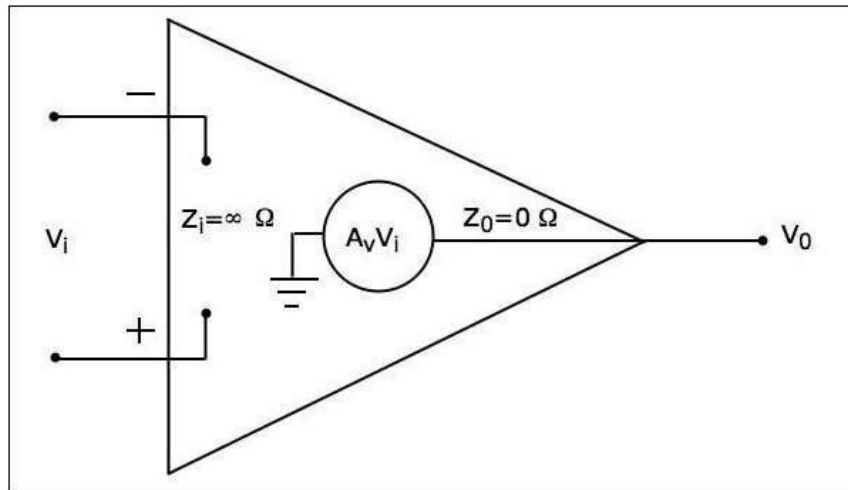An ideal op-amp exists only in theory, and does not exist practically. The **equivalent circuit** of an ideal op-amp is shown in the figure given below –




An ideal op-amp characteristics

- Input impedance $Z_i = \infty \Omega$
- Output impedance $Z_o = 0 \Omega$
- Open loop voltage gain $A_v = \infty$
- If (the differential) input voltage $V_i = 0V$, then the output voltage will be $V_o = 0V$
- Bandwidth is **infinity**. It means, an ideal op-amp will amplify the signals of any frequency without any attenuation.
- Common Mode Rejection Ratio (**CMRR**) is **infinity**.
- Slew Rate (**SR**) is **infinity**. It means, the ideal op-amp will produce a change in the output instantly in response to an input step voltage.

Practical Op-Amp

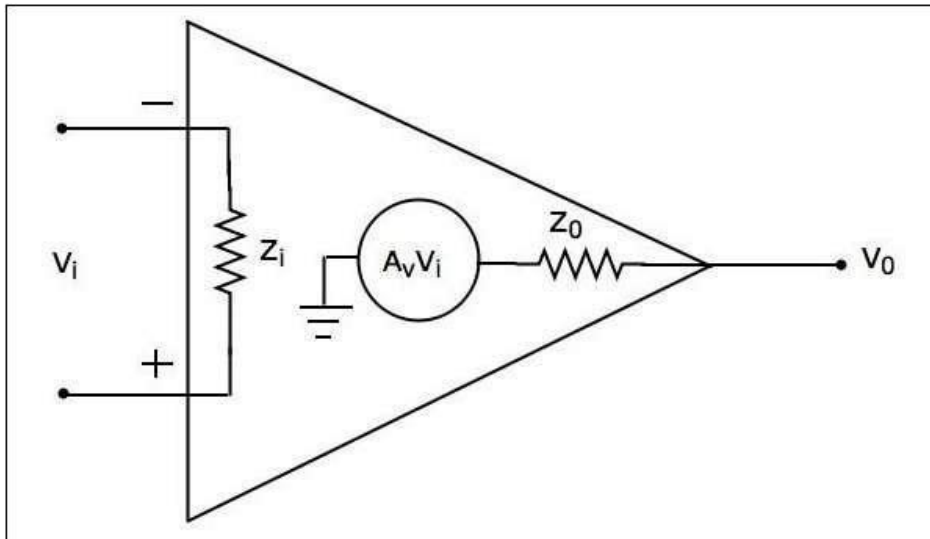Practically, op-amps are not ideal and deviate from their ideal characteristics because of some imperfections during manufacturing. The **equivalent circuit** of a practical op-amp is shown in the following figure –



A **practical op-amp** exhibits the following characteristics –

- Input impedance, Z_i in the order of **Mega ohms**.
- Output impedance, Z_o in the order of **few ohms**.
- Open loop voltage gain, A_v will be **high**.

When you choose a practical op-amp, you should check whether it satisfies the following conditions –

- Input impedance, Z_i should be as high as possible.
- Output impedance, Z_o should be as low as possible.
- Open loop voltage gain, A_v should be as high as possible.
- Output offset voltage should be as low as possible.
- The operating Bandwidth should be as high as possible.
- CMRR should be as high as possible.
- Slew rate should be as high as possible.

Note – IC 741 op-amp is the most popular and practical op-amp.