

PROBLEMS

Problem 1

Design an amplifier with a gain of -10 and input resistance equal to $10\text{ k}\Omega$.

Solution


Since the gain of the amplifier is negative, an inverting amplifier has to be made.

In Fig. 2.5 (a) choose $R_1 = 10\text{ k}\Omega$

$$\begin{aligned}\text{Then } R_f &= -A_{CL} R_1 \text{ (from Eq. 2.4)} \\ &= -(-10) \times 10\text{ k}\Omega = 100\text{ k}\Omega\end{aligned}$$

 Problem 2

In Fig. 2.5 (b), $R_1 = 10\text{ k}\Omega$, $R_f = 100\text{ k}\Omega$, $v_i = 1\text{ V}$. A load of $25\text{ k}\Omega$ is connected to the output terminal. Calculate (i) i_1 (ii) v_o (iii) i_L and total current i_o into the output pin.



Solution

$$(a) \quad i_1 = \frac{v_i}{R_1} = \frac{1\text{ V}}{10\text{ k}\Omega} = 0.1\text{ mA}$$

$$(b) \quad v_o = -\frac{R_f}{R_1} v_i = -\frac{100\text{ k}\Omega}{10\text{ k}\Omega} 1\text{ V} = -10\text{ V}$$

$$(c) \quad i_L = \frac{v_o}{R_L} = \frac{10\text{ V}}{25\text{ k}\Omega} = 0.4\text{ mA}$$

The direction of i_L is shown in Fig. 2.5 (b).

$$(d) \quad i_1 \text{ as calculated above is } 0.1\text{ mA.}$$

Therefore, total current $i_o = i_1 + i_L = 0.1\text{ mA} + 0.4\text{ mA} = 0.5\text{ mA}$. In an inverting amplifier, for a +ive input, output will be -ive, therefore the direction of i_o is as shown in Fig. 2.5 (b).

Problem 3

Design an amplifier with a gain of +5 using one op-amp.

Solution


Since the gain is positive, we have to make a non-inverting amplifier.

In Fig. select $R_1 = 10 \text{ k}\Omega$. Then

$$A_{CL} = 1 + R_f/R_1$$

or, $5 = 1 + R_f/10 \text{ k}\Omega$

or, $R_f = 4 \times 10 \text{ k}\Omega = 40 \text{ k}\Omega$

 

Problem 4

- (a) For the non-inverting amplifier of Fig. 3.2 (b), $R_1 = 1 \text{ k}\Omega$ and $R_f = 10 \text{ k}\Omega$. Calculate the maximum output offset voltage due to V_{os} and I_B . The op-amp is LM 307 with $V_{os} = 10 \text{ mV}$ and $I_B = 300 \text{ nA}$, $I_{os} = 50 \text{ nA}$.
- (b) Calculate the value of R_{comp} needed to reduce the effect of I_B .
- (c) Calculate the maximum output offset voltage if R_{comp} as calculated in (b) is connected in the circuit.

Solution

$$\begin{aligned} \text{(a)} \quad V_{oT} &= \left(1 + \frac{R_f}{R_1}\right) V_{os} + R_f I_B \\ &= \left(1 + \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega}\right) (10 \text{ mV}) + (10 \text{ k}\Omega) (300 \text{ nA}) \\ &= 110 \text{ mV} + 3 \text{ mV} = 113 \text{ mV} \end{aligned}$$

- (b) The value of R_{comp} needed is,

$$R_{comp} = 1 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 990 \Omega$$

- (c) With R_{comp} in the circuit,

$$\begin{aligned} V_{oT} &= \left(1 + \frac{R_f}{R_1}\right) V_{os} + R_f I_{os} \\ &= 110 \text{ mV} + 0.5 \text{ mV} = 110.5 \text{ mV} \end{aligned}$$

Problem 5

A non-inverting amplifier with a gain of 100 is nulled at 25°C . What will happen to the output voltage if the temperature rises to 50°C for an offset voltage drift of $0.15 \text{ mV}/^\circ\text{C}$?

Solution

Input offset voltage due to temperature rise = $0.15 \text{ mV}/^\circ\text{C} \times (50^\circ\text{C} - 25^\circ\text{C}) = 3.75 \text{ mV}$. Since this is an input change, the output voltage will change by

$$\begin{aligned} V_o &= V_{os} \times A_{CL} \\ &= 3.75 \text{ mV} \times 100 = 375 \text{ mV} \end{aligned}$$

This could represent a very major shift in the output voltage.

Problem 6

Design an adder circuit using an op-amp to get the output expression as

$$V_o = -(0.1 V_1 + V_2 + 10 V_3)$$

where V_1 , V_2 , and V_3 are the inputs.

Solution

The output in Fig. 4.2 (a) is


$$V_o = -[(R_f/R_1) V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3]$$

say $R_f = 10 \text{ k}\Omega$, $R_1 = 100 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_3 = 1 \text{ k}\Omega$

Then the desired output expression is obtained.

 Problem 7[GATE EC 2010]

Assuming the OP-AMP to be ideal, the voltage gain of the amplifier shown below is




A $-\frac{R_2}{R_1}$


Correct Answer

 Problem 8 [GATE EE 2023]

Consider the OP AMP based circuit shown in the figure. Ignore the conduction drops of diodes D_1 and D_2 . All the components are ideal and the breakdown voltage of the Zener is 5 V. Which of the following statements is true?



 For positive half cycle the diodes D_1 and D_z are forward bias and D_2 is reverse biased and the circuit is shown below,




When $V_{in} = 10 \text{ V}$,

$$V_0 = \frac{-R}{R} \times 10 = -10 \text{ V}$$

$\therefore V_0$ will be -10 V .

 For negative half cycle, diode D_2 is forward bias and D_1, D_z is reverse bias. Zener diode is in breakdown region and the circuit is shown below,



$$\therefore V_0 = 5 \text{ V}$$

$$\Rightarrow V_{0\max} = 5 \text{ V and } V_{0\min} = -10 \text{ V}$$

Correct Answer

D

The maximum and minimum values of the output voltage V_0 are +5 V and -10 V, respectively.