

SNS COLLEGE OF ENGINEERING

Coimbatore-35 An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF CSE (IoT)

23ECT102- ELECTRONIC DEVICES AND CIRCUITS I YEAR/ II SEMESTER

UNIT 5 – Rectifier & Filters

TOPIC -FILTERS





- Harmonics are voltage or current waveforms with frequencies that are integer multiples of the fundamental frequency (e.g., 2×f, 3×f, etc.).
- In rectifiers, the output waveform is not purely DC—it contains distorted waveforms due to **the non-linear switching action** of diodes.
- This distortion leads to **harmonic components** in the output, especially in the absence of filtering.
- Harmonics can:
- Reduce efficiency of power systems,
- Cause overheating in motors and transformers,
- Lead to electromagnetic interference (EMI),
- Distort nearby signals in electronic circuits.
- Therefore, **filter circuits** are essential to **suppress harmonics** and provide a smoother DC output.



Types of Filters Used in Rectifiers



- To smooth the rectified output, different types of filters are used depending on the load requirements and ripple tolerance.
- The main types of filters are:
- **1. Inductor Filter**
- Uses an inductor (choke) in series with the load
- Blocks AC components while allowing DC to pass

2. Capacitor Filter

- Uses a capacitor in parallel with the load
- Bypasses AC to ground, allowing DC through

3. LC Filter (L-section Filter)

- Combines inductor and capacitor
- More effective in reducing ripple than individual filters

4. CLC Filter (π-type Filter)

- Two capacitors with an inductor in between
- Provides superior ripple suppression
 Common in high-quality regulated power supplies





- An **inductor filter** uses an inductor (also called a choke) placed in series with the rectifier output and the load.
- The inductor opposes changes in current due to its property of inductance (L), which makes it effective at blocking AC (ripple) components.
- It allows the DC component to pass through to the load with minimal resistance.
- More effective under **high load currents**, as the ripple reduction improves with increasing current.

Advantages:

- Simple design
- Effective for high-current applications

Disadvantages:

- Bulky and expensive
- Not suitable for light loads (poor filtering at low current)









• A capacitor filter uses a capacitor connected in parallel with the load at the output of the rectifier.

Working Principle:

- Capacitors store charge and resist changes in voltage.

– They bypass AC components (ripples) to ground while allowing DC to reach the load.

Ripple Reduction:

 The capacitor charges during the peaks of the waveform and discharges during valleys, smoothing the output.

- More effective for light or moderate loads.

Advantages:

- Simple, compact, and low cost
- Good ripple suppression at low currents

Disadvantages:

- Less effective under heavy load
- Can produce high peak currents during charging

Used in: Small DC power supplies, chargers, and electronic gadgets.



Capacitor Filter









- An LC filter (also called L-section filter) combines an inductor (L) in series and a capacitor (C) in parallel with the load.
 Working Principle:
- The **inductor** blocks high-frequency AC (ripple).
- The capacitor shunts remaining AC components to ground.

- Together, they provide **better ripple reduction** than single-component filters.

Advantages:

- More effective filtering
- Suitable for medium to high load currents

Disadvantages:

- Larger and more expensive than single filters
- Performance depends on load conditions.



LC (L-Section) Filter



L-C Filter - Inductor input L Section Filter



L - C Filter - Capacitor input Filter



5/20/2025



CLC (π-Type) Filter



- A CLC filter (also called a π -type filter) consists of:
- > A capacitor (C_1) connected in parallel at the input,
- > An inductor (L) in series,
- > Another **capacitor** (C_2) in parallel at the output.
- The arrangement looks like the Greek letter π (pi), hence the name.

Working Principle:

- •C₁ reduces the initial ripple by bypassing AC.
- •L blocks remaining AC components.
- •C₂ filters out any leftover ripple, giving a smooth DC output.

Advantages:

- •Excellent ripple reduction—even better than LC filters.
- •Provides a very stable DC voltage.

•Suitable for **high-load** and **sensitive electronic applications**. **Disadvantages:**

- •More costly and bulky (uses two capacitors and one inductor).
- •Requires good quality components for optimal performance.

Used in: High-end regulated power supplies, audio equipment, communication devices.

5/20/2025



CLC (π -Type) Filter





5/20/2025

Rectifiers & Filters/23ECT102- ELECTRONIC DEVICES AND CIRCUITS/D.KAVITHA /AP/CSE(IoT)/SNSCE

11



Comparison of Filters



Filter Type	Ripple Reduction	Suitable Load	Size / Cost	Remarks
Inductor Filter	Moderate	High current	Large / Expensive	Better at high load; bulky design
Capacitor Filter	Moderate	Light load	Small / Inexpensive	Simple and low-cost; poor at high load
LC (L-section)	Good	Medium to high load	Medium / Moderate cost	Balanced performance and size
CLC (π-type)	Excellent	High & sensitive loads	Large / Expensive	Best ripple suppression; costly & bulky

5/20/2025





Thank you!