

SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore - 641 107



AN AUTONOMOUS INSTITUTION


Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai

III Semester

B.E- Mechanical and Mechatronics Engineering (Additive Manufacturing) 23EEB204 – Electrical Machines and Power Systems Regulations 2023

Question 1


Find the odd word.

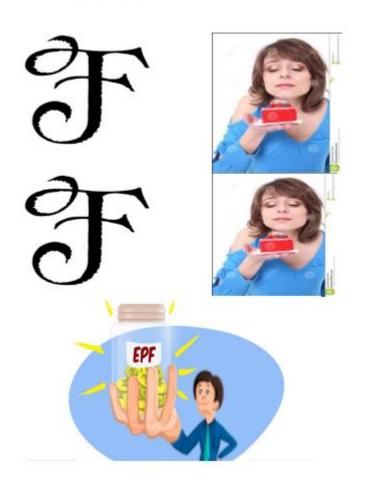



Question 2

The below diagram represents_____

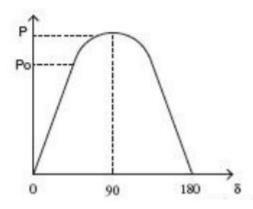

Question 3

The synchronizing power co-efficient is given as_____

Explain about the theory

Clue: Connect the pictures



