Department of Electrical and Electronics Engineering

Topic Name: Introduction to FACTS Duration: 10 Mins

No. of Questions : 04

1. Write the full for "FACTS"-

K-2

2. List out the needs for FACTS in AC Line

1._____

2.____


3._____

4._____

5.

K-2

3. Identify the Devices given below

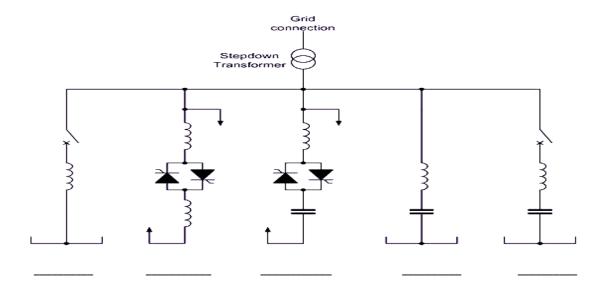

K-2