



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

AN AUTONOMOUS INSTITUTION



Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai

I Semester

B.E- Mechanical and Mechatronics Engineering (Additive Manufacturing)

23EET101 – Basics of Electrical and Electronics Engineering

Regulations 2023

Question 1


Find the odd word.

श
श



Question 2

The below diagram represents _____

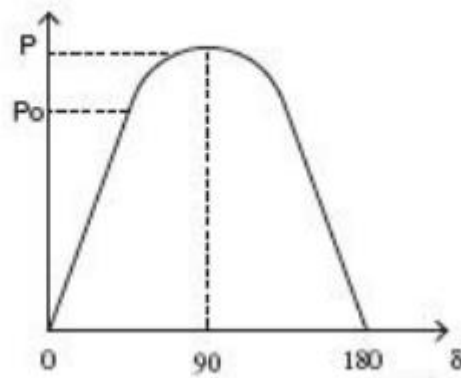

Question 3

The synchronizing power co-efficient is given as _____

Explain about the theory

Clue: Connect the pictures

